

UNIT 2 BIPOLAR JUNCTION TRANSISTORS


DR. GURLEEN KAUR WALIA

ASSISTANT PROFESSOR

SIGNAL AND IMAGE PROCESSING (ED2)

**SCHOOL OF ELECTRONICS & ELECTRICAL
ENGINEERING (SEEE)**


EMAIL ID: GURLEEN.24800@LPU.CO.IN

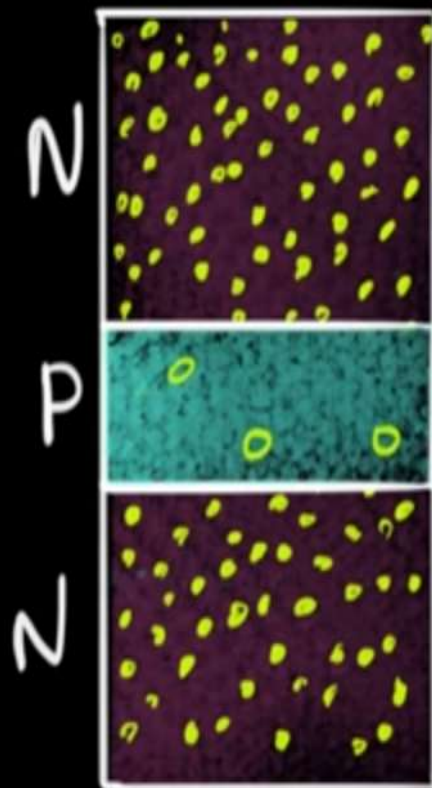



Transistor


① Very thin


② Very lightly doped

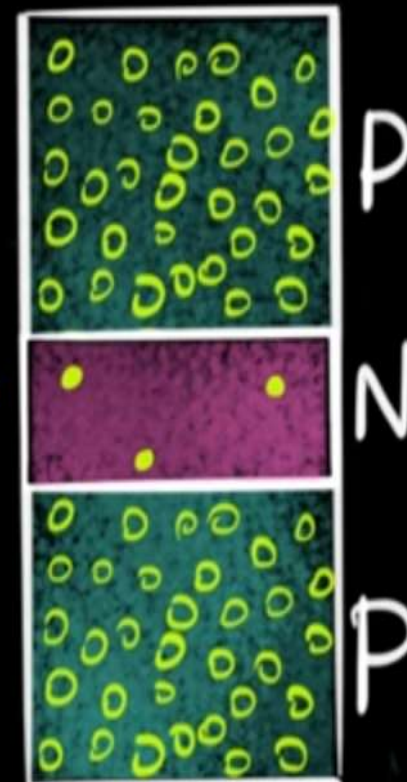


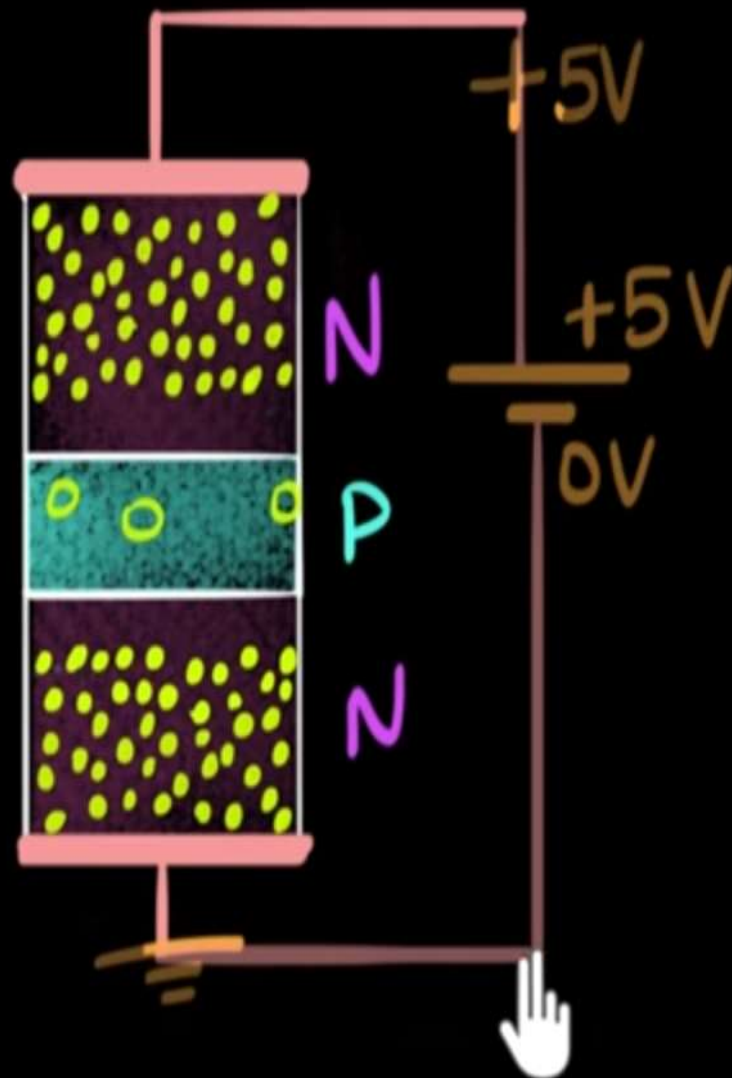

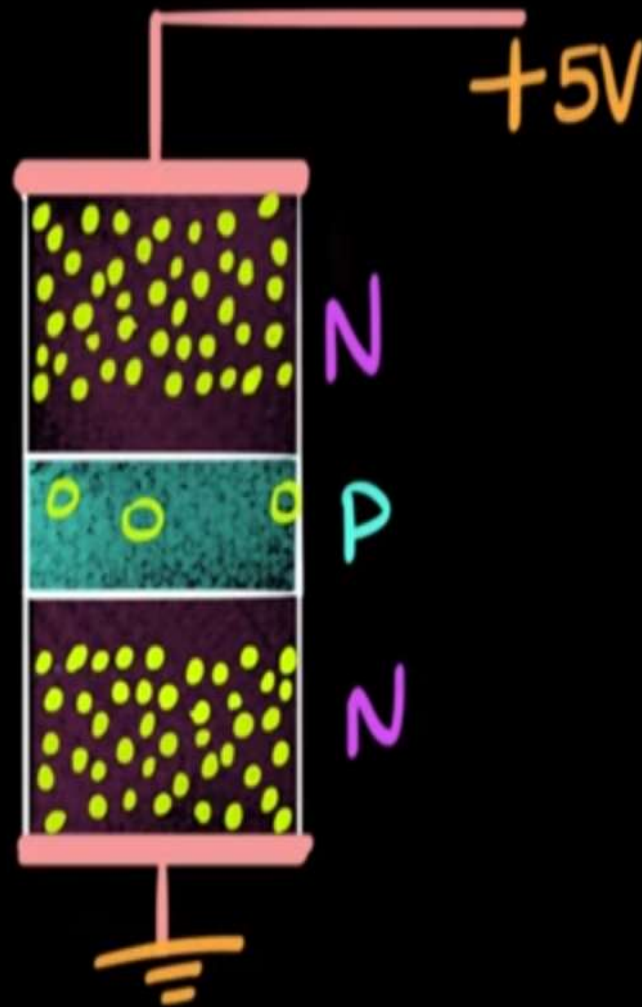

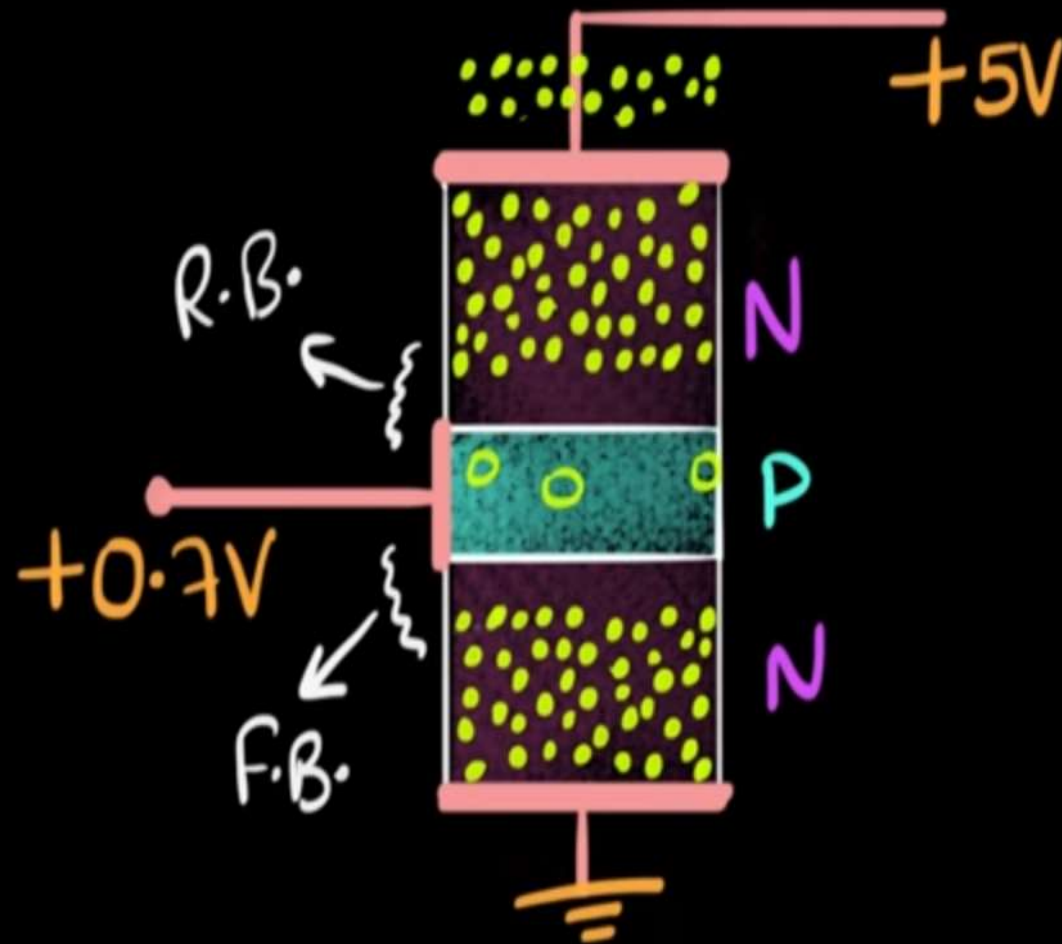

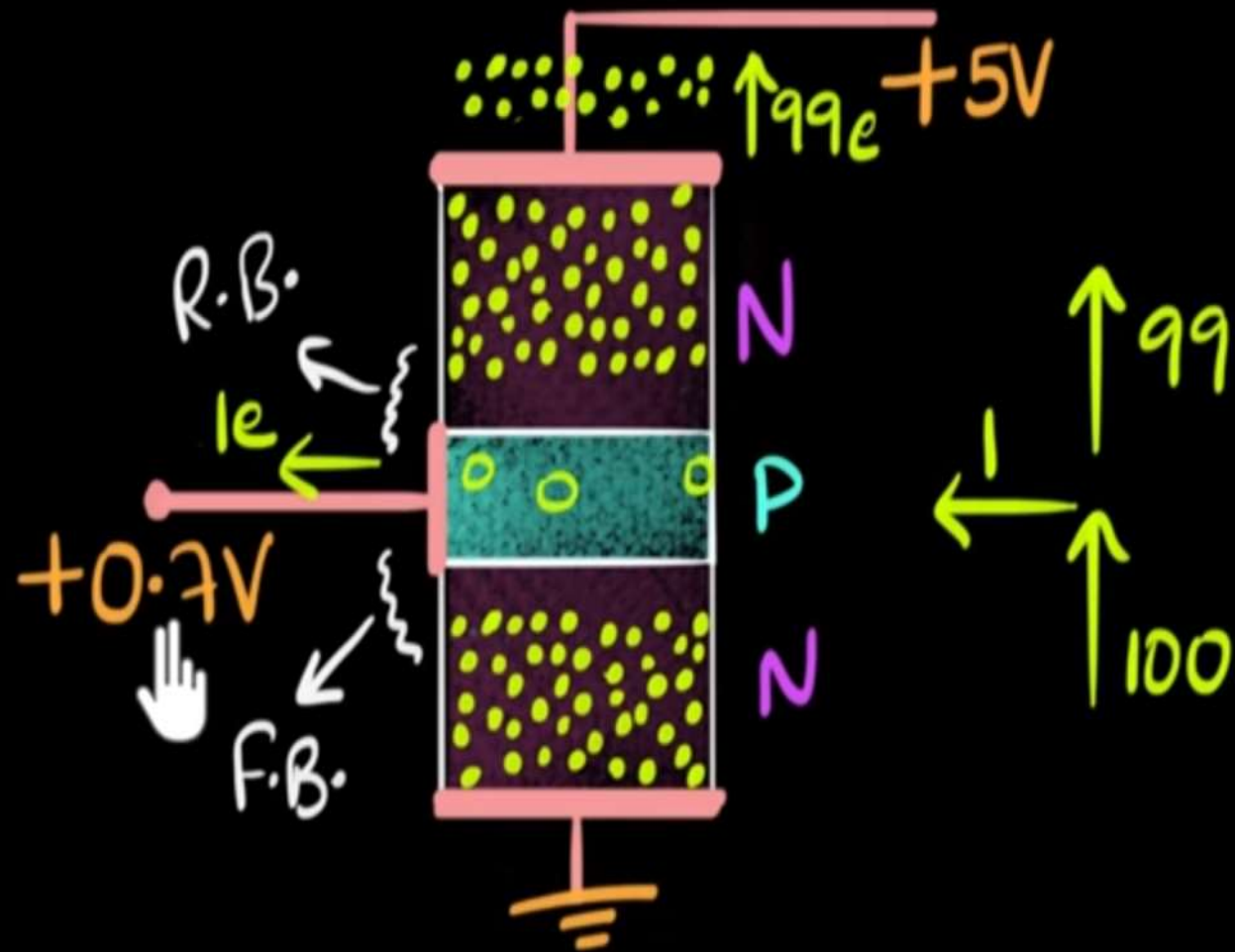


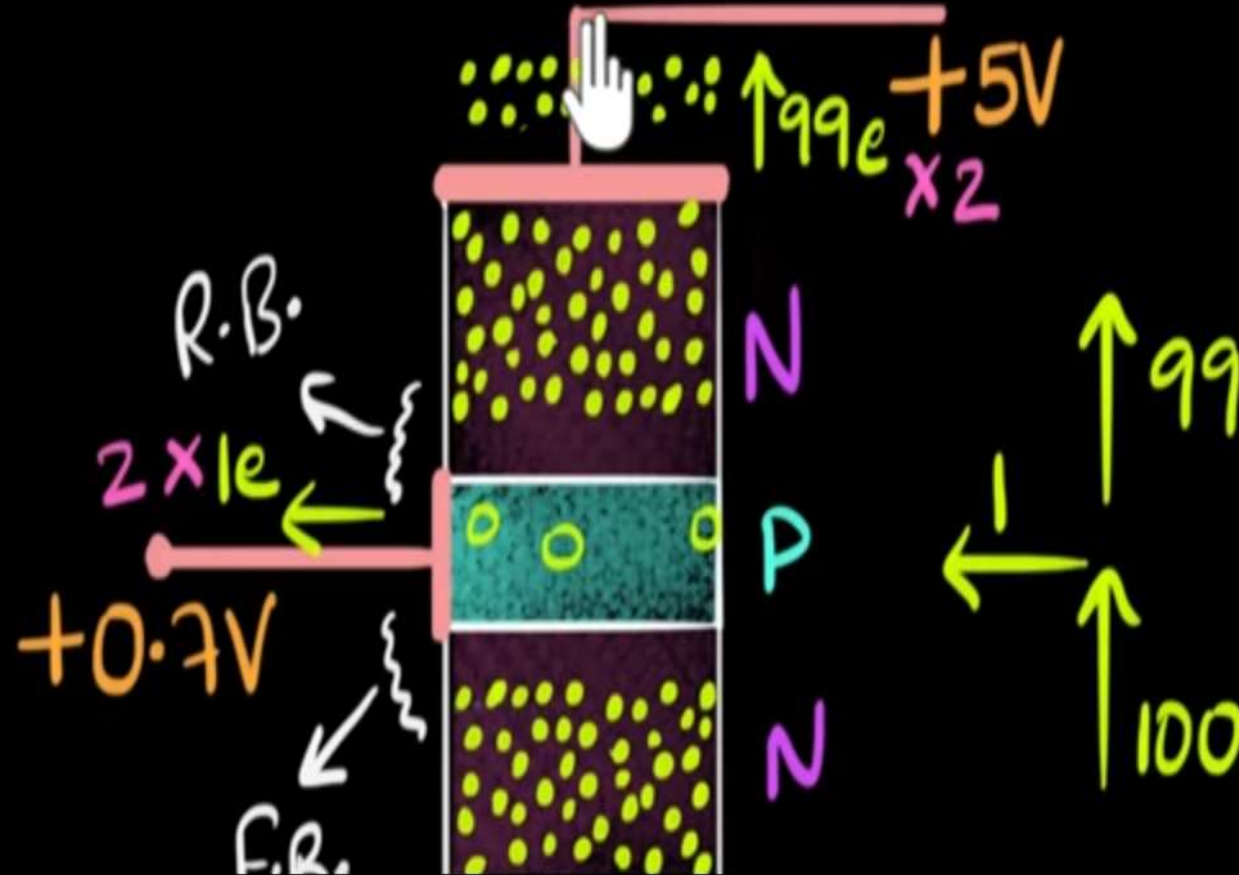



other words if the current in this wire
fluctuates the current in this wire



C-B \rightarrow Large V_R

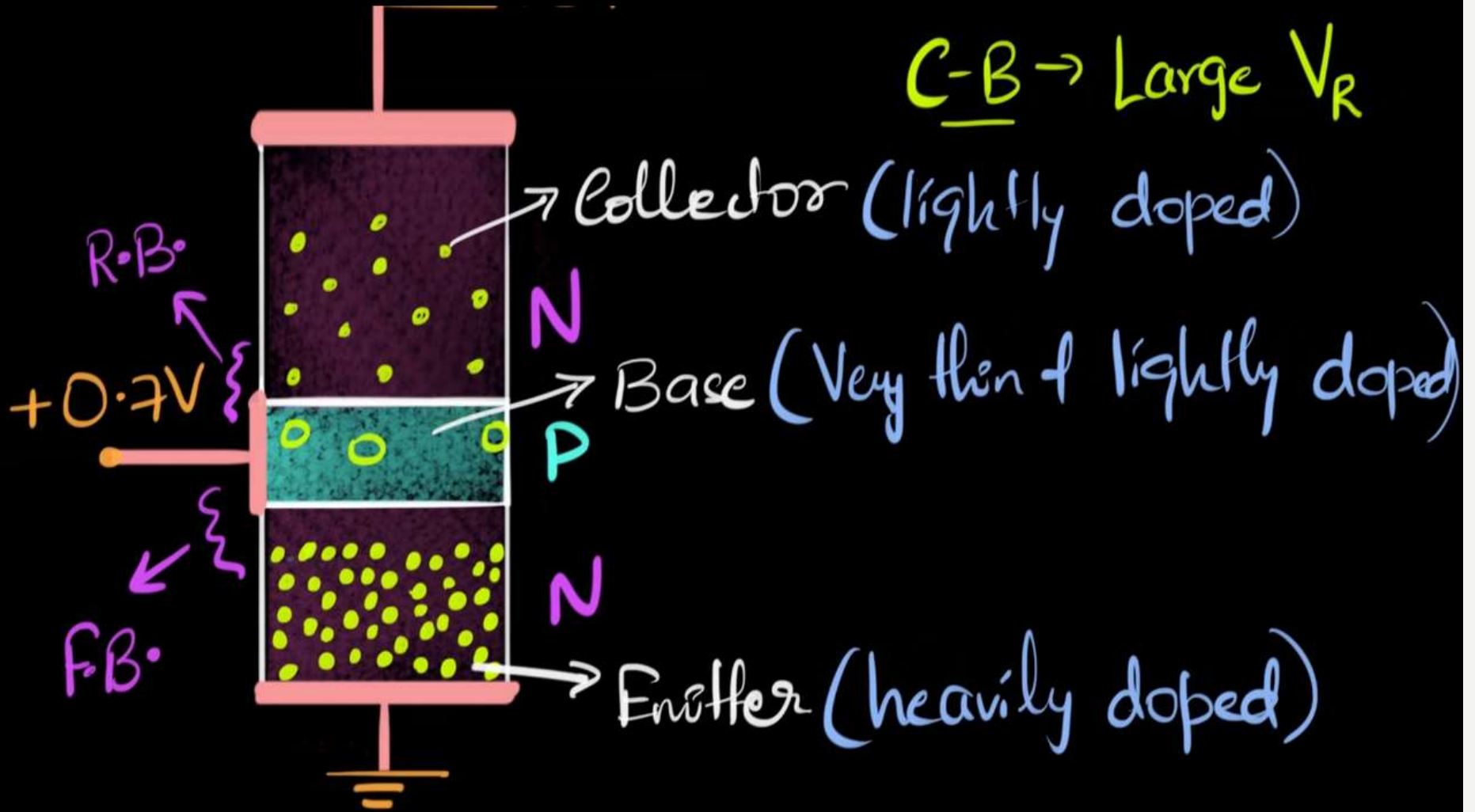

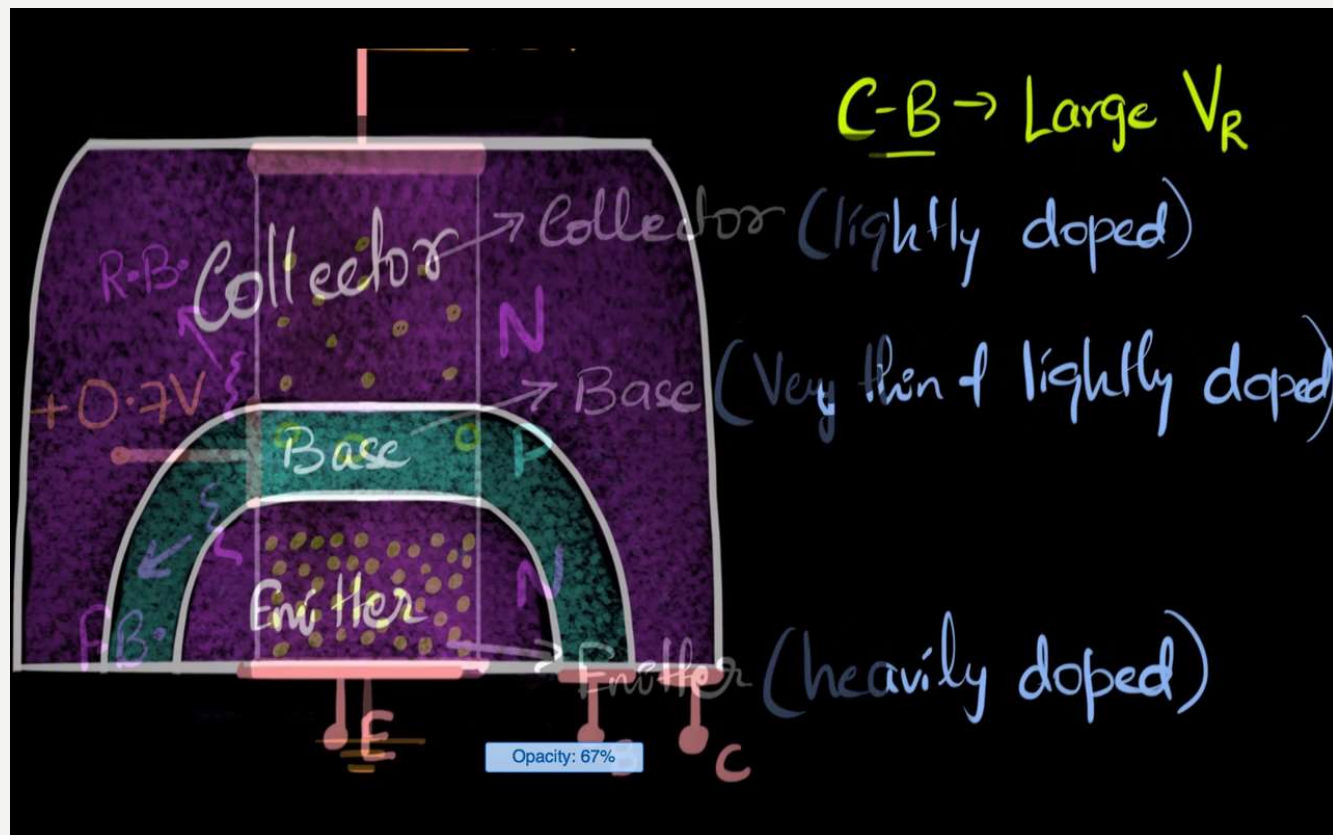

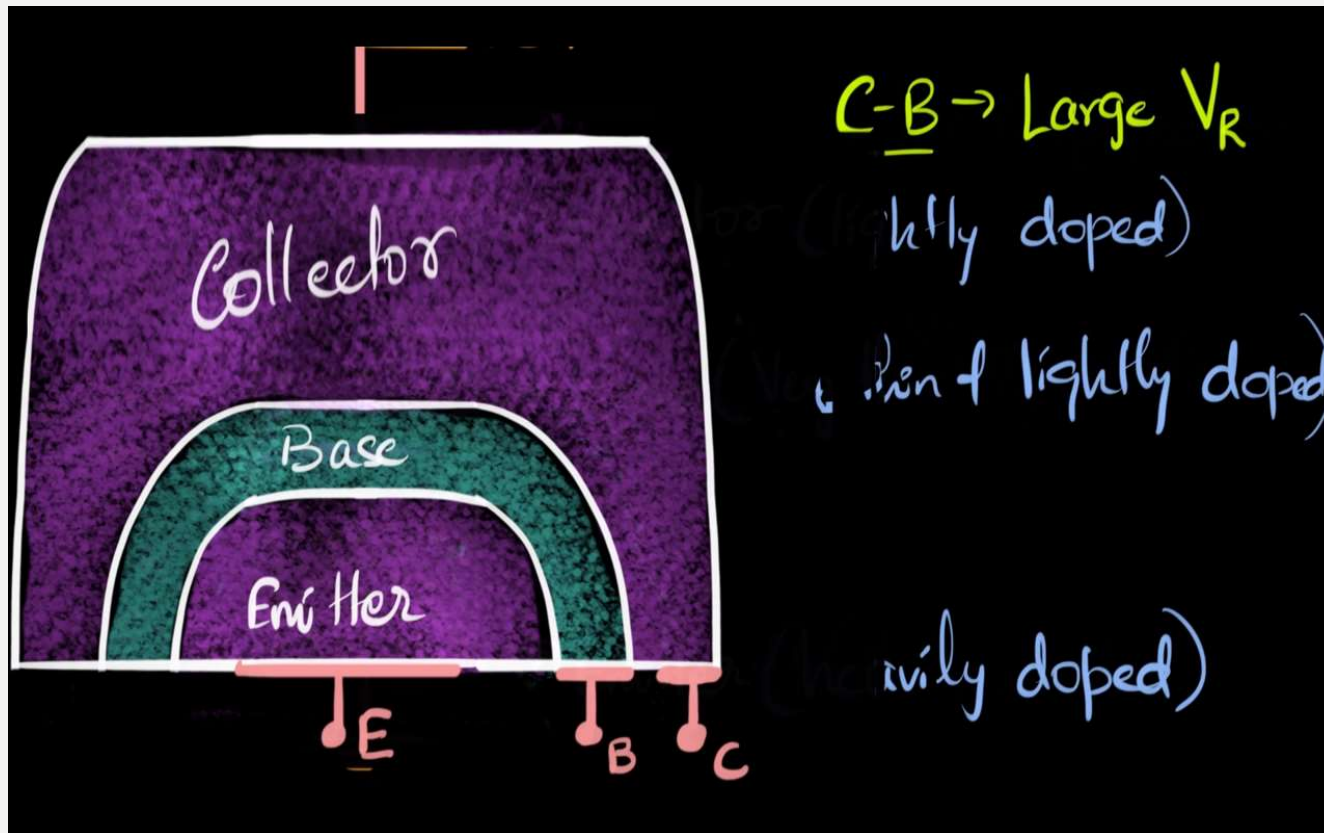

- Order of doping in ascending order

A E, B ,C

B C,B,E

C B,E,C

D B,C,E


- Order of Width in ascending order


A E, B ,C


B C,B,E

C B,E,C

D B,C,E

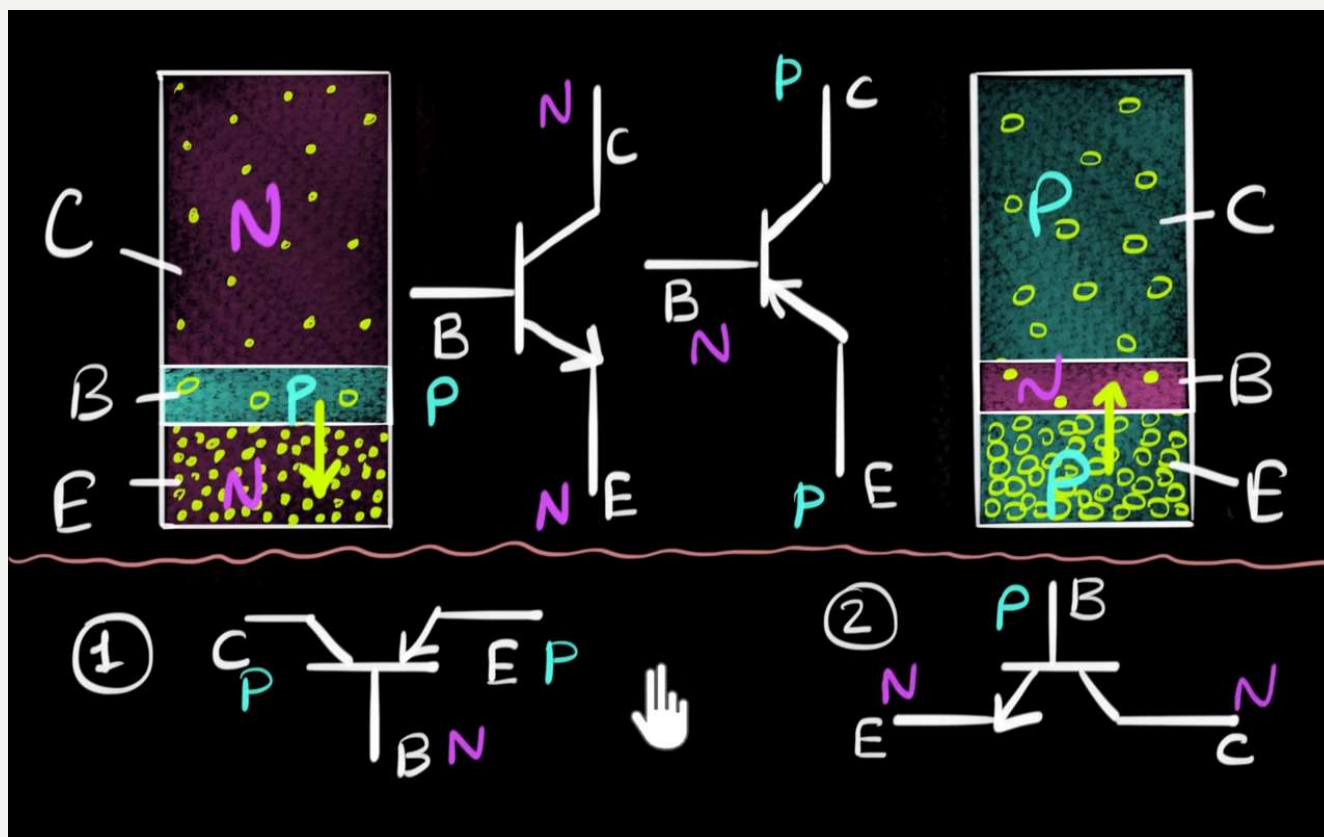


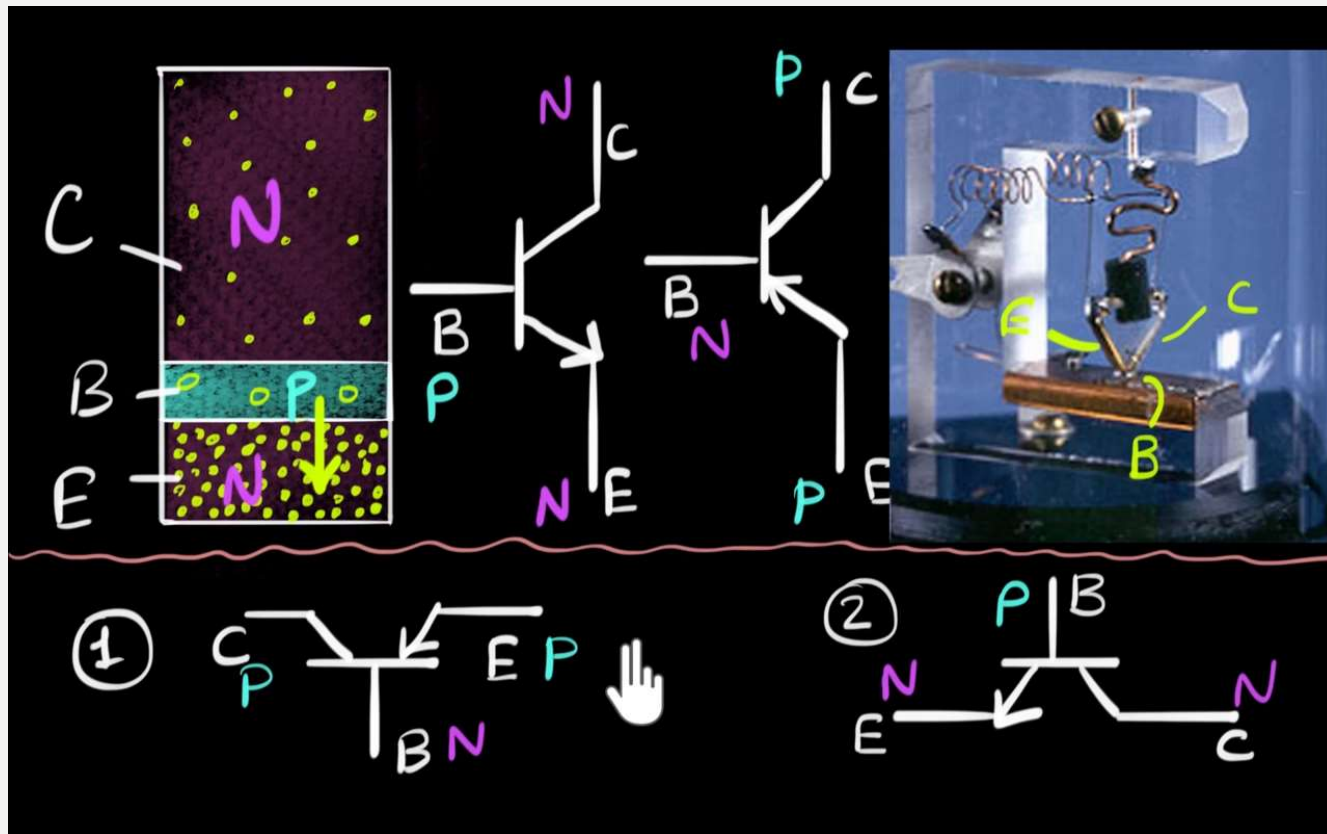

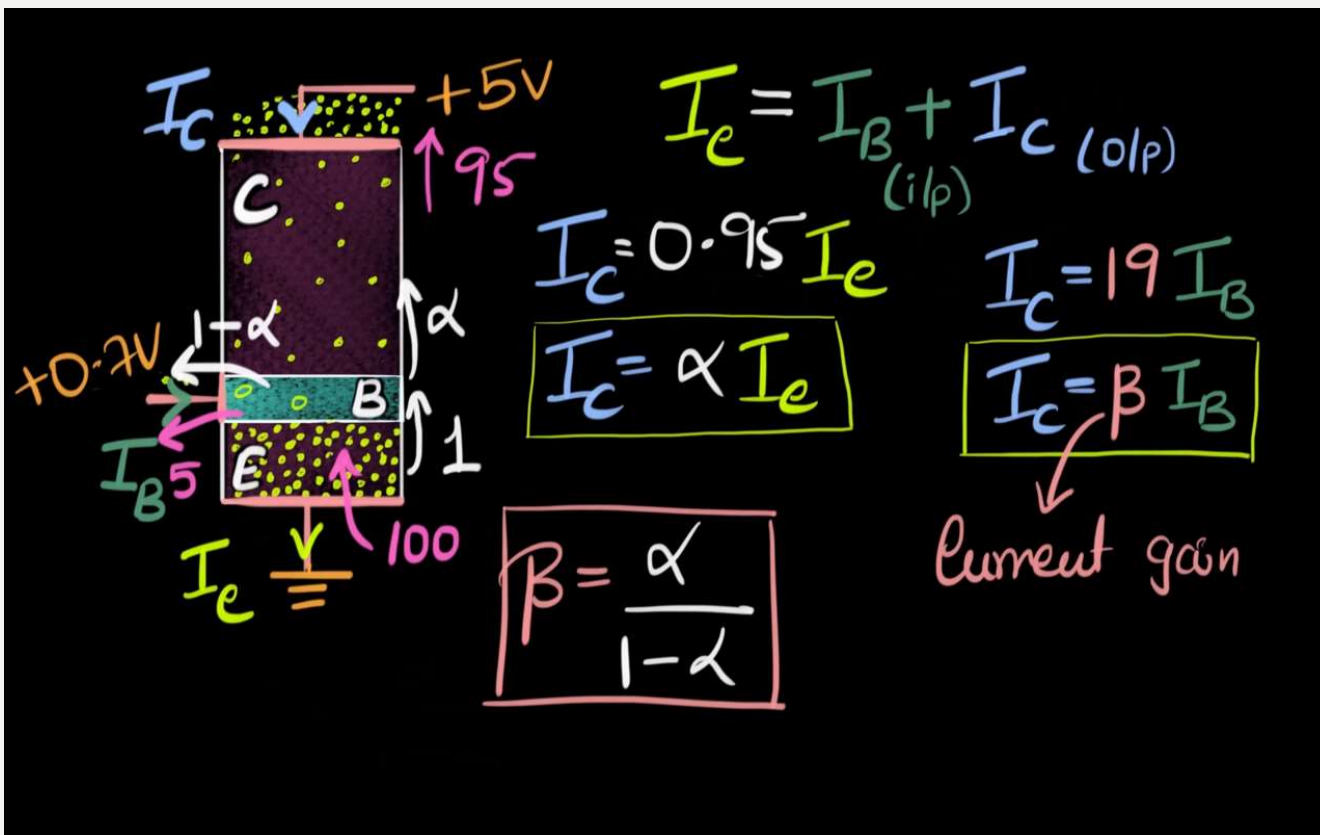

BJT

Physical St. :

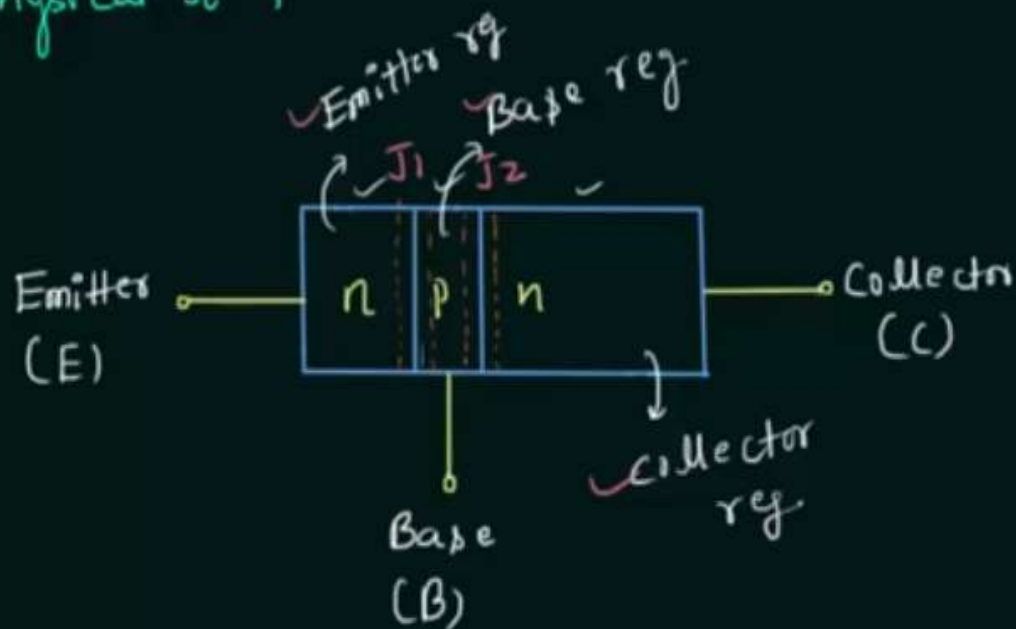


$J_1 \rightarrow$ emitter-base
 $J_2 \rightarrow$ coll. - base

width: $E > B$
 doping: $E > C > B$



Cross section view:

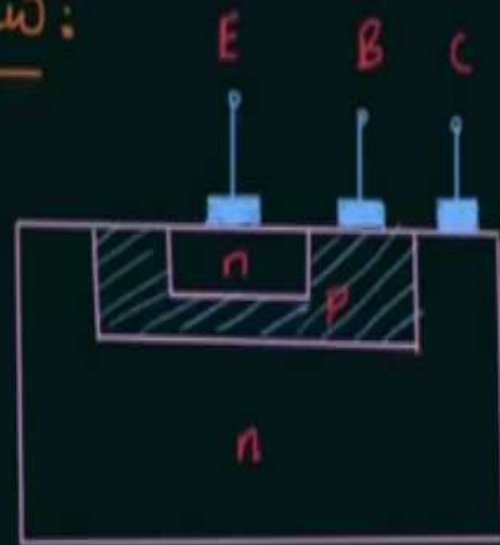

Symbol :



Bipolar Junc. Trans

i) e^-

ii) holes

$$\text{Transistor} = \text{Transfer} + \text{Resistor}$$


$J_1 \rightarrow \text{f-b.}$


$J_2 \rightarrow \text{r-b.}$


BJT

Regions of op :

J_1	J_2	Region of op.	
f.b.	r.b.	<u>Active</u>	→ Amplifier
f.b.	f.b.	Sat.	→ 'ON'
r.b.	r.b.	cutoff	→ Off
r.b.	f.b.	Inverted	→ rarely used

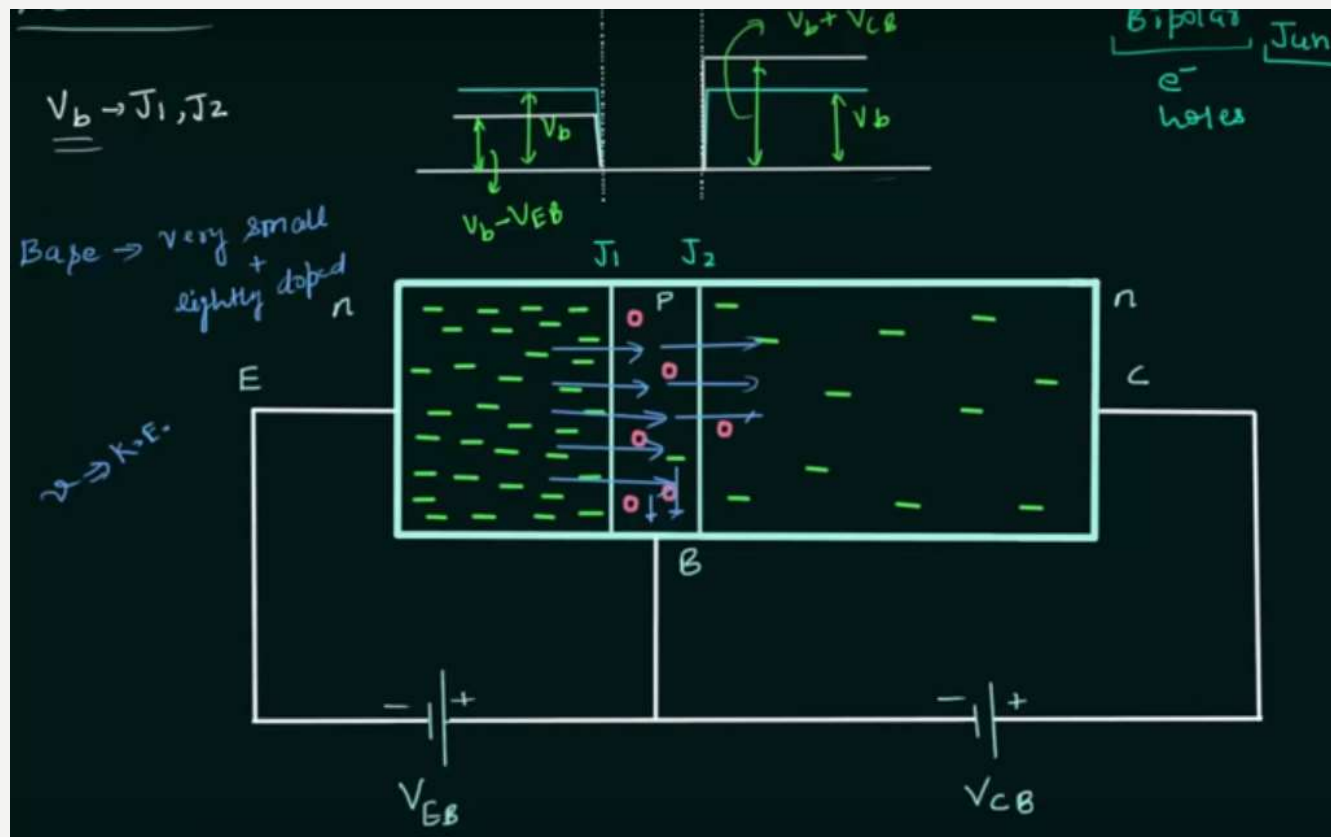

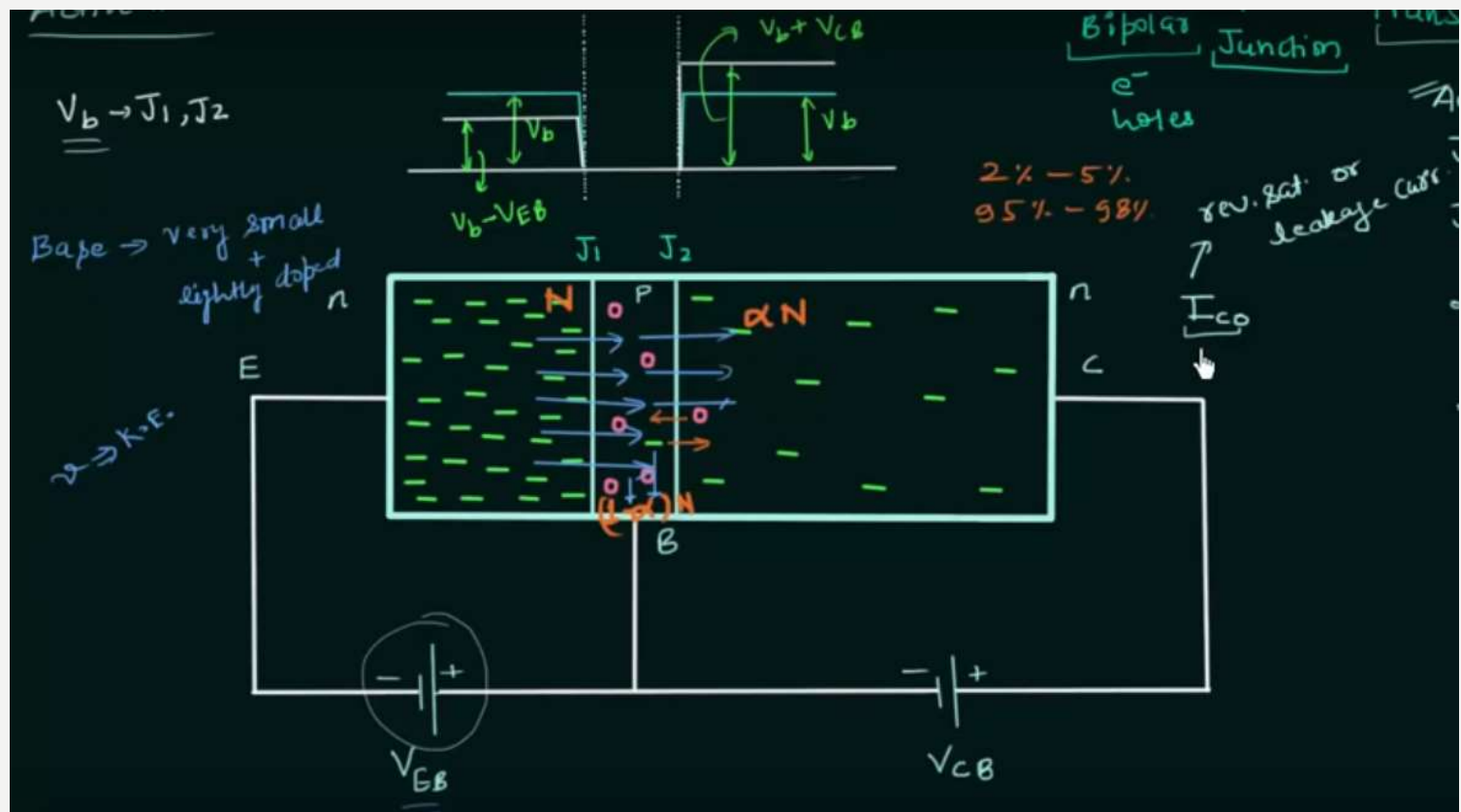

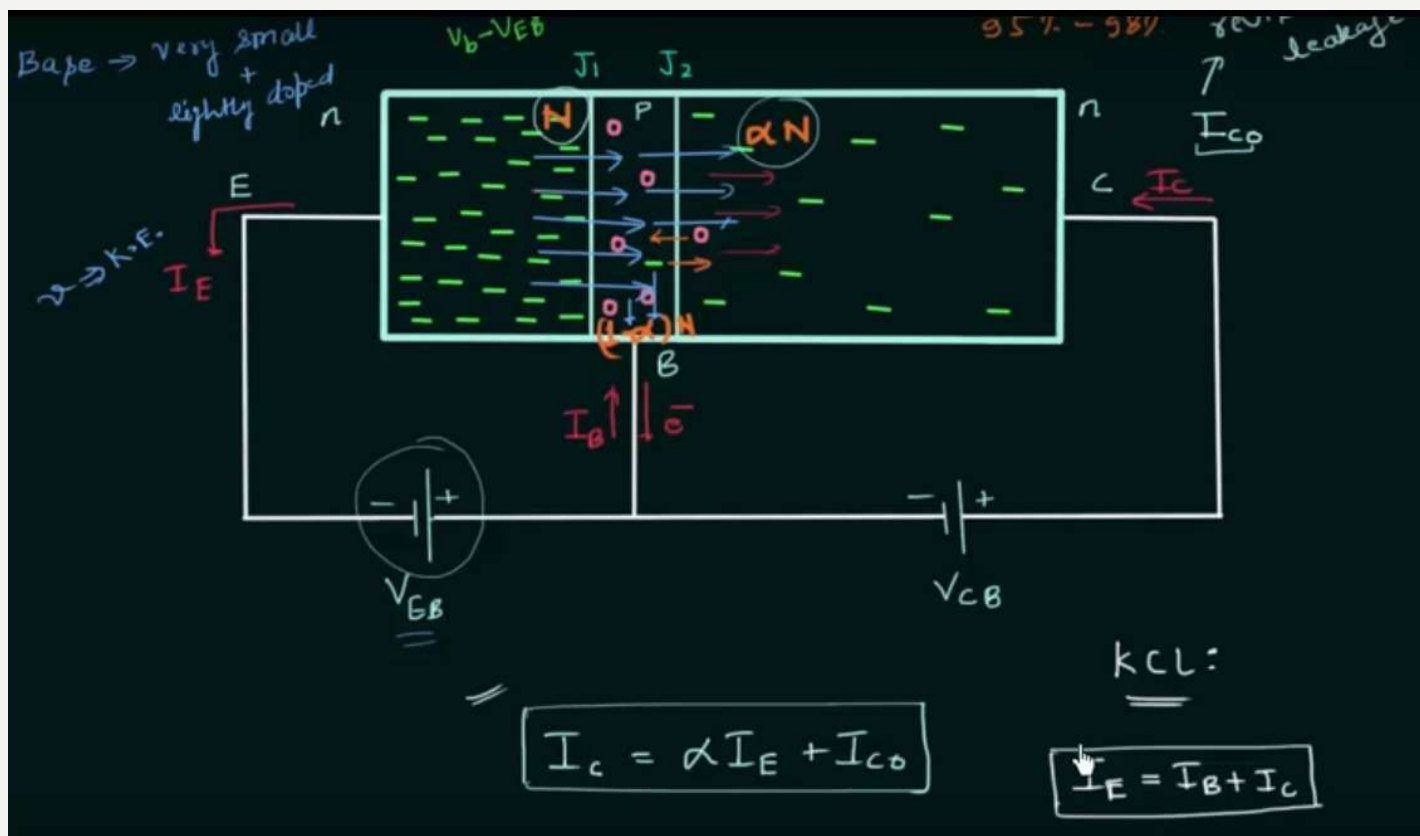



TRANSISTOR BIASING

① ER

[ACTIVE]


$V_{BE} = 0.5V / 0.7V$ for Ge/Si

$V_{CB} = 3V - 20V$ or $> 20V$

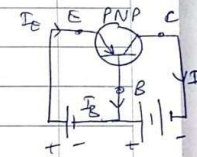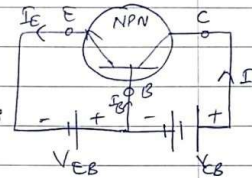


② EE

[SATURATION]

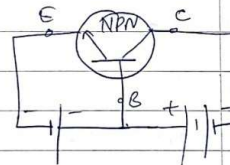


③ RE

[INVERTED]

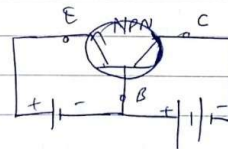

④ RR


[CUT-OFF]

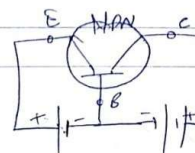

Notes

- I_{CBO} is the collector **current** with collector junction reverse biased and base open-circuited.
- I_{CEO} is the collector **current** with collector junction reverse biased and emitter open-circuited.

TRANSISTOR CURRENT COMPONENTS

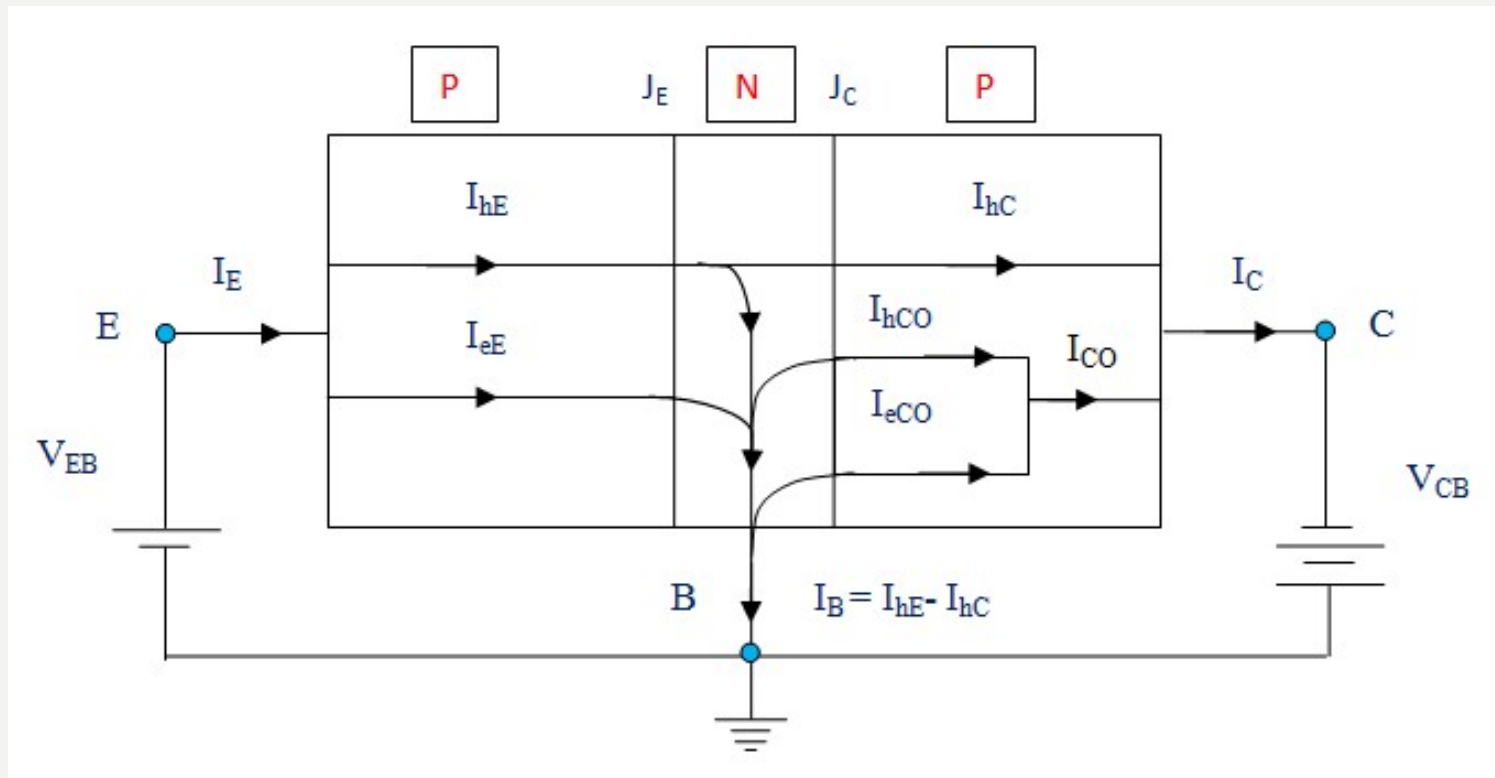

We know that, the current arrives the transistor through the emitter and this current is called emitter current (I_E). This current consists of two constituents – **Hole current** (I_{hE}) and **Electron current** (I_{eE}). I_{eE} is due to passage of electrons from base to emitter and I_{hE} is due to passage of holes from emitter to base.

$$I_E = I_{hE} + I_{eE}$$

Normally, the emitter is heavily doped compared to base in industrial transistor. So, the Electron current is negligible compared to Hole current. Thus we can conclude that, the whole emitter current in this transistor is due to the passage of holes from the emitter to the base.

Some of the holes which are crossing the junction J_E (emitter junction) combines with the electrons present in the base (N-type). Thus, every holes crossing J_E will not arrive at J_C . The remaining holes will reach the collector junction which produces the hole current component, I_{hC} . There will be bulk recombination in the base and the current leaving the base will be

$$I_B = I_{hE} - I_{hC}$$

The electrons in the base which are lost by the recombination with holes (injected into the base across J_E) are refilled by the electrons that enter into the base region. The holes which are arriving at the collector junction (J_C) will cross the junction and it will go into the collector region.

When the emitter circuit is open circuited, then $I_E = 0$ and $I_{hC} = 0$. In this condition, the base and collector will perform as reverse biased diode. Here, the collector current, I_C will be same as reverse saturation current (I_{CO} or I_{CBO}).

I_{CO} is in fact a small reverse current which passes through the **PN junction diode**. This is due to thermally generated minority carriers which are pushed by barrier potential. This reverse current increase; if the junction is reverse biased and it will have the same direction as the collector current. This current attains a saturation value (I_0) at moderate reverse biased voltage.

When the emitter junction is at forward biased (in active operation region), then the collector current will become

$$I_C = \alpha I_E + I_{CO}$$


The α is the large signal current gain which is a fraction of the emitter current which comprises of I_{hC} .

When the emitter is at closed condition, then $I_E \neq 0$ and collector current will be

$$I_C = I_{CO} + I_{hC}$$



In a PNP transistor, the reverse saturation current (I_{CBO}) will comprises of the current due to the holes passing through the collector junction from the base to collector region (I_{hCO}) and the current due to the electrons which are passing through the collector junction in the opposite direction (I_{eCO}).
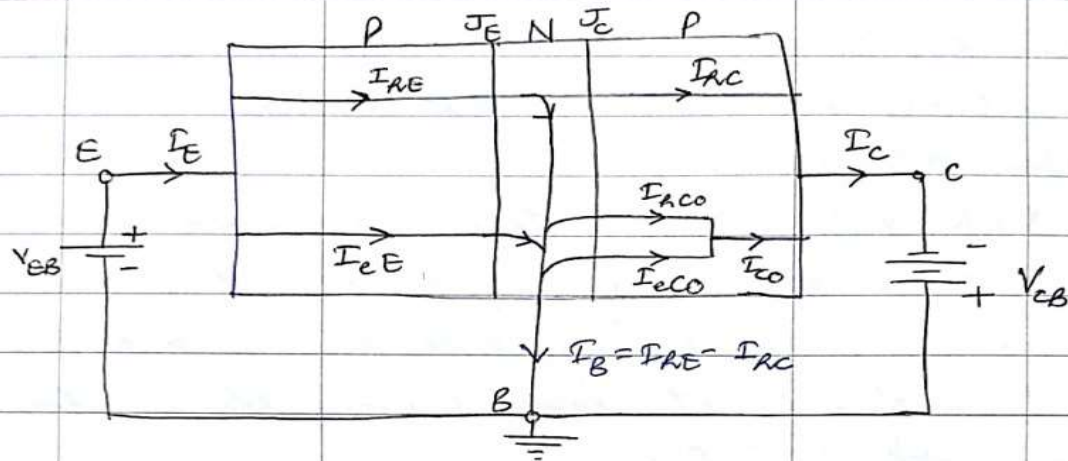
$$\text{Therefore, } I_{CO} = I_{hCO} + I_{eCO}$$





- Emitter effy. $\gamma = \frac{I_{BE}}{I_E}$
- Transport factor $\beta = \frac{I_{AC}}{I_{BE}}$
- Large signal current gain $\alpha = \frac{I_C - I_{CO}}{I_E} = \frac{I_{AC}}{I_E} = \frac{I_{AC}}{I_{BE}} \times \frac{I_{BE}}{I_E}$
- $0.95 \leq \alpha \leq 0.99$ $\alpha < 1$ $[\alpha = \beta \times \gamma]$
- DC current gain $\alpha_{dc} = \frac{I_C}{I_E} = \text{Current Amplification Factor}$
- Small signal current gain $\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$
- Current gain factor $= \frac{\Delta I_C}{\Delta I_B} = \text{Transport factor}$


CUT-OFF, ACTIVE AND SATURATION REGIONS

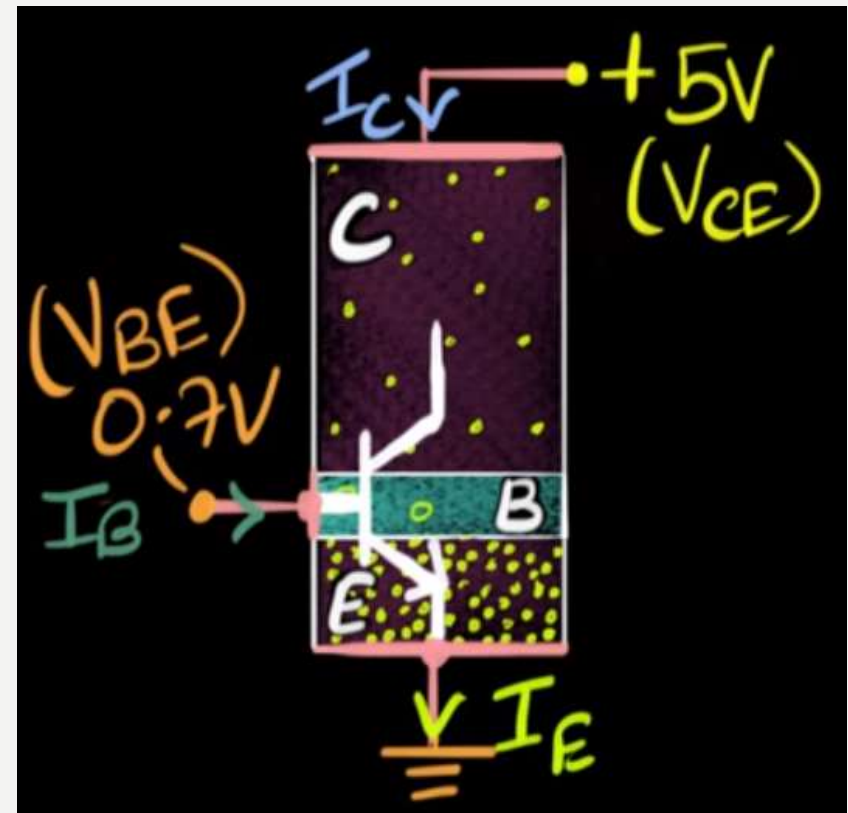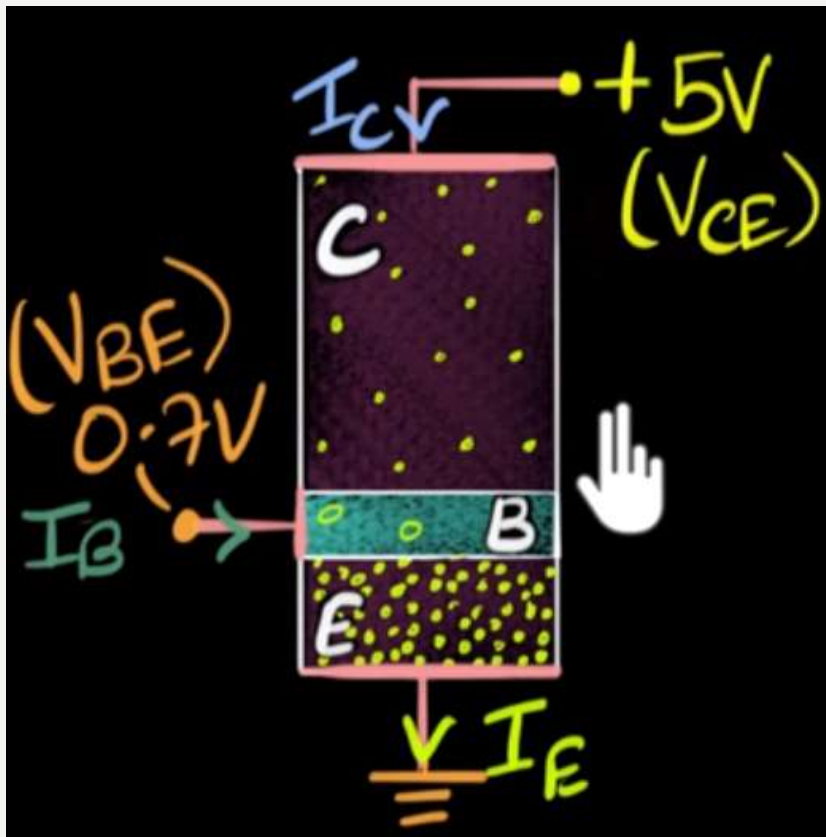

CUT-OFF AND ACTIVE

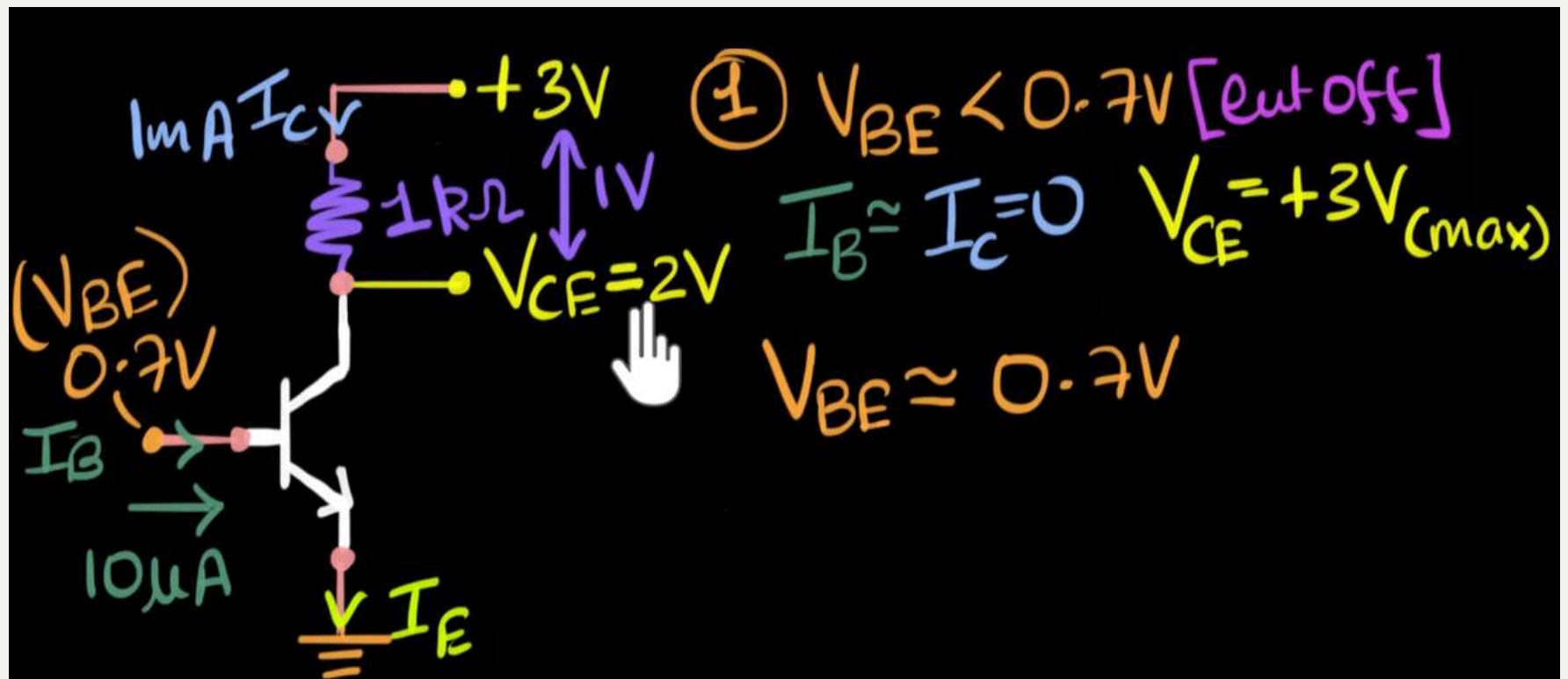

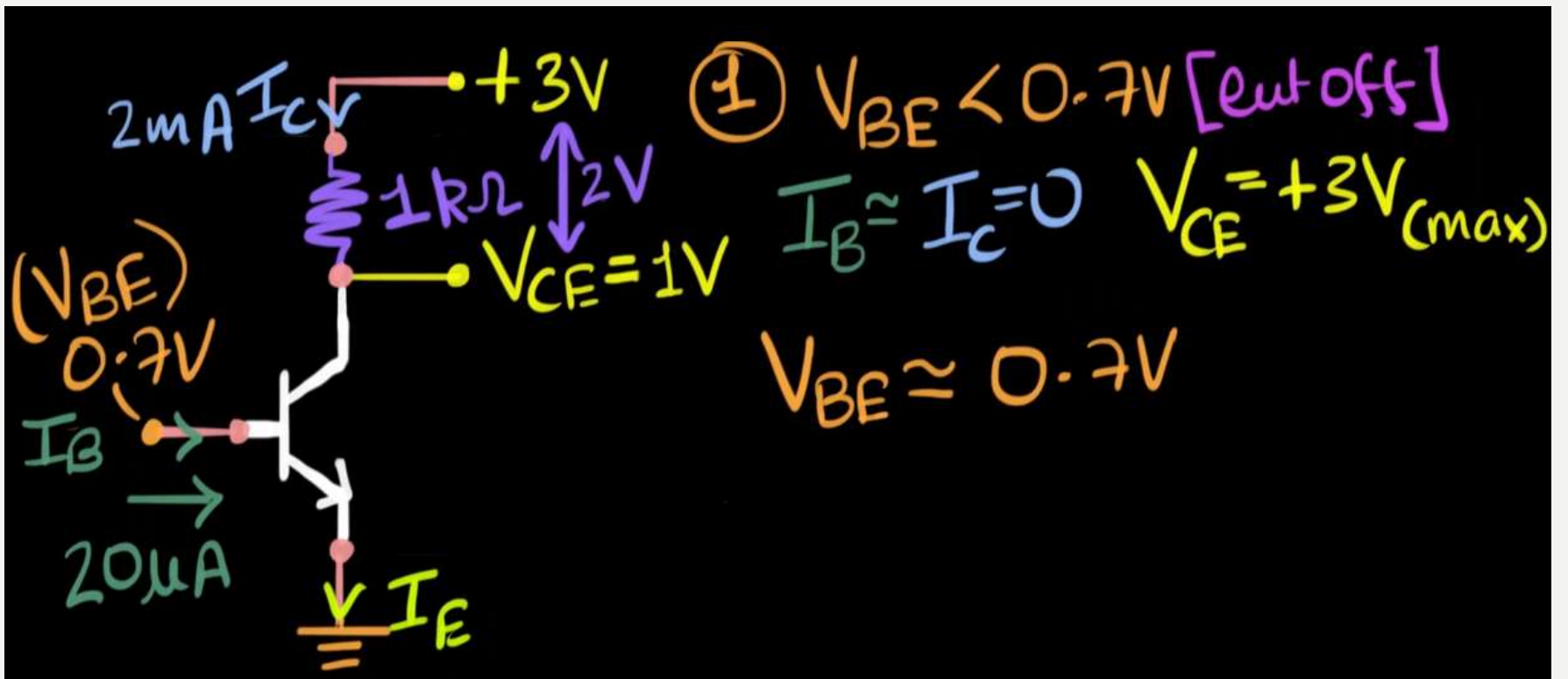

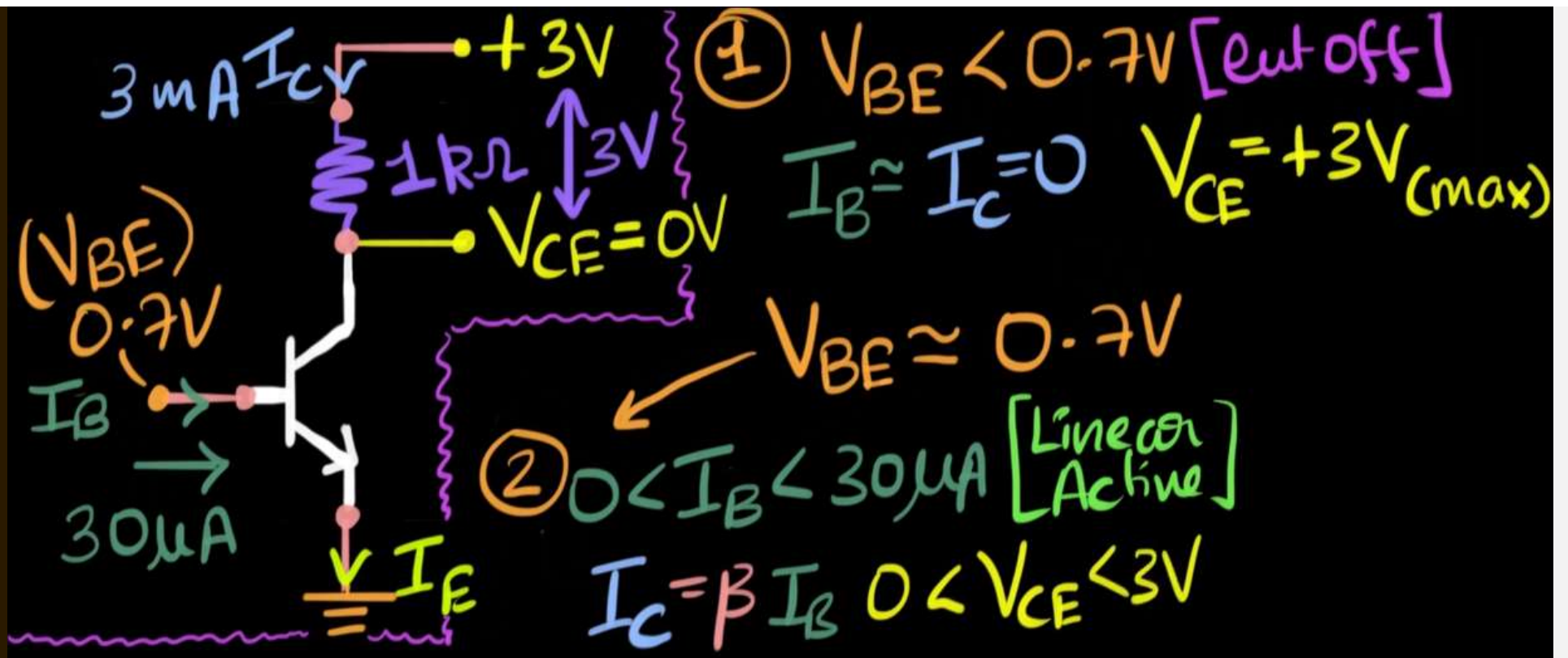

IF CURRENT IS INCREASED BEYOND 30 MA, THE OUTPUT CURRENT REMAINS SAME BECAUSE IF THE CURRENT BECOMES 4MA, THE DROP AROUND THE RESISTOR BECOMES 4V BUT THE SUPPLY VOLTAGE IS ONLY 3 V AND SO IT CAN'T HAS A DROP MORE THAN 3 V. THUS EVEN IF THE INPUT CURRENT IS INCREASED, THE OUTPUT CURRENT STAYS AT 3MA ONLY.

③ $I_B > 30\mu A$ [Saturation]
 $I_C = 3mA_{(max)}$ $V_{CE} = 0_{(min)}$

- The collector of a transistor is doped
 - a) heavily
 - b) moderately
 - c) lightly
 - d) none of the above

- In a transistor as an amplifier, the reverse saturation current
 - a) Doubles for every $^{\circ}\text{C}$ rise in temperature
 - b) Doubles for every 10°C rise in temperature
 - c) Decreases linearly with temperature
 - d) Increase linearly with temperature

- In a transistor if $\beta = 100$ and collector current is 10 mA, then I_E is
- a) 100 mA
- b) 100.1 mA
- c) 110 mA
- d) none of the above

• If the value of α is 0.9, then value of β is

a) 9


b) 0.9

c) 900


d) 90

USE OF CUT-OFF AND SATURATION REGIONS?

TRANSISTOR AS A SWITCH

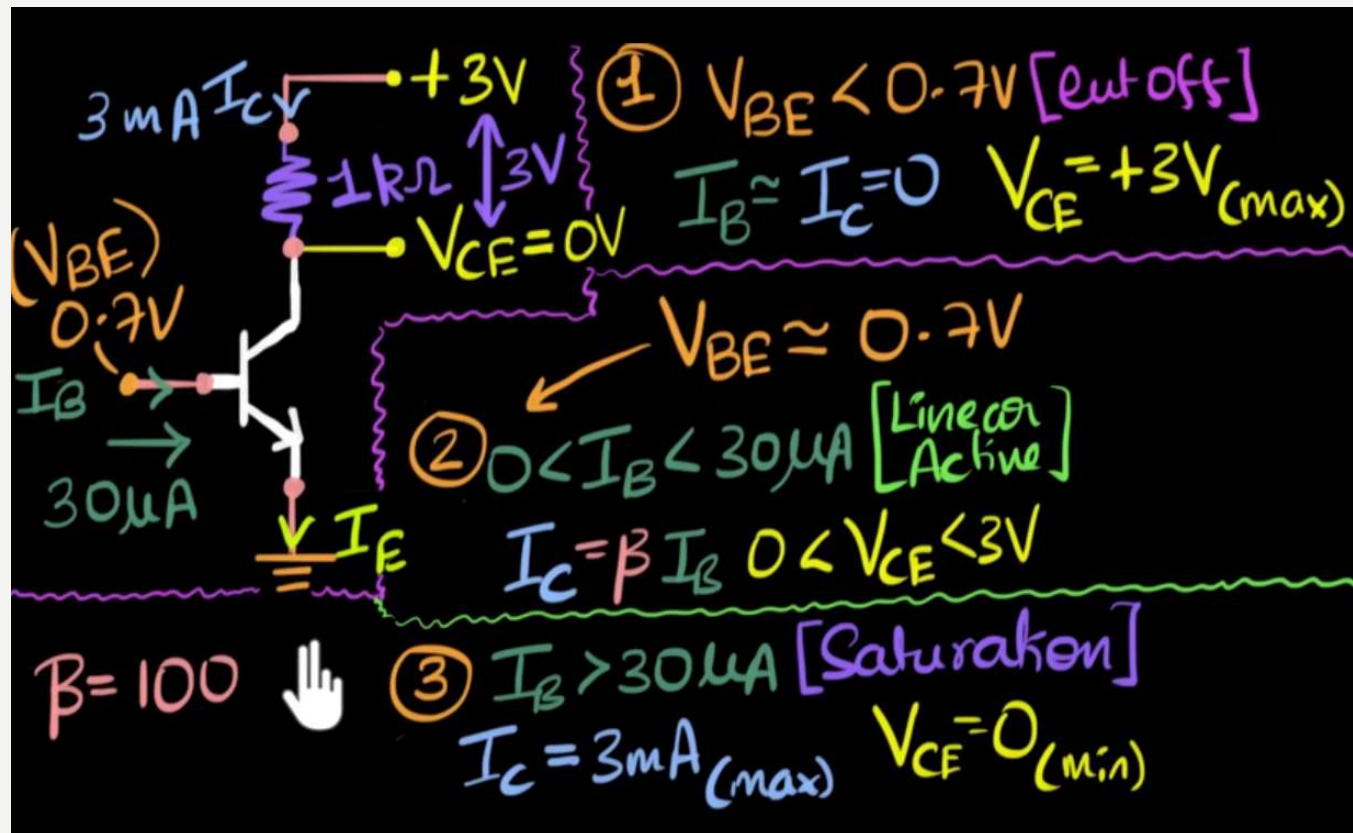

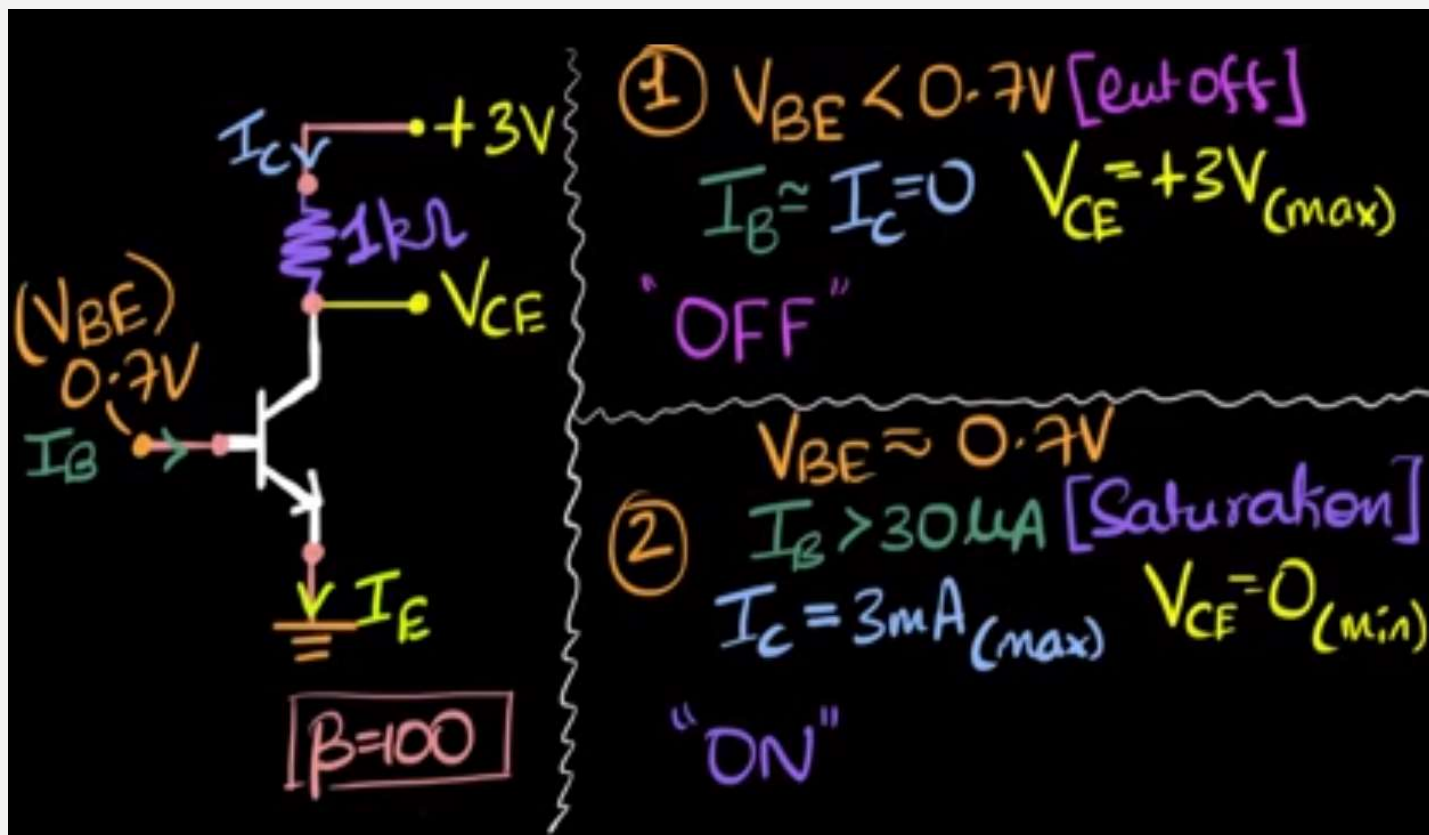
- When input current is within a particular range, the transistor acts as an amplifier.
- But outside that range, transistor exhibits other characteristics.
- **Cut-off**- O/P voltage is very high, I/P current is very low.
- **Saturation**- I/P current is very high but the O/P voltage is zero. When input current is increased beyond the limit, the output current does not increase at all further.




CUT-OFF




SATURATION

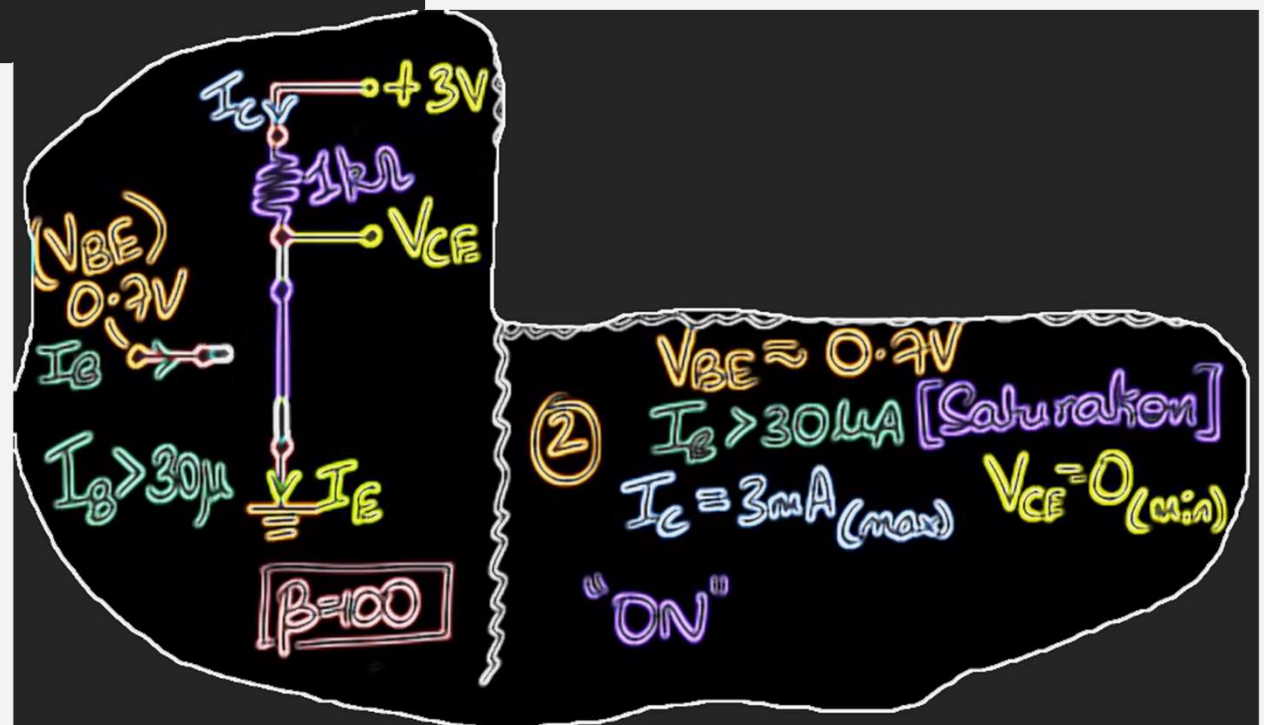

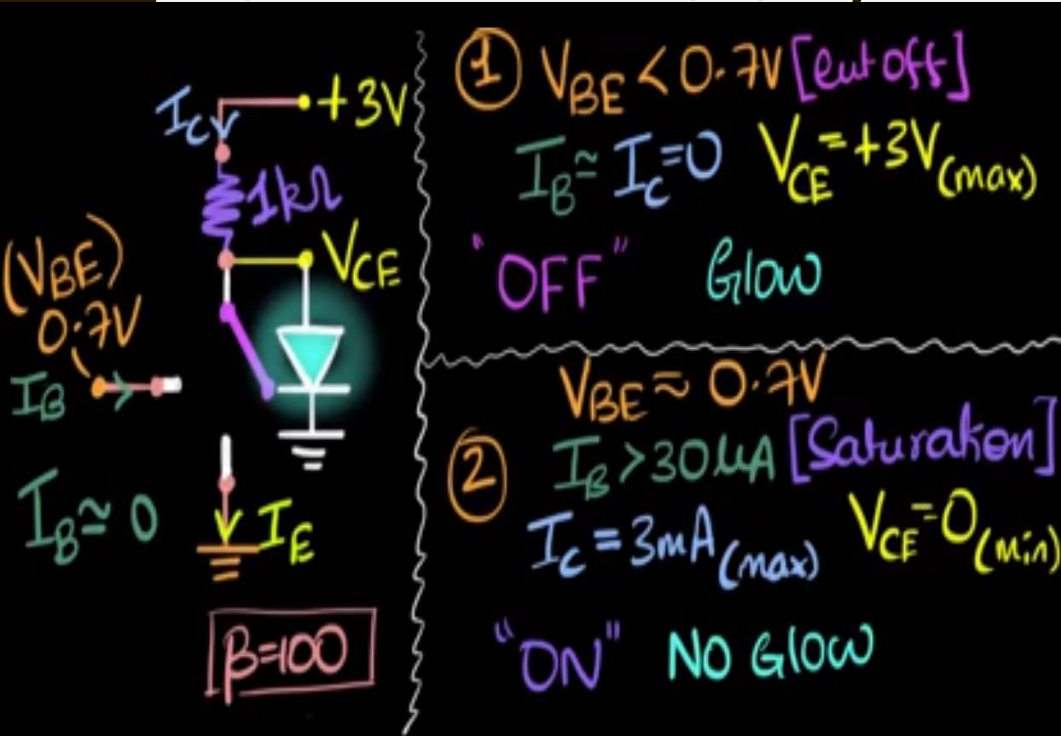CUT-OFF (TRANSISTOR IS OFF BUT THE LED IS ON)





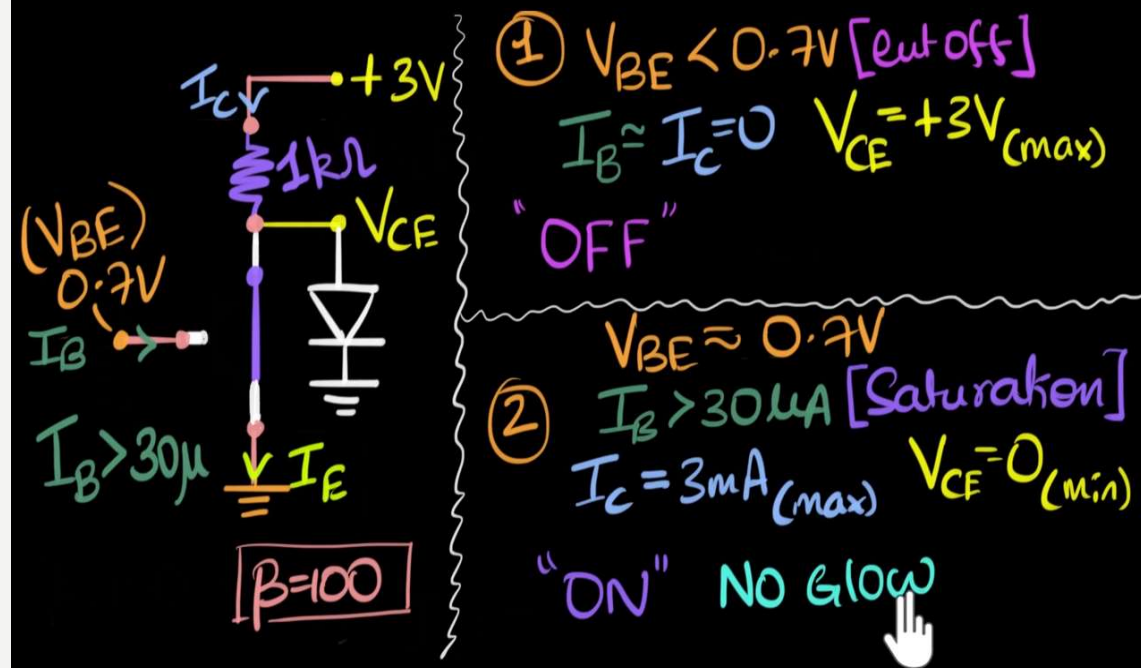
SATURATION (TRANSISTOR IS ON BUT THE LED IS OFF)




WHY NOT USE A MECHANICAL SWITCH INSTEAD?

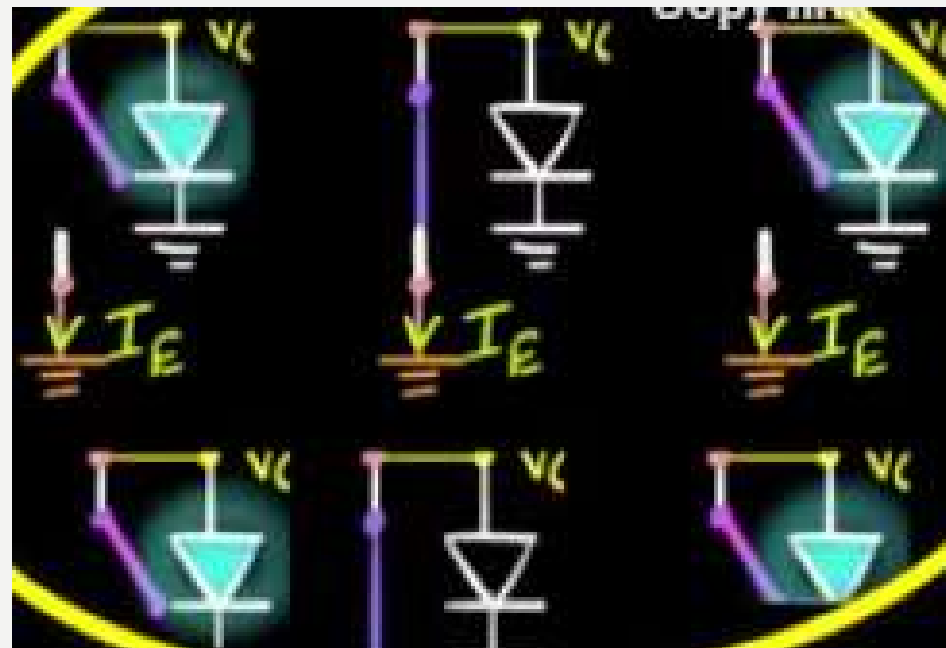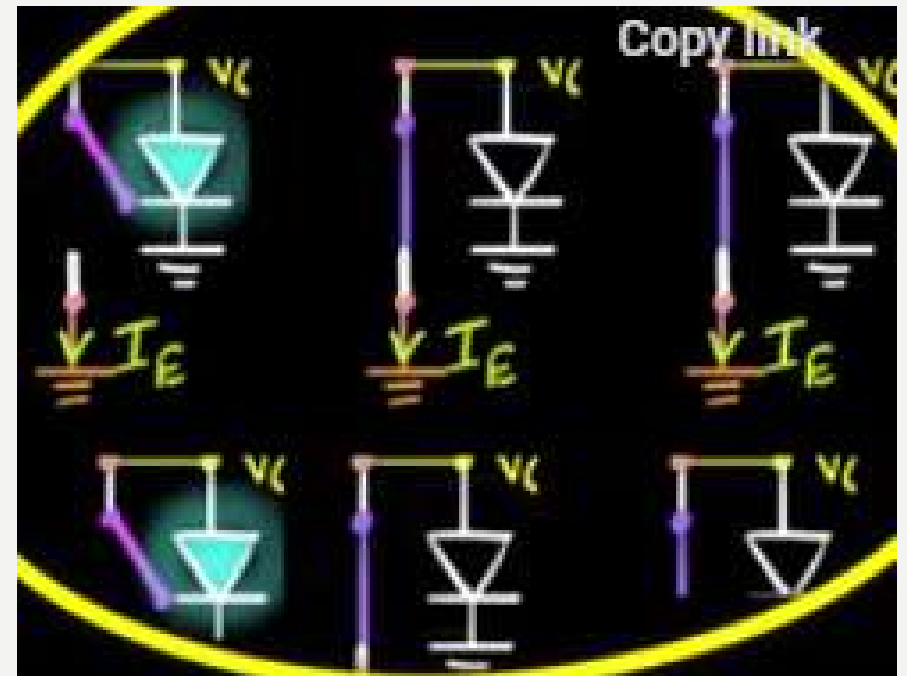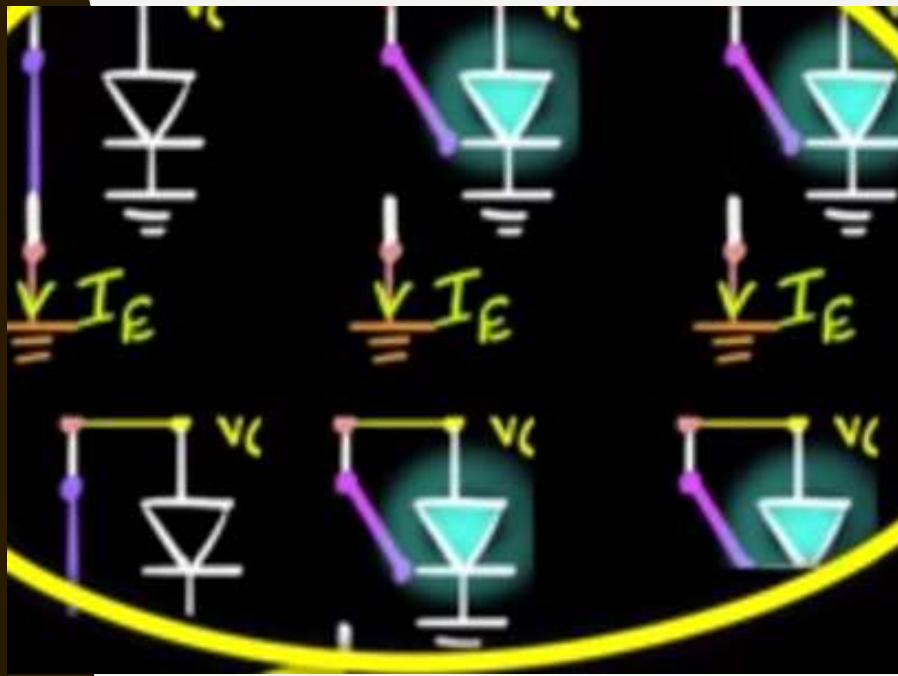- 1) It has no moving parts (With moving parts, there is a limit to how fast it is turned on and off), so its switching speed is incredibly high.
[EXTREMELY FAST]
- 2) Power consumption is very low as it consumes very less electricity, thus it is extremely efficient. [EXTREMELY LOW POWER]
- 3) Today's transistors can be made extremely tiny, thus a lot of switches can be placed in a very small space. [EXTREMELY TINY]

So, by combining these switches together in a great number, we can make operators, we can do addition, subtraction and all the mathematical computing and thus make a computer (because inside it there are lot many switches)





TRANSISTOR AS AN AMPLIFIER

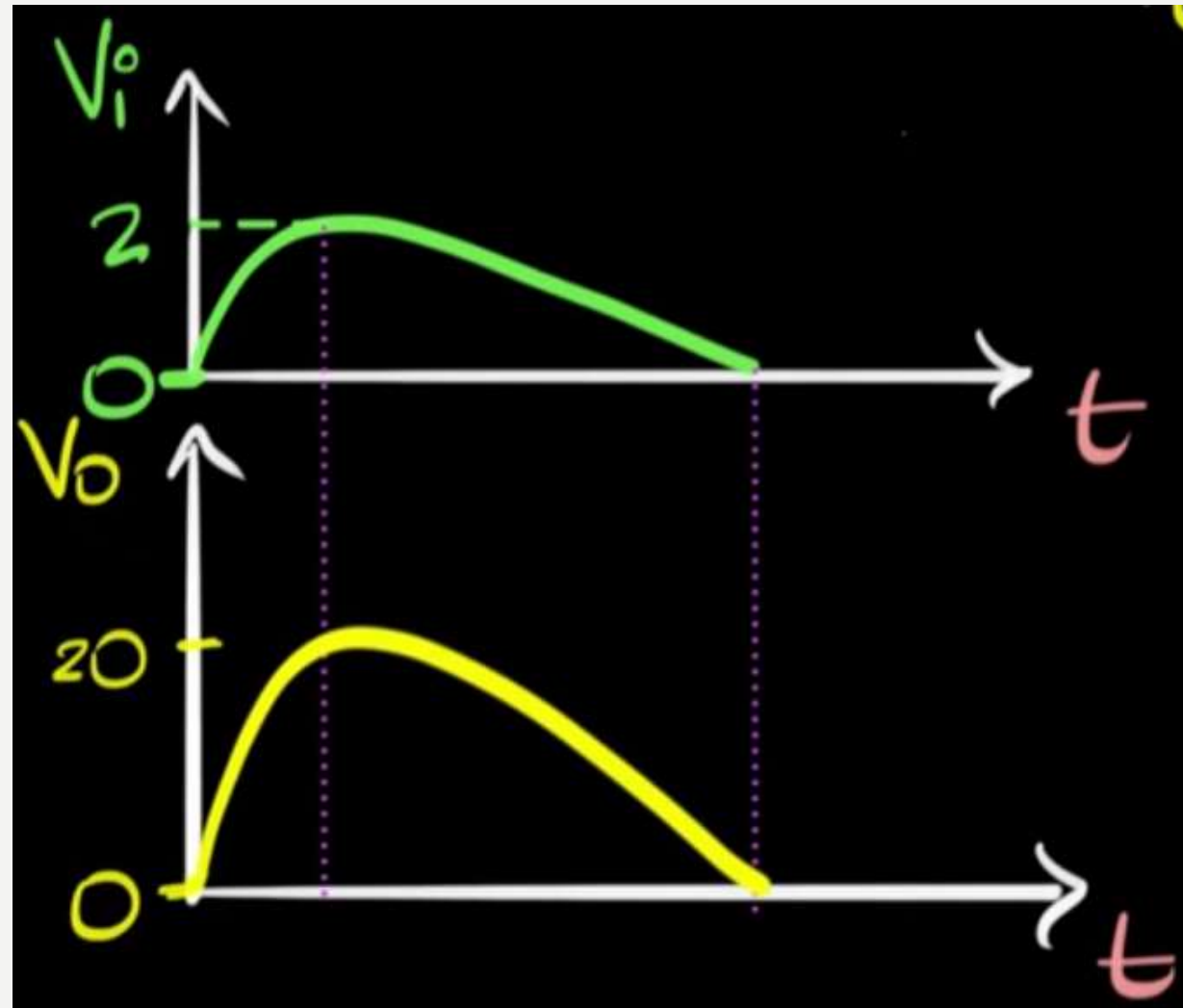

$$V_o = 10 V_i$$

$$\Delta V_o = 10 \Delta V_i$$

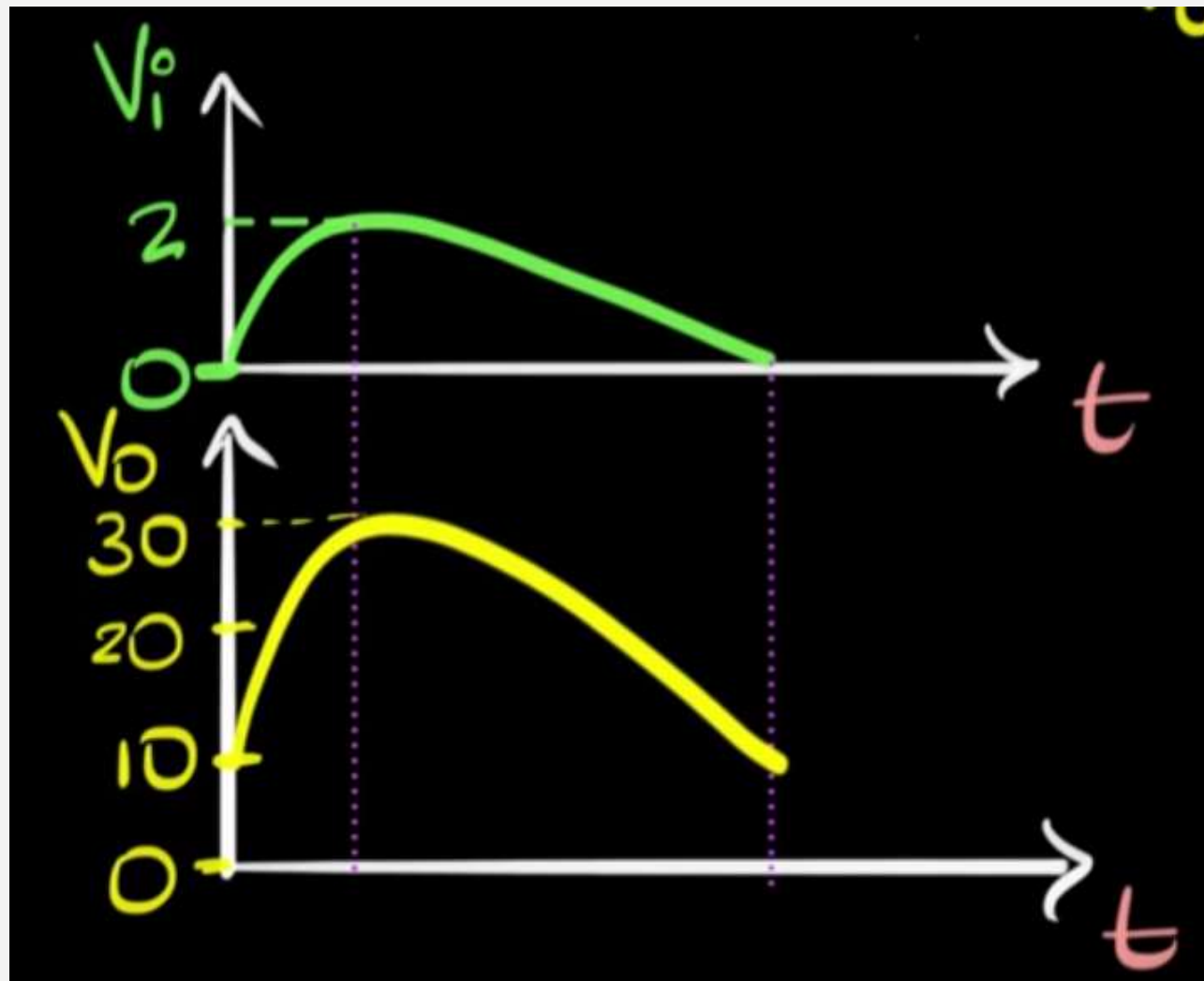

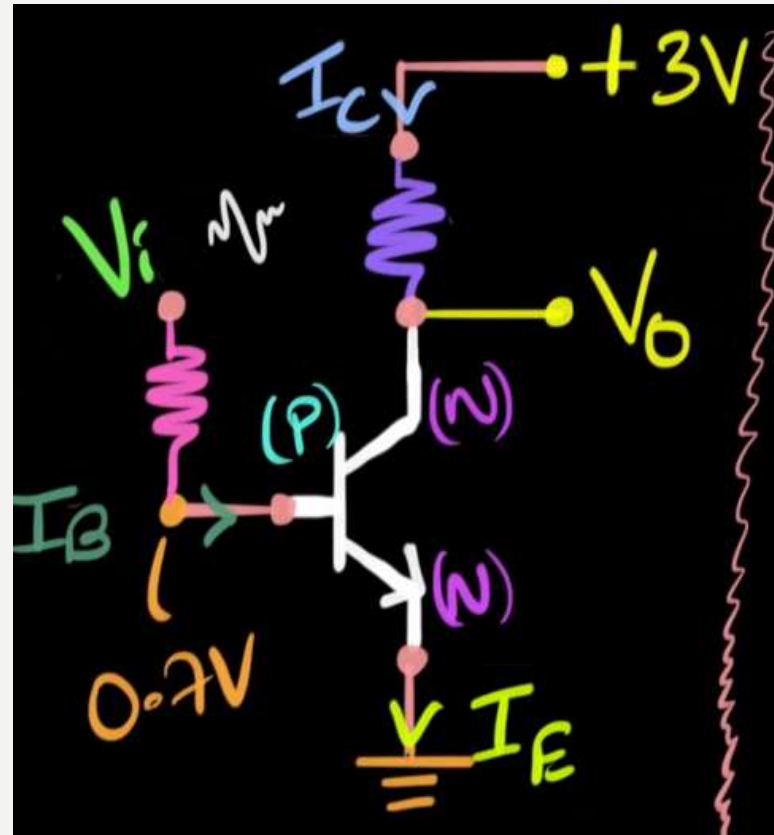


$$\Delta I_C = \beta \Delta I_B \quad \Delta V_O = 10 \Delta V_i$$

$$I_{C1} = \beta I_{B1}$$

$$I_{C2} = \beta I_{B2}$$

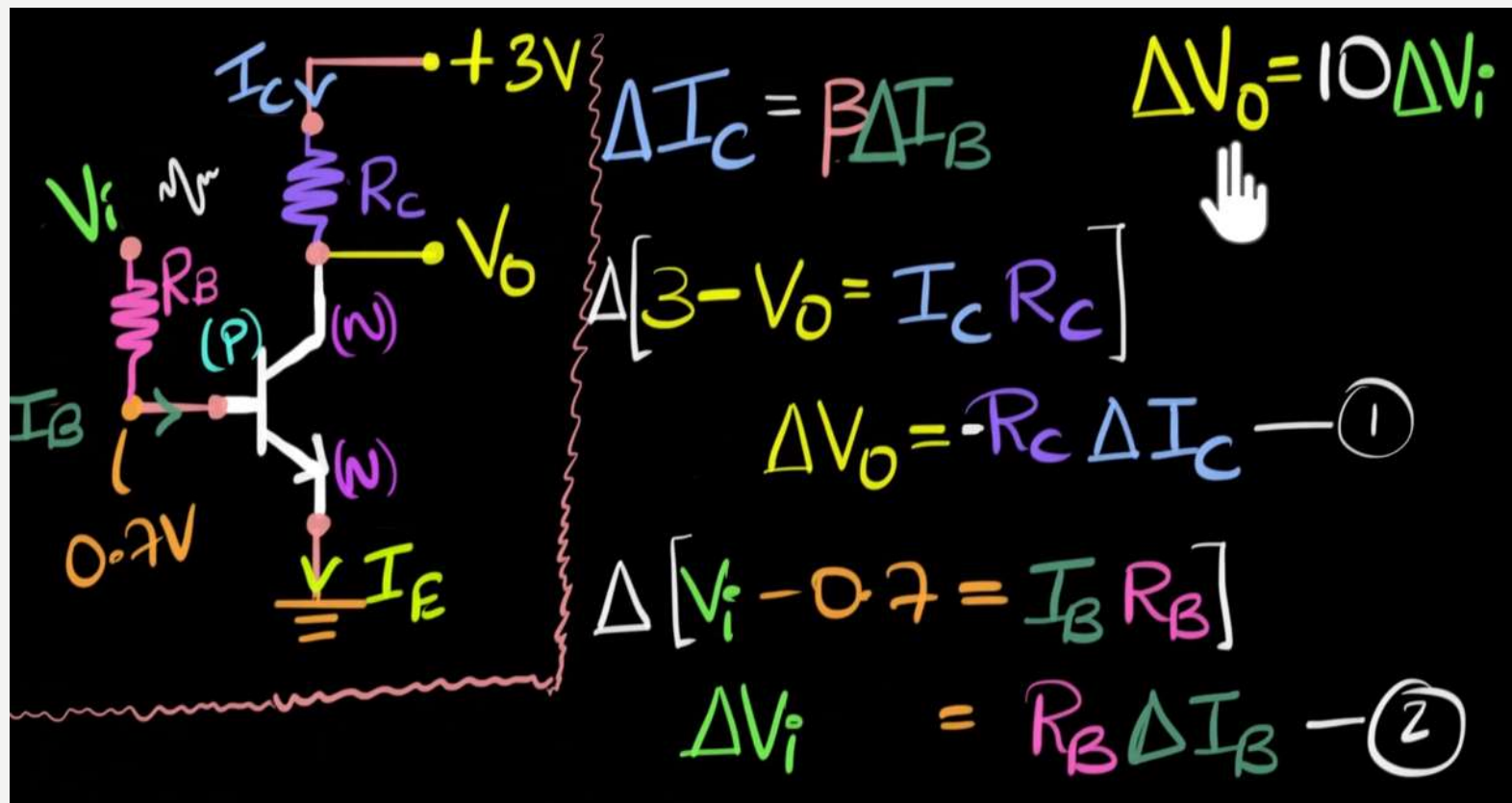
$$I_{C2} - I_{C1} = \beta I_{B2} - \beta I_{B1}$$



$$\Delta V_o = - \frac{R_c}{R_B} \beta \Delta V_i$$

A_v
Voltage gain

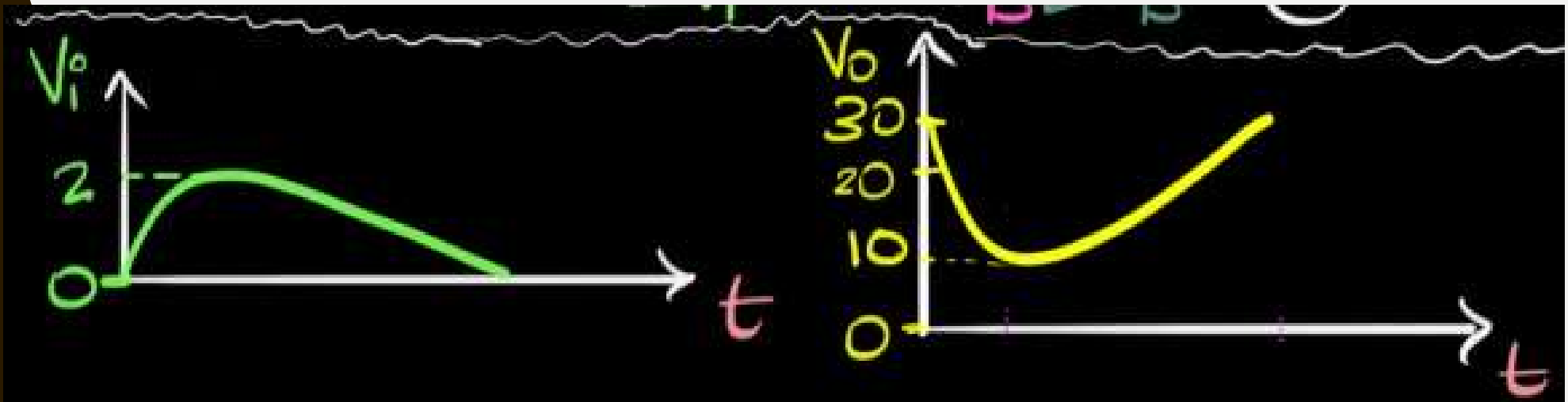- If input voltage V_i increases, current I_B increases, due to which I_C increases, due to which there is more voltage drop across R_C
- As a result, there is a higher voltage drop at the output.





Common-Base Configuration of Transistor

B, E and C

i) Common Base

ii) Common Emitter

iii) Common Collector

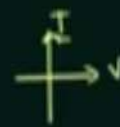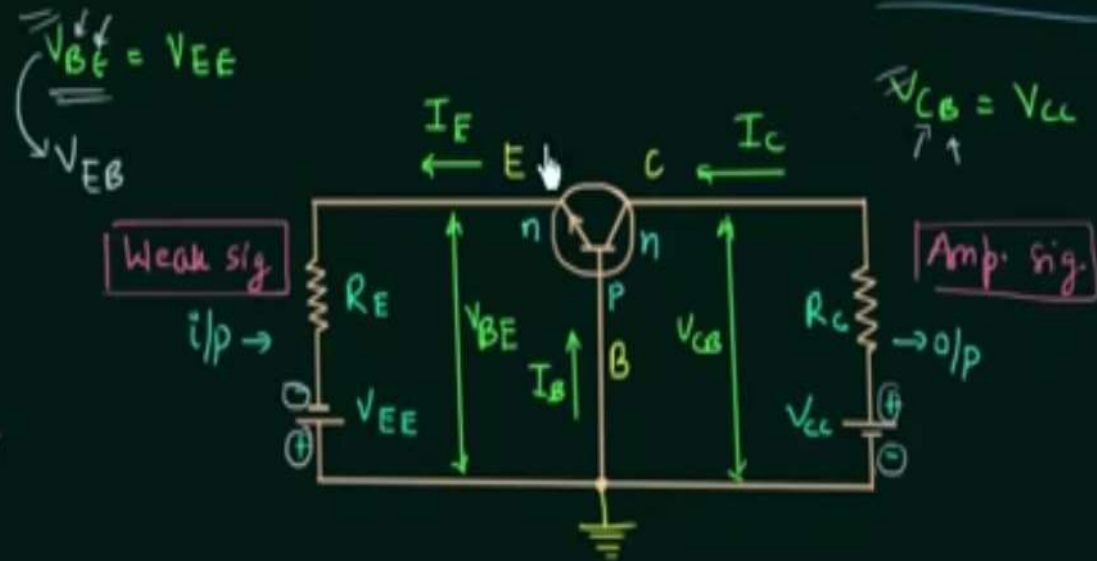

D \rightarrow single port

I \rightarrow two port

i/p ch. $\rightarrow I_E$ vs V_{BE}

o/p ch. $\rightarrow I_C$ vs V_{CB}

$J_1 \rightarrow$ f.b.

$J_2 \rightarrow$ r.b.

$E-B$ diode

$B-C$ diode



KCL:

active mode

$$I_E = I_B + I_C \quad \text{--- (1)}$$

r.s.c.

$$I_C = \alpha I_E + I_{C0}$$

open ct

$$\text{or } I_C = \alpha I_E + I_{C0}$$

$$I_E \gg I_{C0}$$

$$I_C = \alpha I_E \Rightarrow$$

o/p
↑
 $\alpha = \frac{I_C}{I_E}$ i/p

Common base current gain/am. factor

$$\alpha = 0.95 - 0.98 \Rightarrow 95\% \text{ to } 98\%$$

$$I_B = (1 - \alpha) I_E$$



D → single port

I → two port

i/p a → I_E vs V_{BE}

o/p c → I_C vs V_{CB}

$J_1 \rightarrow$ f.b.



$J_2 \rightarrow$ r.b.

EB diode


BC diode
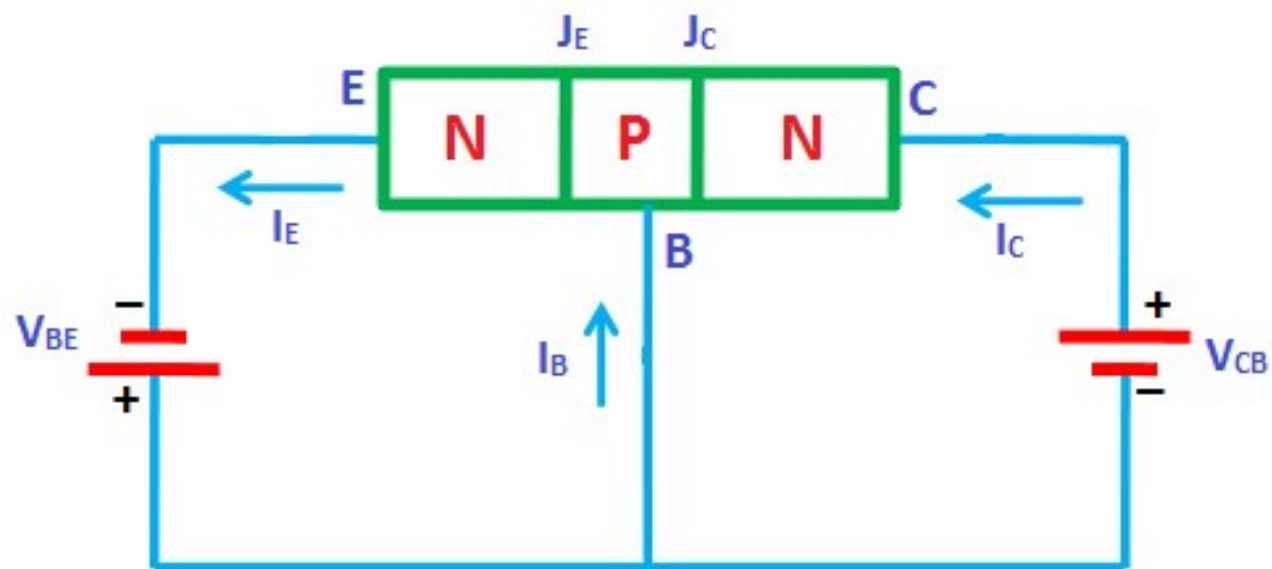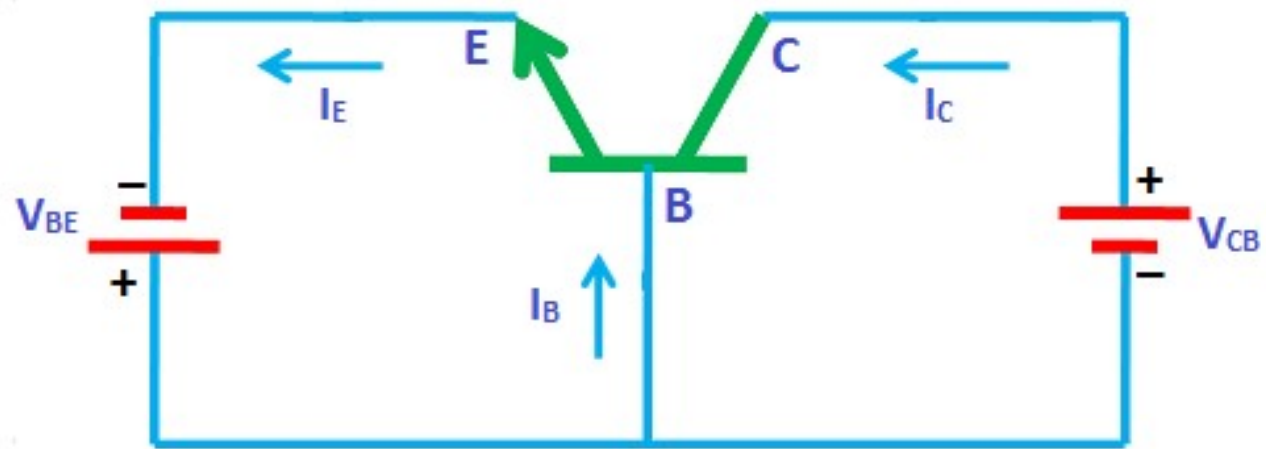
$$\text{gain} = \frac{\text{o/p}}{\text{i/p}}$$






Common base configuration

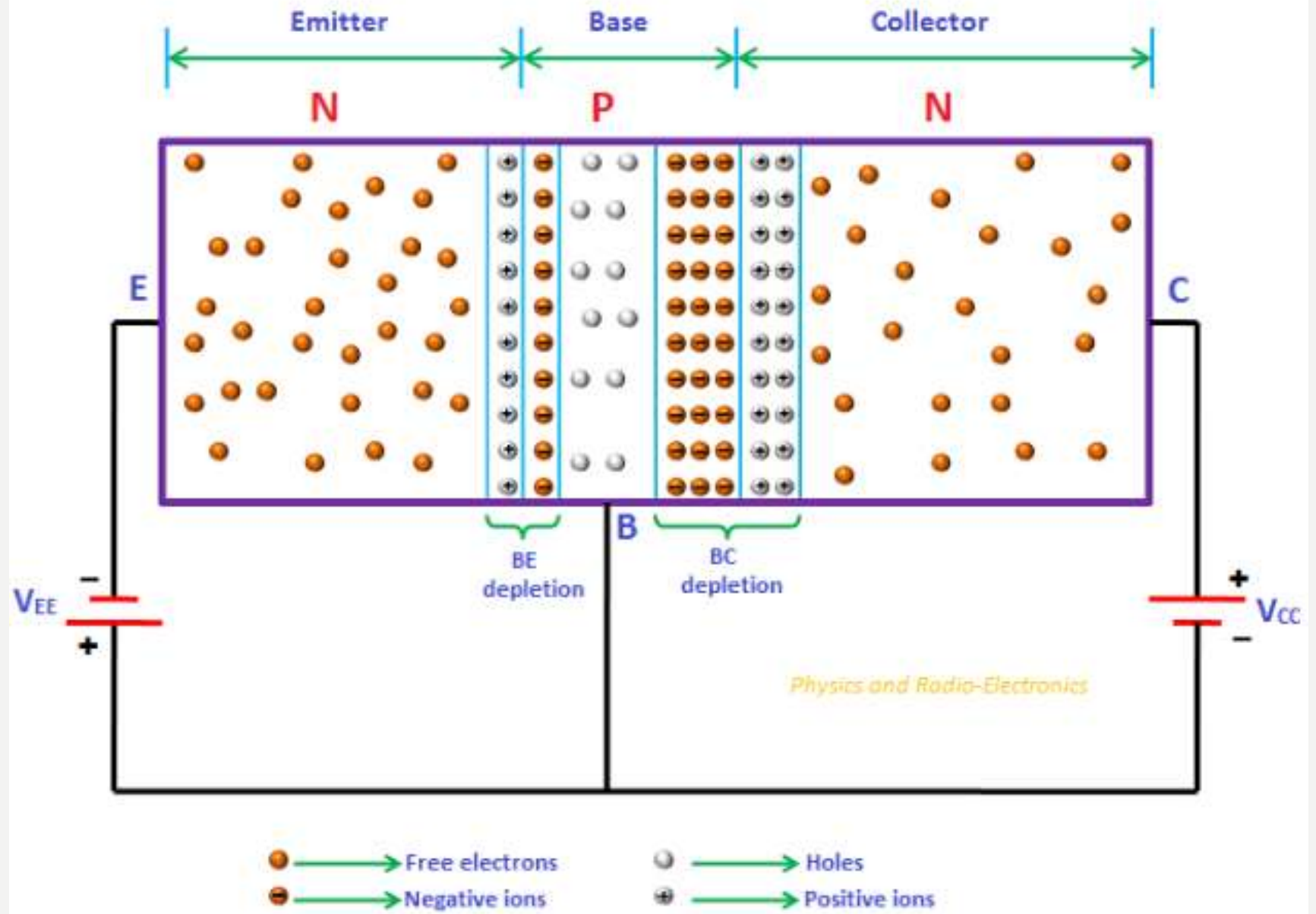


INPUT CHARACTERISTICS

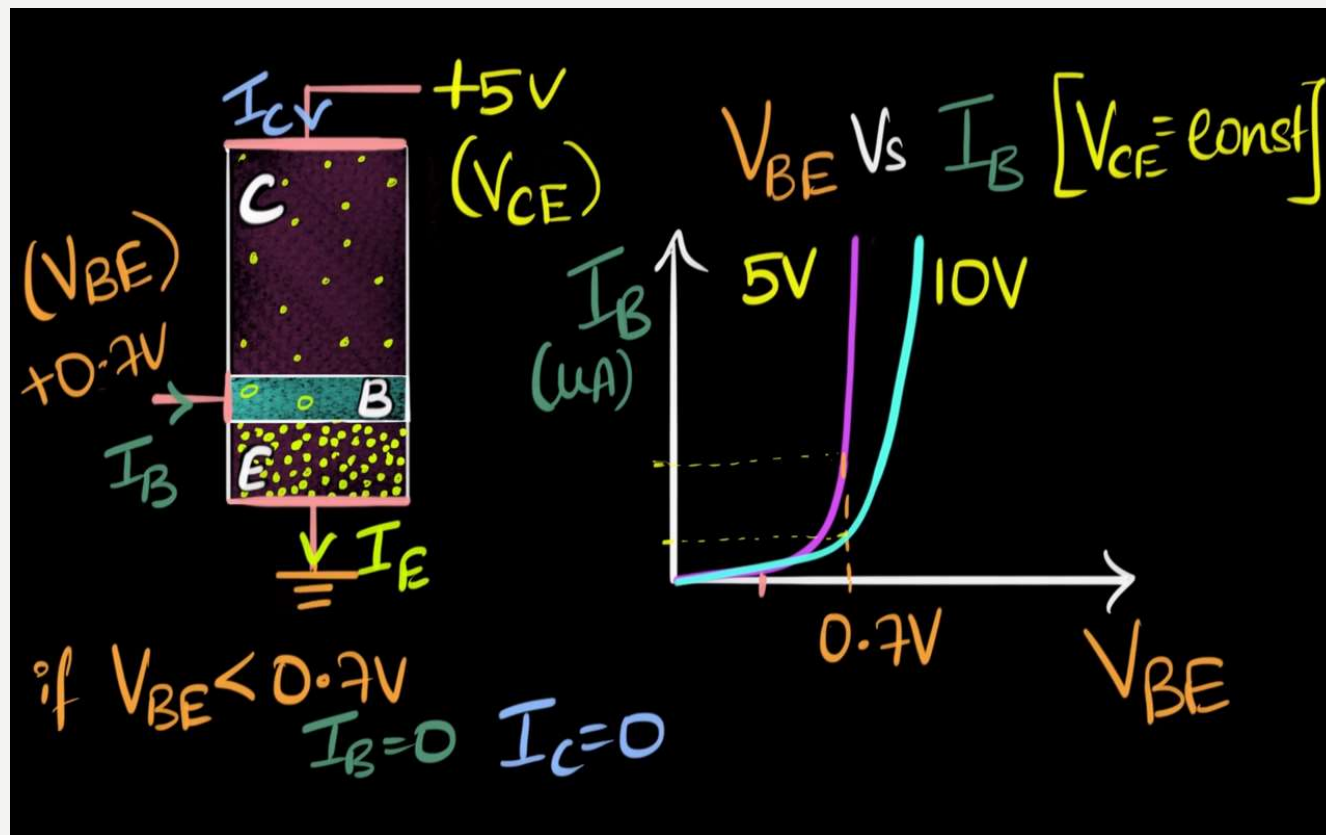

Common Base Transistor (Input Characteristics)

Early Effect

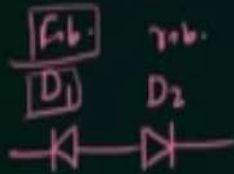

f.b. diode


i/p I V_{CB} i/p V for diff o/p V.

$$\underline{i/p I} = \underline{I_E}$$

$$\underline{i/p V} = \underline{V_{BE}}$$

$$o/p I = I_C$$
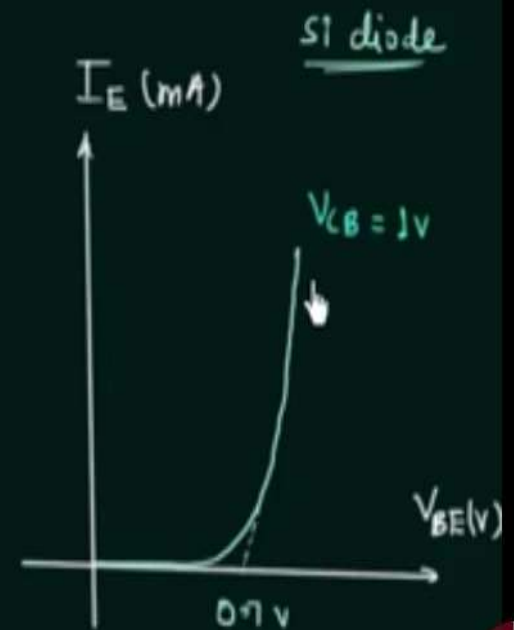
$$\underline{o/p V} = \underline{V_{CB}}$$




James M. Early

Early Effect: base width mod.

$$\boxed{V_{CB} \uparrow} \Rightarrow I_E \uparrow$$


O/p $I = I_C$

O/p $V = \boxed{V_{CB}}$

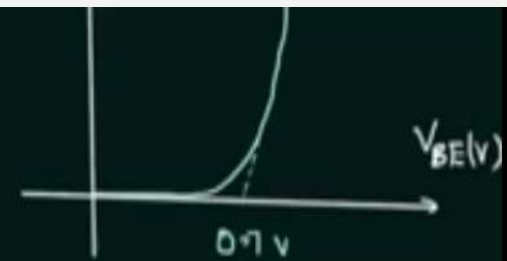

width of d.l. \uparrow

Conc. grad \uparrow

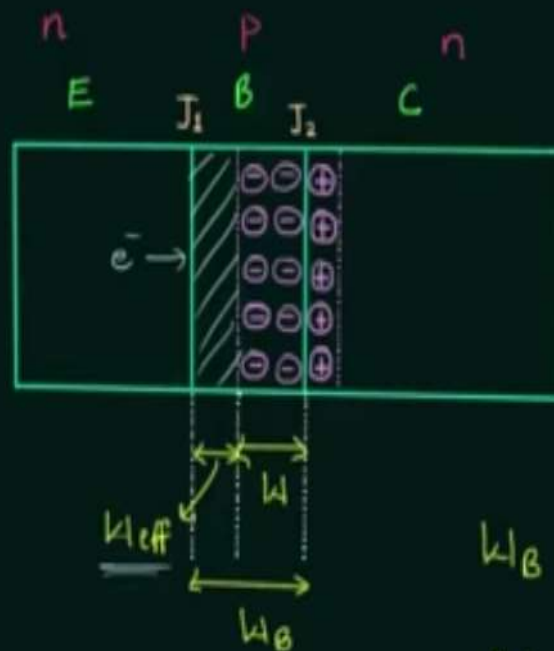

$W_B \rightarrow$ width of base/

Metallurgical base width

$$W_B = W_{eff} + W \quad V_{CB} \uparrow \Rightarrow W \uparrow \Rightarrow \boxed{W_{eff} \downarrow}$$

$$W_{eff} = W_B - (W)$$

$$\downarrow$$

$$\boxed{I_E \uparrow}$$


Early effect (or) Base-width modulation:-

In Common Base configuration in the Reverse Bias, As the voltage V_{CC} increases, the space-charge width between collector and base tends to increase, with the result that the effective width of the base decreases. This dependency of Base-width on the Collector to emitter voltage is known as the early effect.

The early effect has three consequences:-

1. There is less chance for recombination with in the base region. Hence α increases with increasing $|V_{CB}|$.
2. The charge gradient is increased with in the base and consequently, the current of minority carriers injected across the emitter junction increases.
3. For extremely large voltages, the effective Base-width may be reduced to zero, causing voltage break-down in the transistor. This phenomenon is called the Punch-through.

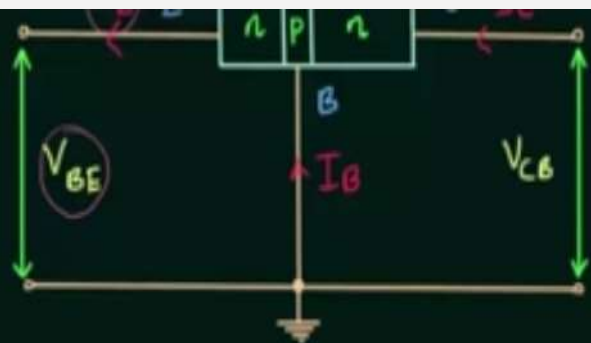For higher values of V_{CB} , due to early effect the value of α increases, for example α changes say from 0.98 to 0.985. Hence there is a very small positive slope in the CB output characteristics and hence the output resistance is not zero.




James M. Early

Early Effect: base width mod.

$$\boxed{V_{CB} \uparrow} \Rightarrow I_E \uparrow$$

Conc. grad \uparrow

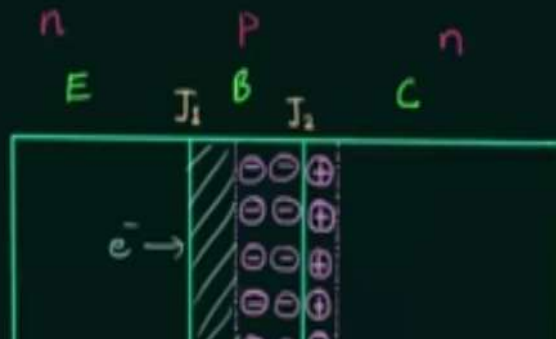


$$i/p I = I_E$$

$$i/p V = V_{BE}$$

$$o/p I = I_C$$

$$o/p V = \boxed{V_{CB}}$$

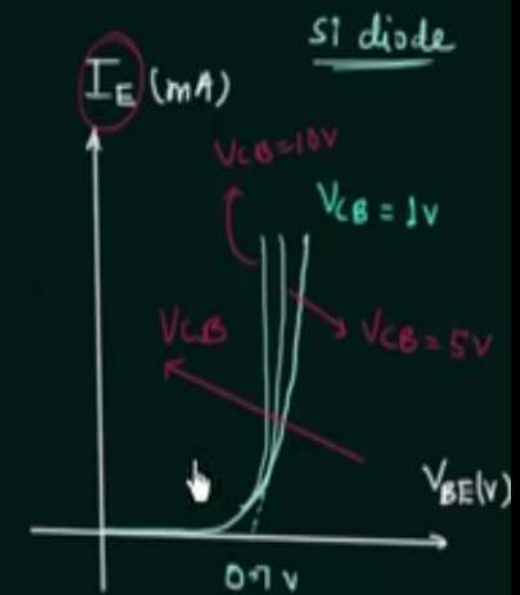


width of d.l. \uparrow


$W_B \rightarrow$ width of base/

Modulation of base



Fig. 5-7 Common-base input characteristics of a typical p - n - p germanium junction transistor.

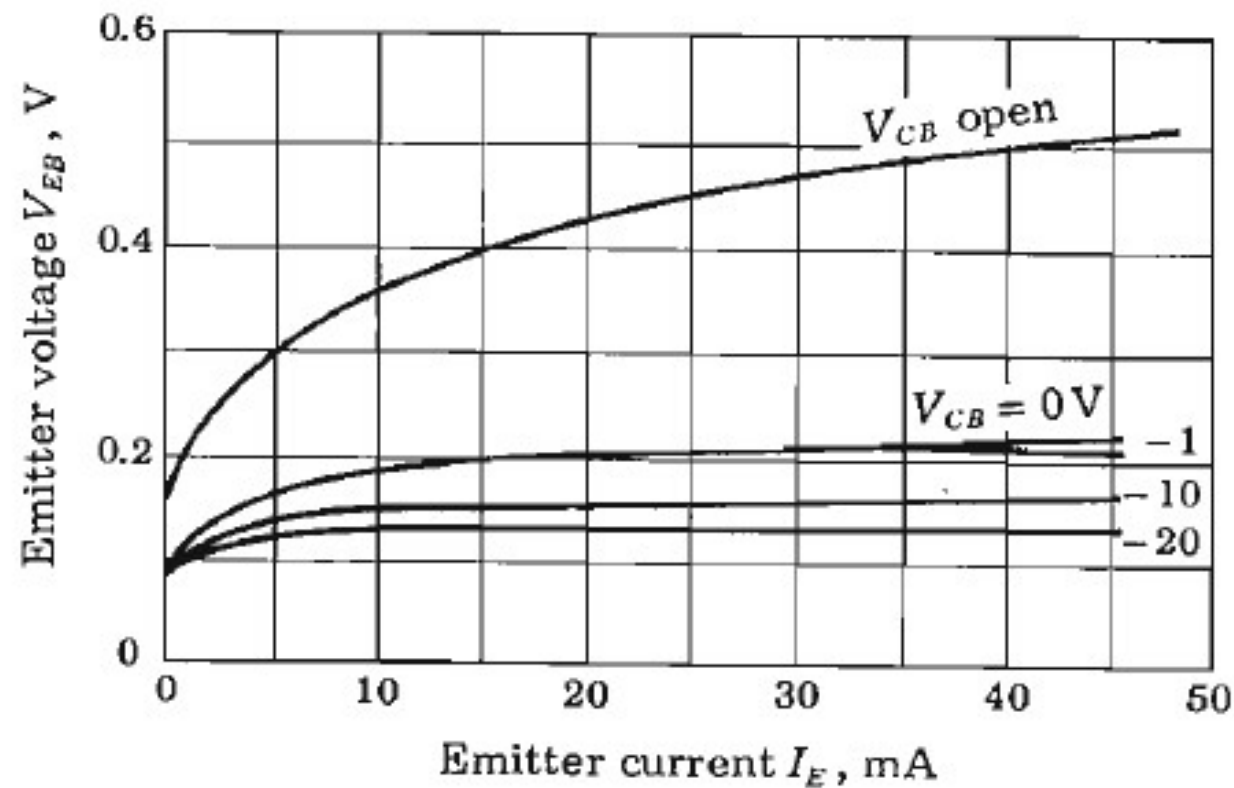

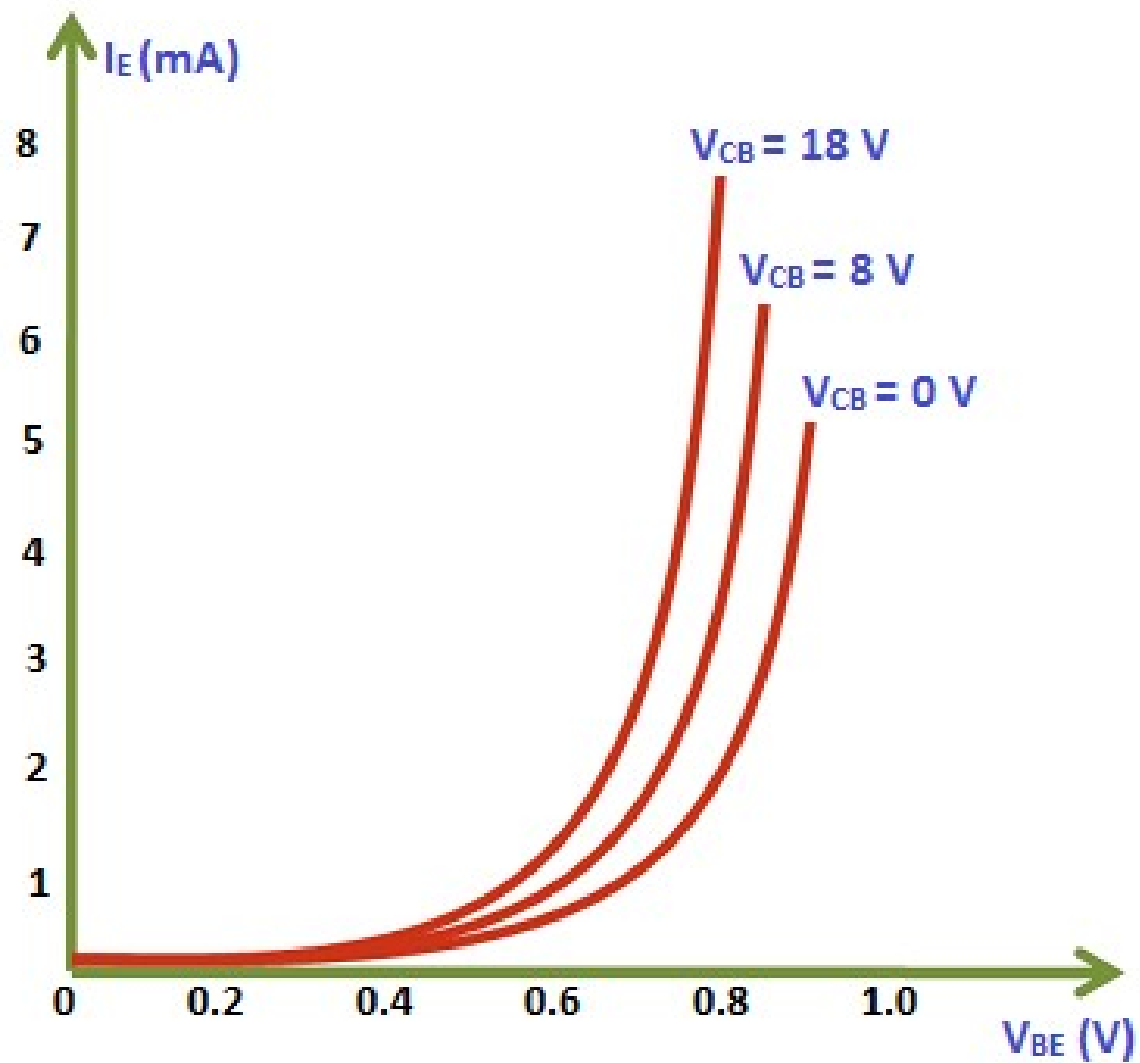


I/p characteristics CB configuration

- What is the value of thermal voltage at room temperature?
- (a) 26 V (b) 26 mV (c) 260 mV (d) 0.026 mV


- The Early Effect is also called as
- a) Base-width modulation effect
- b) Base-width amplification effect
- c) Both of the mentioned
- d) None of the mentioned

- The value of alpha of a transistor is
- a) more than 1 b) less than 1 c) 1 d) none of the above

OUTPUT CHARACTERISTICS

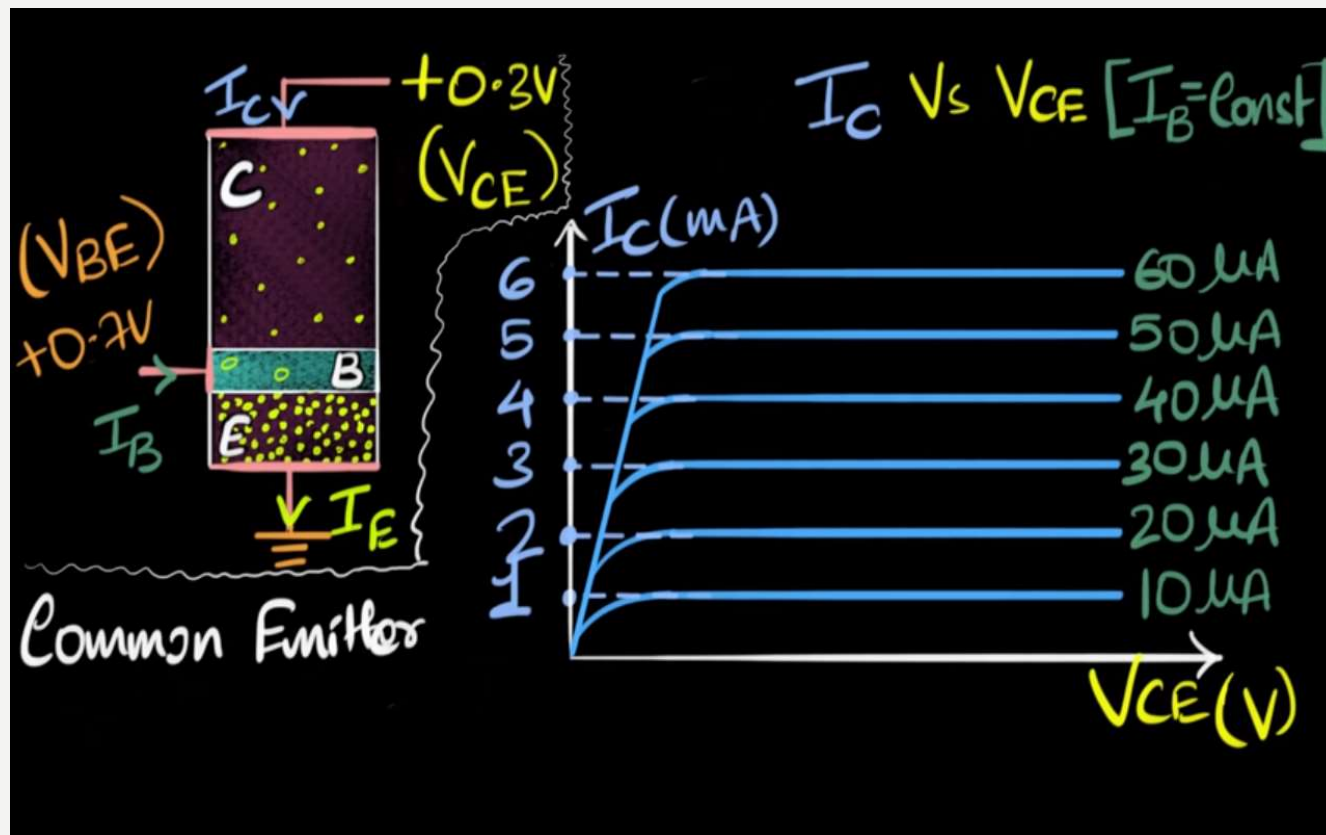

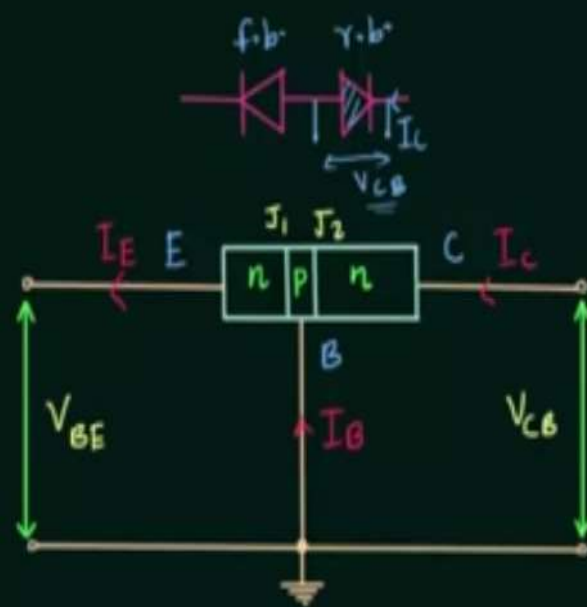
Common Base Transistor (Output Characteristics)




$$I_C = \alpha I_E + I_{CBO}$$

r_{cb} diode

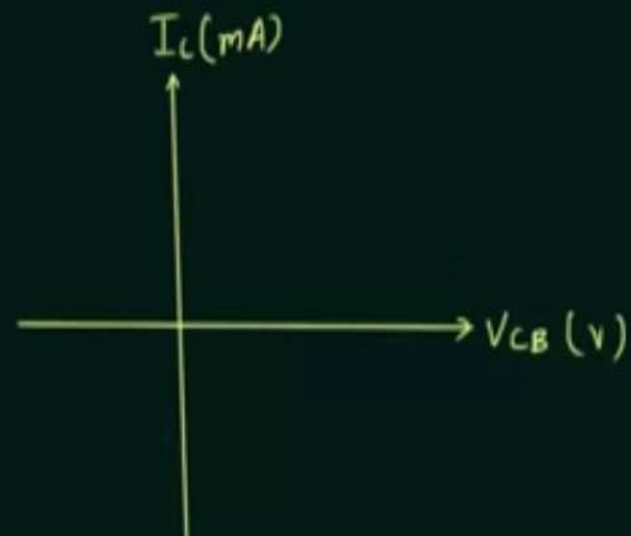O/p I_C vs O/p V_{CB} for various
levels of i/p I_E



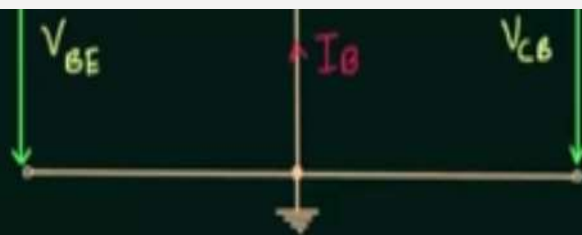


$$I_C = \alpha I_E + \boxed{I_{CBO}} \text{ (independent of } V_{CB})$$

$$I_C \approx \alpha I_E$$

$$\boxed{I_C \approx I_E} \quad (\alpha = 0.95 - 0.98)$$

o/p
i/p

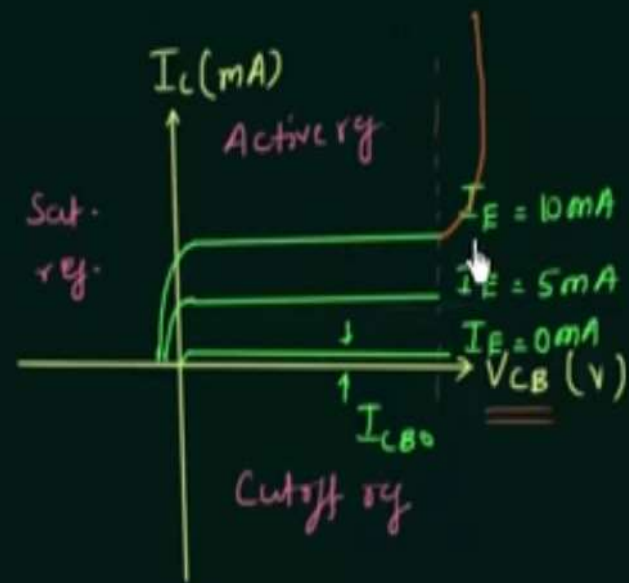

$$I_C = \alpha I_E + I_{CBO} \quad (\text{independent of } V_{CB})$$

$$I_C \approx \alpha I_E$$

$$\boxed{I_C \approx I_E} \quad (\alpha = 0.95 - 0.98)$$

o/p i/p



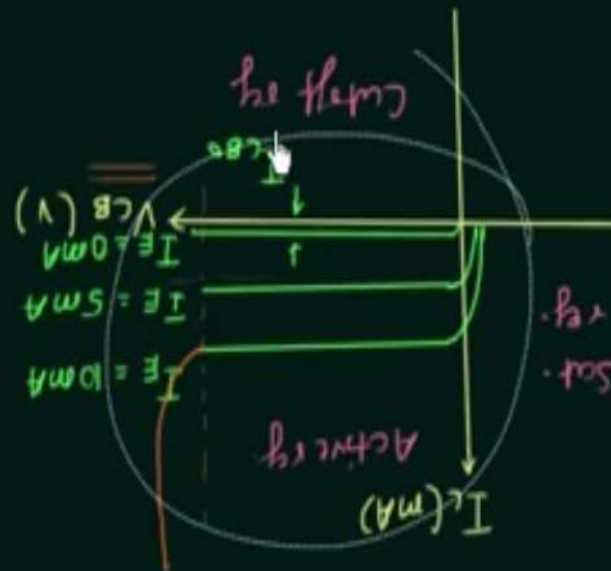
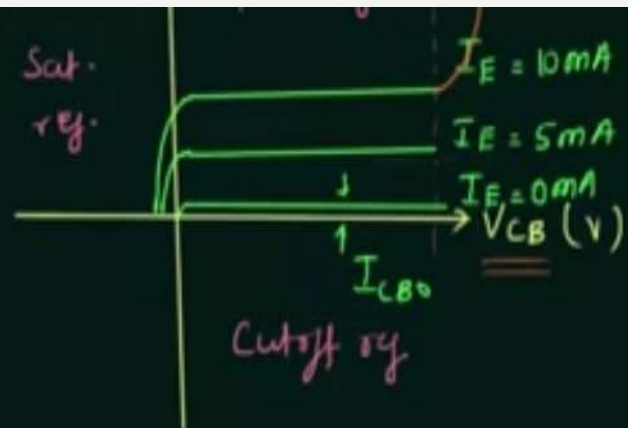




Fig. 5-6 Typical common-base output characteristics of a $p-n-p$ transistor. The cutoff, active, and saturation regions are indicated. Note the expanded voltage scale in the saturation region.

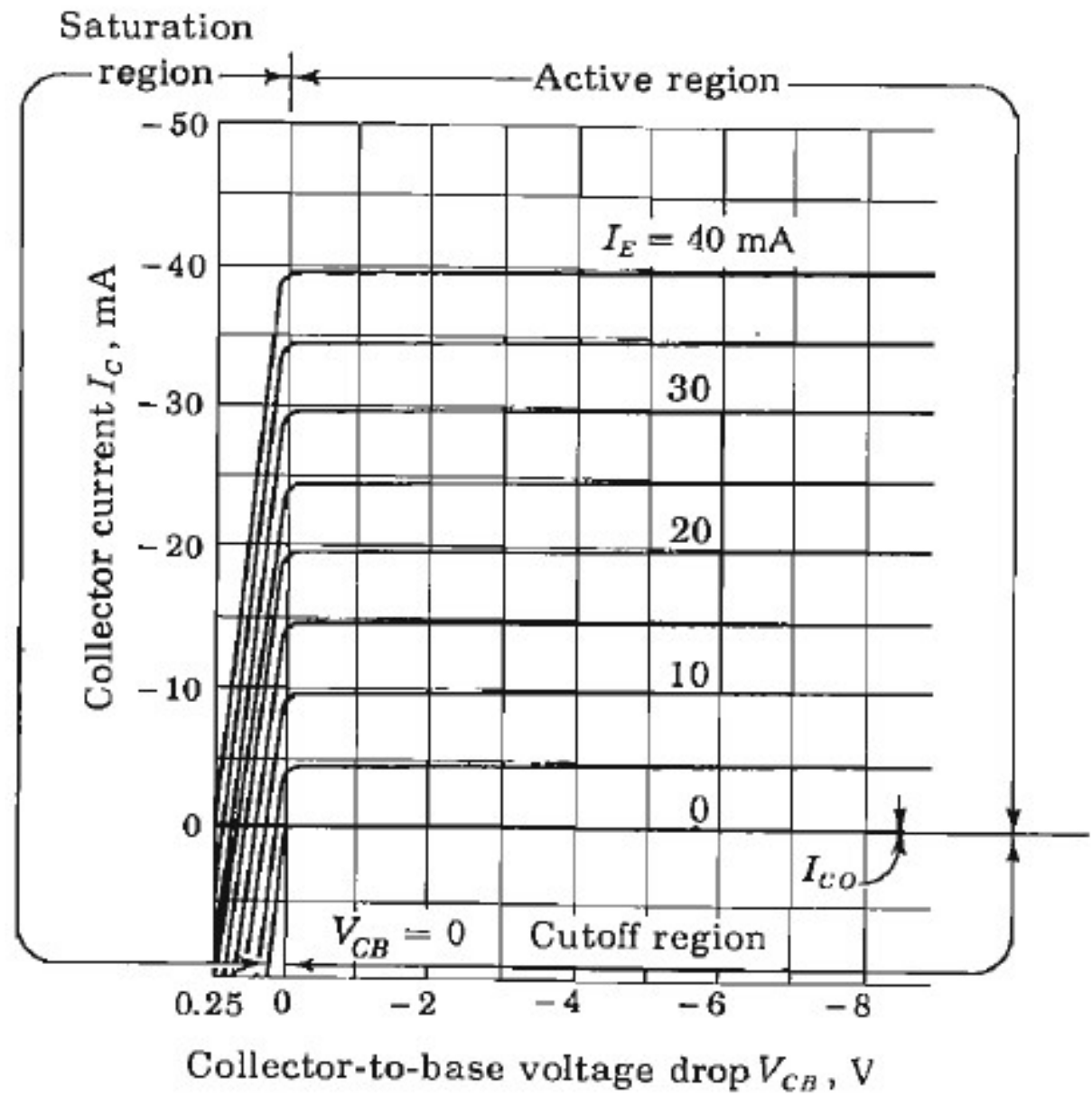

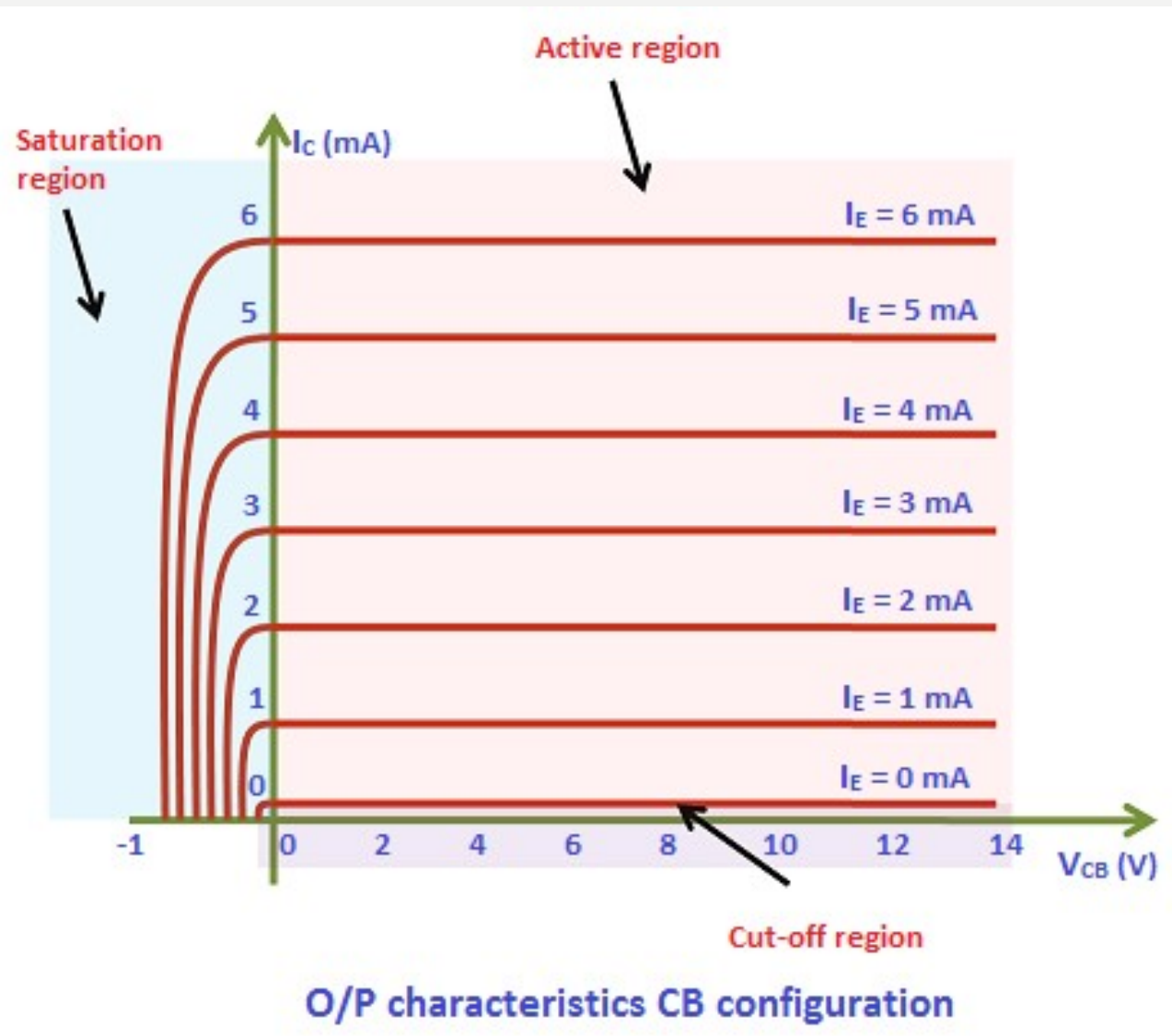

Common-Emitter Configuration of Transistor

Amplifier \Rightarrow Active mode

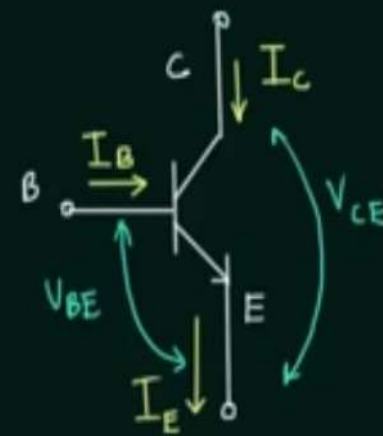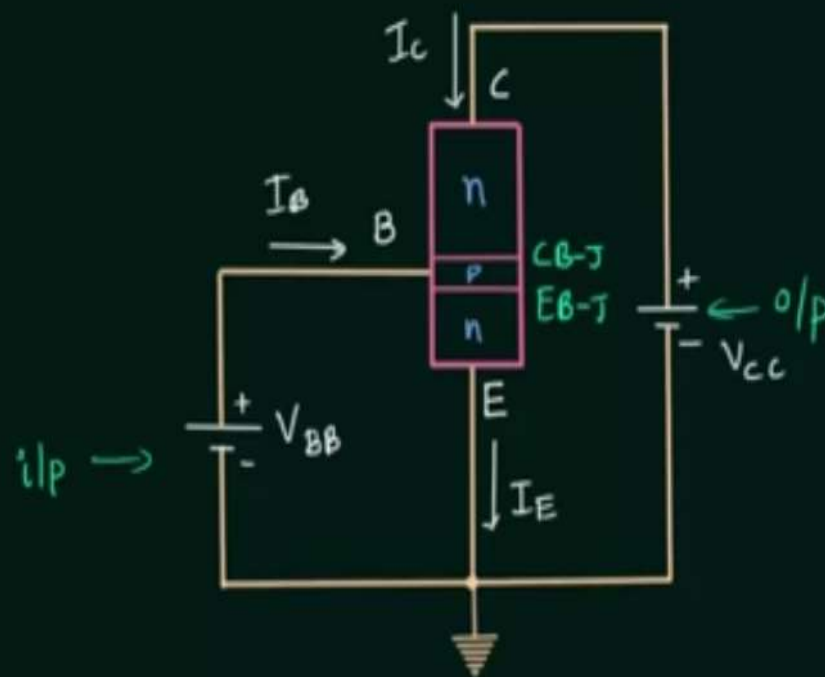

i/p cur. $\rightarrow I_B$

o/p cur. $\rightarrow I_C$

i/p vol. $\rightarrow V_{BE}$

o/p vol. $\rightarrow V_{CE}$



- Input current in CB configuration?
- A I_B
- B I_C
- C I_E
- D None of the above

- Input current in CE configuration?

A I_B

B I_C

C I_E

D None of the above



i/p cur. $\rightarrow I_B$
i/p vol. $\rightarrow V_{BE}$

o/p cur. $\rightarrow I_C$
o/p vol. $\rightarrow V_{CE}$

$$I_E = I_C + I_B \quad \text{--- ①}$$

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- ②}$$

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$\therefore (1 - \alpha) I_C = \alpha I_B + I_{CBO}$$



$$I_C = \alpha I_E + I_{CBO} \quad \text{--- ②}$$

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$\Rightarrow (1-\alpha)I_C = \alpha I_B + I_{CBO}$$

$$\begin{aligned} \beta+1 &= \frac{\alpha}{1-\alpha} + 1 \\ &= \frac{1}{1-\alpha} \end{aligned}$$

$$I_C = \underbrace{\frac{\alpha}{1-\alpha}}_{\beta} I_B + \underbrace{\frac{1}{1-\alpha}}_{\beta+1} I_{CBO}$$

$$\Rightarrow I_C = \beta I_B + (\beta+1) I_{CBO}$$

$$\rightarrow \alpha < 1$$

$$\text{Case-I} \rightarrow 50 \leq \beta \leq 400$$

$$\alpha = 0.98$$

$$\beta = \frac{0.98}{1-0.98} = 49$$

Case-II

$$\alpha = 0.95$$

$$\beta = \frac{0.95}{1-0.95} = 19$$



$$\beta + 1 = \frac{\alpha}{1 - \alpha} + 1$$

$$= \frac{1}{1 - \alpha}$$

$$I_C = \underbrace{\frac{\alpha}{1 - \alpha}}_{\beta} I_B + \underbrace{\frac{1}{1 - \alpha}}_{\beta + 1} I_{CBO}$$

$$\Rightarrow I_C = \beta I_B + \underbrace{(\beta + 1) I_{CBO}}_{I_{CEO}}$$

$$I_C = \beta I_B + I_{CEO}$$

$$I_{CEO} \ll \beta I_B$$

$$I_C = \beta I_B$$

$$\beta = \frac{I_C}{I_B}$$

Current Amp
fact.

CE Conf → C.A.

$$I_B = \underline{1 \text{ mA}}$$

$$\beta = 100$$

$$I_C = \beta I_B$$

$$I_C = \underline{100 \text{ mA}}$$



CE conf → C.A.

$$I_B = \underline{1 \text{ mA}}$$

$$\beta = 100$$

$$I_C = \beta I_B$$

$$I_C = \underline{100 \text{ mA}}$$

NOTE :-

$$\underline{I_C} = \alpha \underline{I_E} + \underline{I_{CBO}}$$

$$I_C = \beta I_B + I_{CE0}$$

$$I_{CE0} \ll \beta I_B$$

$$I_C = \beta I_B$$

$$\beta = \frac{I_C}{I_B}$$


Current Amp
fact

CE

$$\underline{I_C} = \beta I_B + (\beta + 1) \underline{I_{CBO}}$$



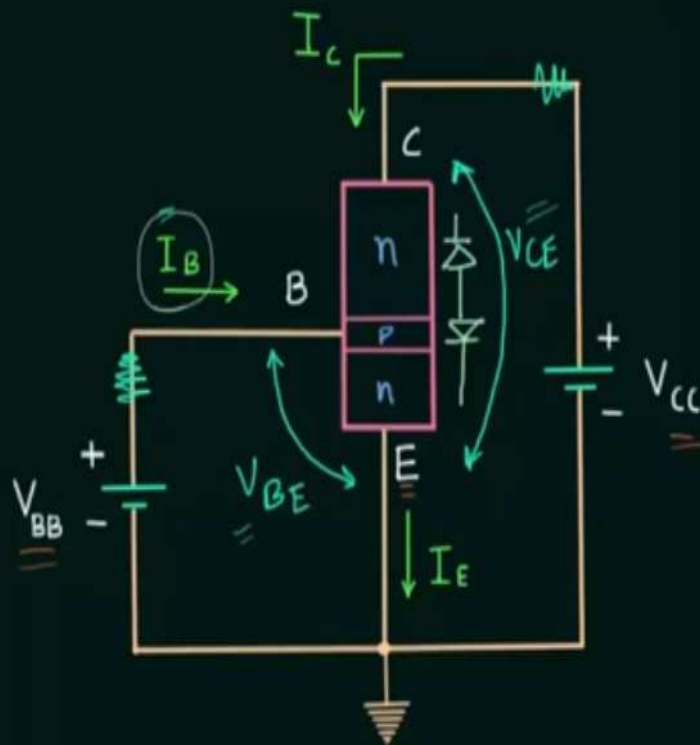Common Emitter Transistor (Input & Output Characteristics)




V_{BB} & $V_{CC} \rightarrow$ Biasing pot

$\rightarrow I_B$ vs V_{BE} for diff. values of

V_{CE}

I_B (mA)

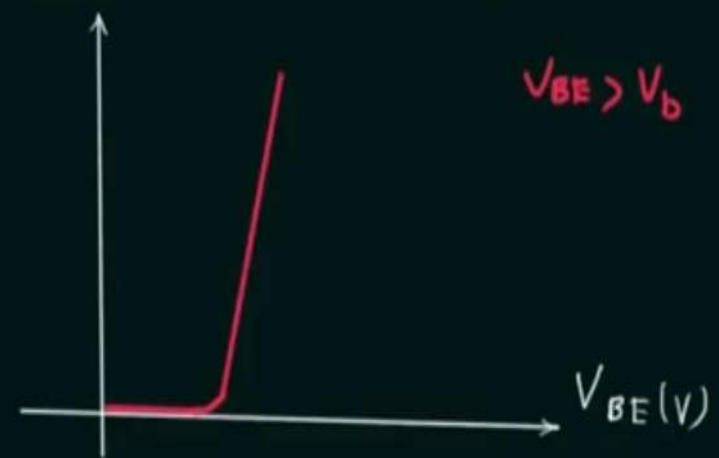

$$V_{BE} = f_1(V_{CE}, I_B)$$

$$I_C = f_2(V_{CE}, I_B)$$



3. A transistor has a β_{DC} of 250 and a base current, I_B , of $20 \mu A$. The collector current, I_C , equals:
- A. $500 \mu A$
 - B. 5 mA
 - C. 50 mA
 - D. 5 A

1. Which of the following condition is true for cut-off mode?

- a) The collector current is zero
- b) The collector current is proportional to the base current
- c) The base current is non zero
- d) All of the mentioned

Which of the following is true for a pnp transistor in saturation region?

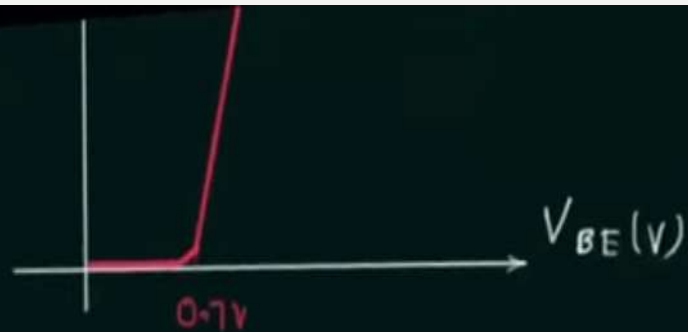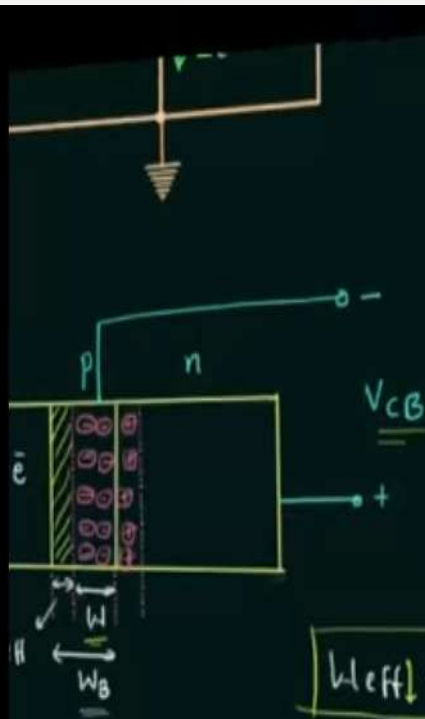- a) CB junction is reversed bias and the EB junction is forward bias
- b) CB junction is forward bias and the EB junction is forward bias
- c) CB junction is forward bias and the EB junction is reverse bias
- d) CB junction is reversed bias and the EB junction is reverse bias



$$V_{CE} = \underline{\underline{V_{CB} + V_{BE}}}$$


$$\boxed{W_{eff} \downarrow = W_B - W}$$

↓
const.


$$\boxed{V_{CE} \uparrow} \Rightarrow V_{CB} \uparrow \Rightarrow W \uparrow \Rightarrow \underline{\underline{W_{eff} \downarrow}} \Rightarrow \boxed{I_B \downarrow} \text{ (i/p current)}$$

↓




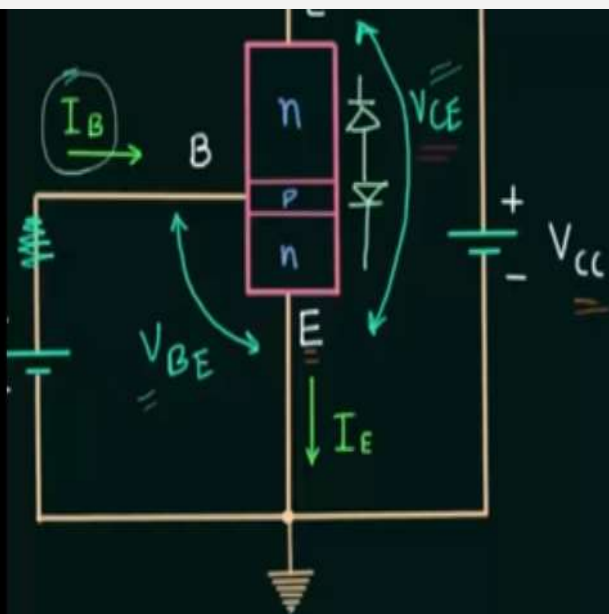

→ I_B vs V_{BE} for diff. values of

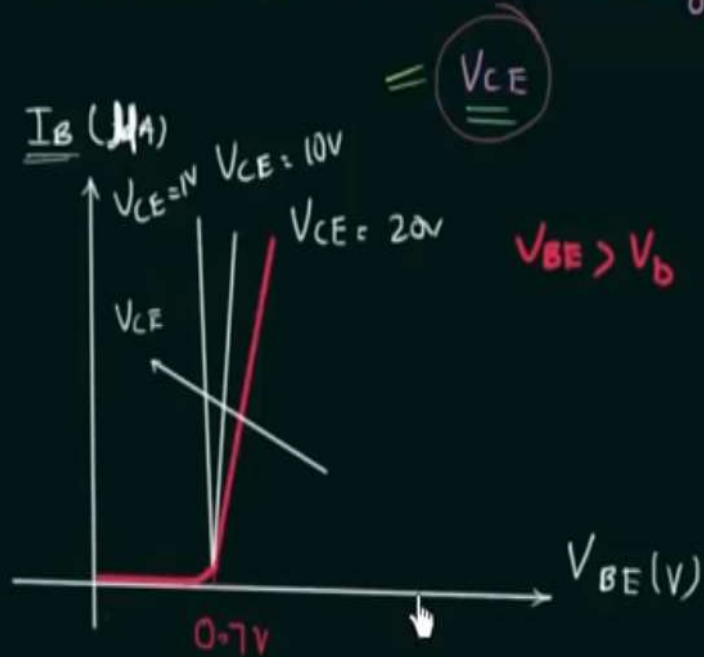

$V_{BE} > V_D$

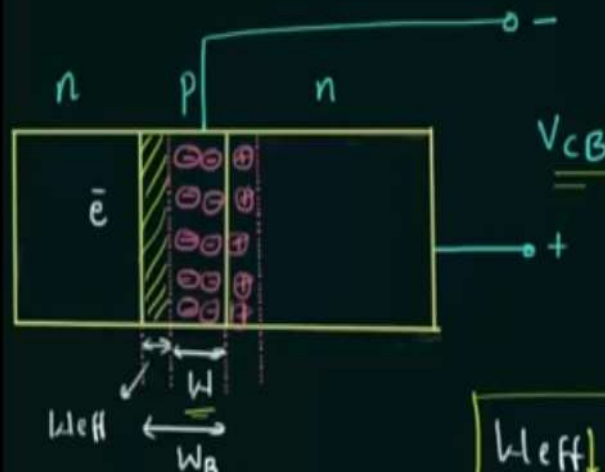

$$V_{CE} = V_{CB} + V_{BE}$$

$$W_{eff} = W_B - W_1$$



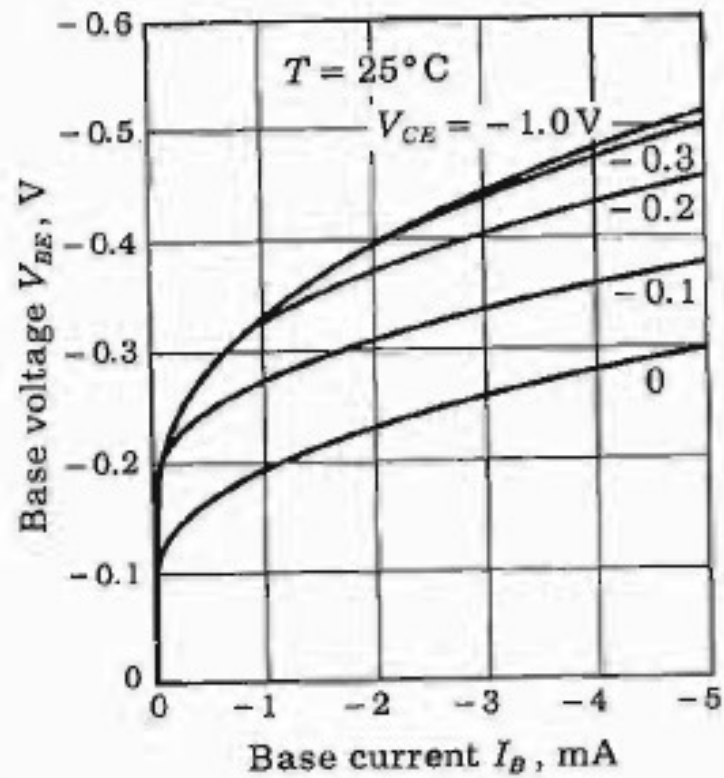


Fig. 5-11 Typical common-emitter input characteristics of the *p-n-p* germanium junction transistor of Fig. 5-10.

I_C vs V_{CE} for diff levels of I_B

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$


$$\underline{I_B = 0}$$

$$\underline{I_C = (\beta + 1) I_{CBO}}$$

$$I_B = 0.1 \text{ mA} \rightarrow I_C = 5 \text{ mA}$$

$$I_B = 0.2 \text{ mA} \rightarrow I_C = 10 \text{ mA}$$
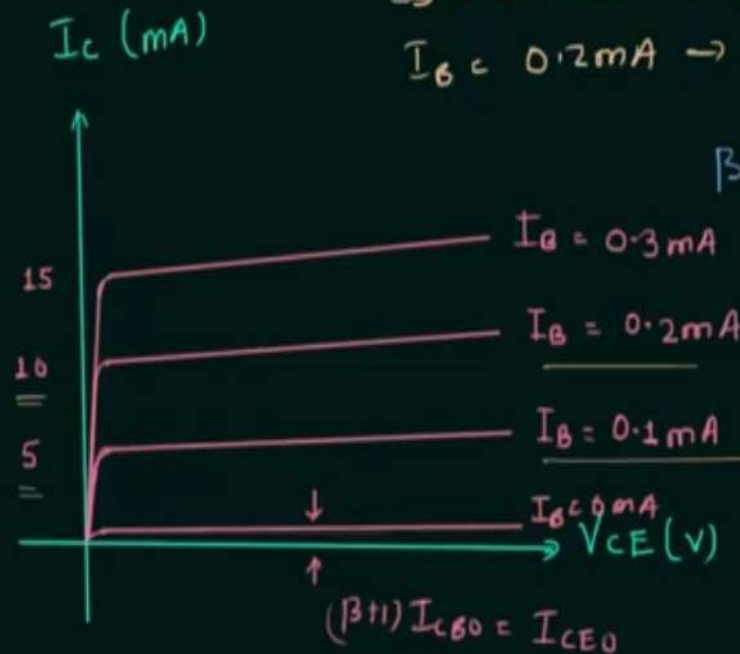
$$\beta = \frac{\Delta I_C}{\Delta I_B}$$



$$= \beta \underline{I_B} + (\beta + 1) I_{CBO}$$

$$\underline{(\beta + 1) I_{CBO}}$$



$$I_B = 0.1 \text{ mA} \rightarrow I_C = 5 \text{ mA}$$

$$I_B = 0.2 \text{ mA} \rightarrow I_C = 10 \text{ mA}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{10 - 5}{0.2 - 0.1}$$

$$\boxed{\beta = 50}$$

$$I_B = 0.3 \text{ mA}$$

$$I_B = 0.2 \text{ mA}$$

$$I_B = 0.1 \text{ mA}$$

$$I_B = 0 \text{ mA}$$

$$\underline{(\beta + 1) I_{CBO} = I_{CEO}} \quad \underline{V_{CE} (V)} \quad E-E.$$

$$\underline{\underline{\uparrow V_{CE} = \uparrow V_{CB} + V_{BE}}}$$

$$k_{eff} \downarrow \Rightarrow \underline{I_B} \downarrow \Rightarrow \underline{I_C} \uparrow$$



$$\beta I_B + (\beta + 1) I_{CBO}$$

$$(\beta + 1) I_{CBO}$$

Col I Col II

A → Sat.

B → Cut.
C → Active

V_{CE} very small (C)

$$-V_{CE} = V_{CB} + V_{BE}$$


$$\text{f.v. } V_{CB} = -V_{CE} - V_{BE}$$

$$I_B = 0.1 \text{ mA} \rightarrow I_C = 5 \text{ mA}$$

$$I_B = 0.2 \text{ mA} \rightarrow I_C = 10 \text{ mA}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{10 - 5}{0.2 - 0.1}$$

$$\beta = 50$$

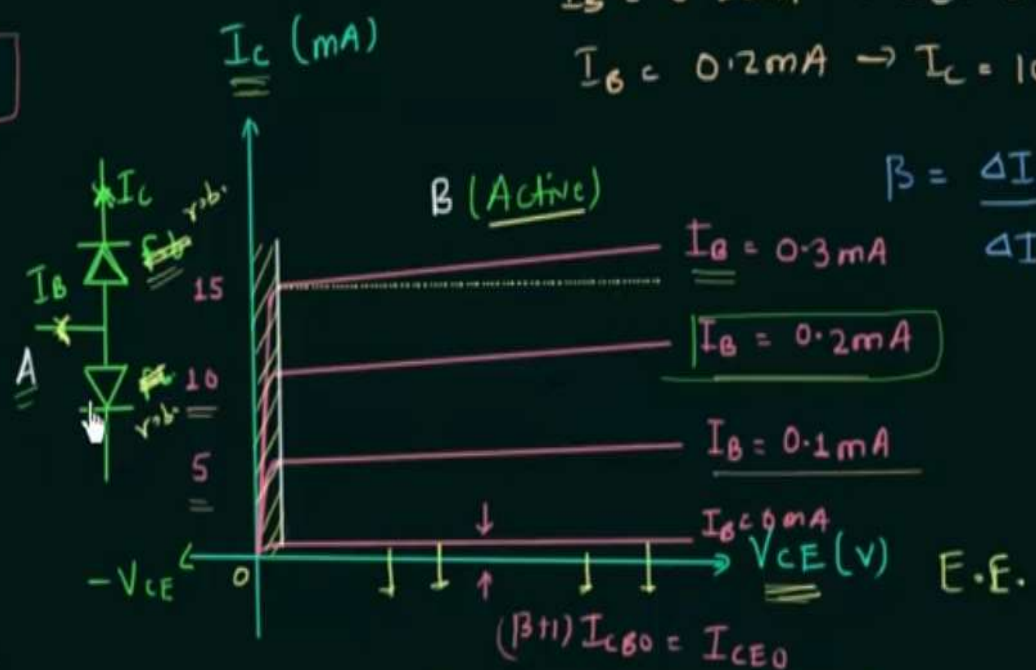


$$\uparrow V_{CE} = \uparrow V_{CB} + V_{BE}$$

$$k_{eff} \downarrow \Rightarrow I_B \downarrow \Rightarrow I_C \downarrow$$



$$V_{CB} = V_{CE} - V_{BE}$$



Fig. 5-10 Typical common-emitter output characteristics of a p - n - p germanium junction transistor. A load line corresponding to $V_{CC} = 10$ V and $R_L = 500 \Omega$ is superimposed. (Courtesy of Texas Instruments, Inc.)

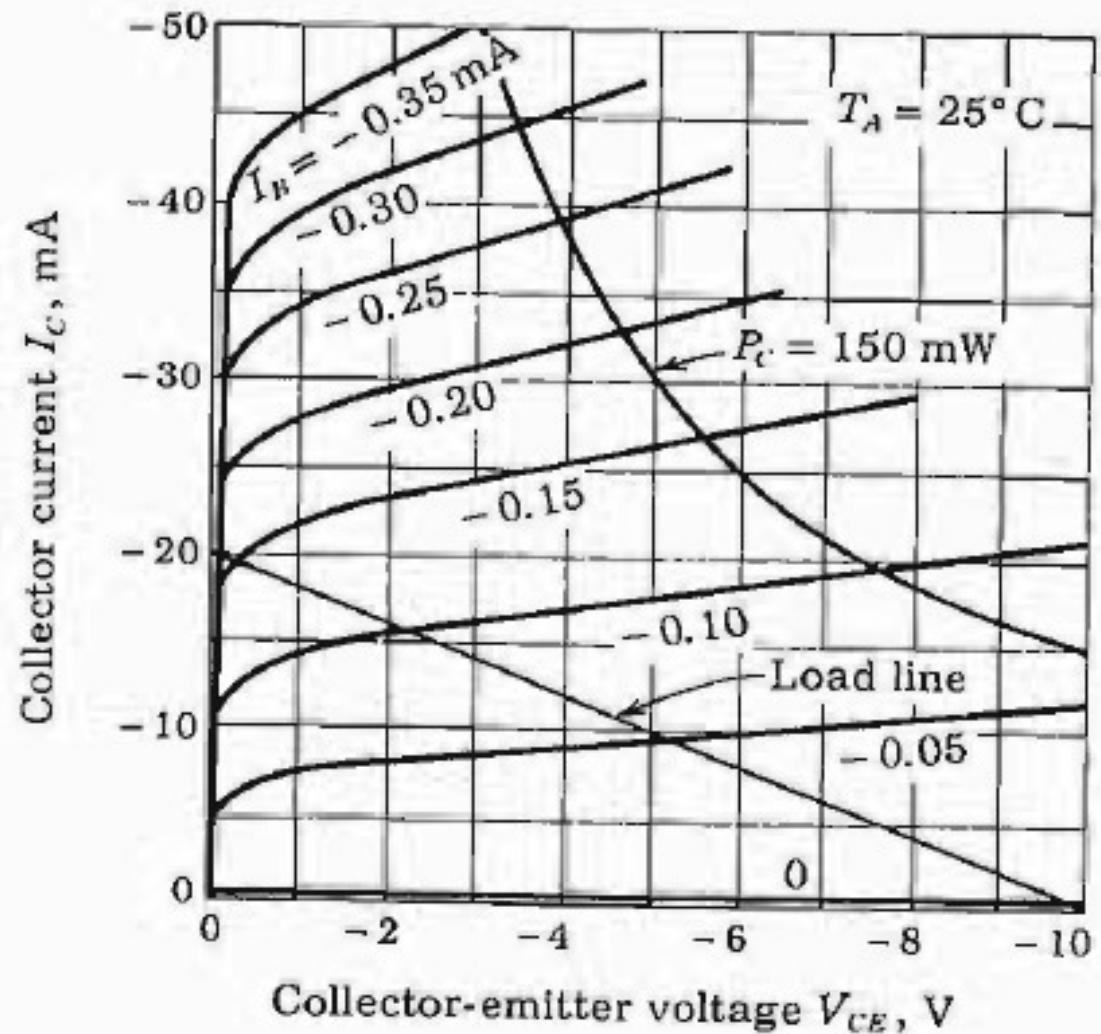

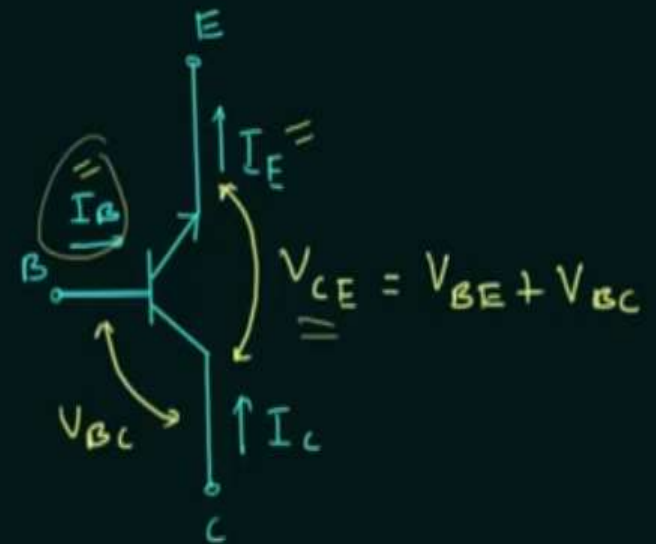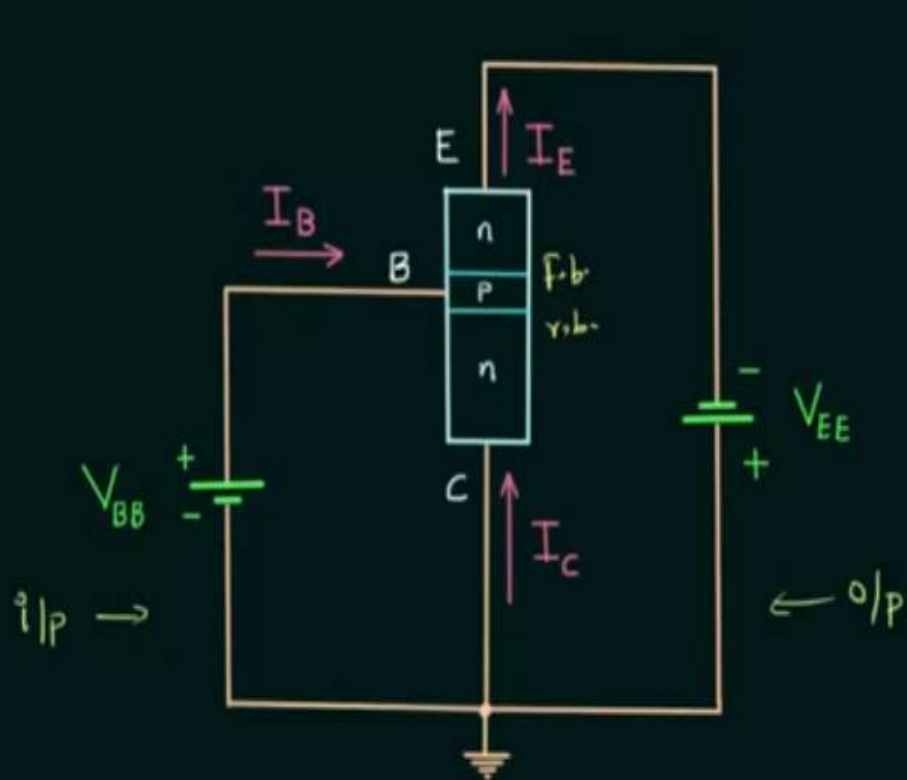Common-Collector Configuration of Transistor



I_E vs V_{CE} for various levels
of I_B

The common-collector configuration is used for IMPEDANCE MATCHING, because of high i/p impedance and low o/p impedance.



$\underline{I_C}$
 $\underline{I_E}$ vs $\underline{V_{CE}}$ for various levels of $\underline{I_B}$

imp

o/p ch. of CE \equiv o/p ch. of CC

$$I_C = \alpha I_E$$

$$\alpha = 0.95 - 0.98 \approx 1$$

$$I_C \approx I_E$$



$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$I_E = I_C + I_B \quad \text{--- ①}$$

$$\underline{I_C} = \alpha I_E + I_{CBO} \quad \text{--- ②}$$

I_E
 I_B

$$I_E = \alpha I_E + I_{CBO} + I_B$$

$$\underline{(1-\alpha) I_E} = I_B + I_{CBO}$$

α, β, γ

$$I_E = \left(\frac{1}{1-\alpha} \right) I_B + \left(\frac{1}{1-\alpha} \right) I_{CBO}$$

$$\boxed{I_E = \gamma I_B + \gamma I_{CBO}}$$