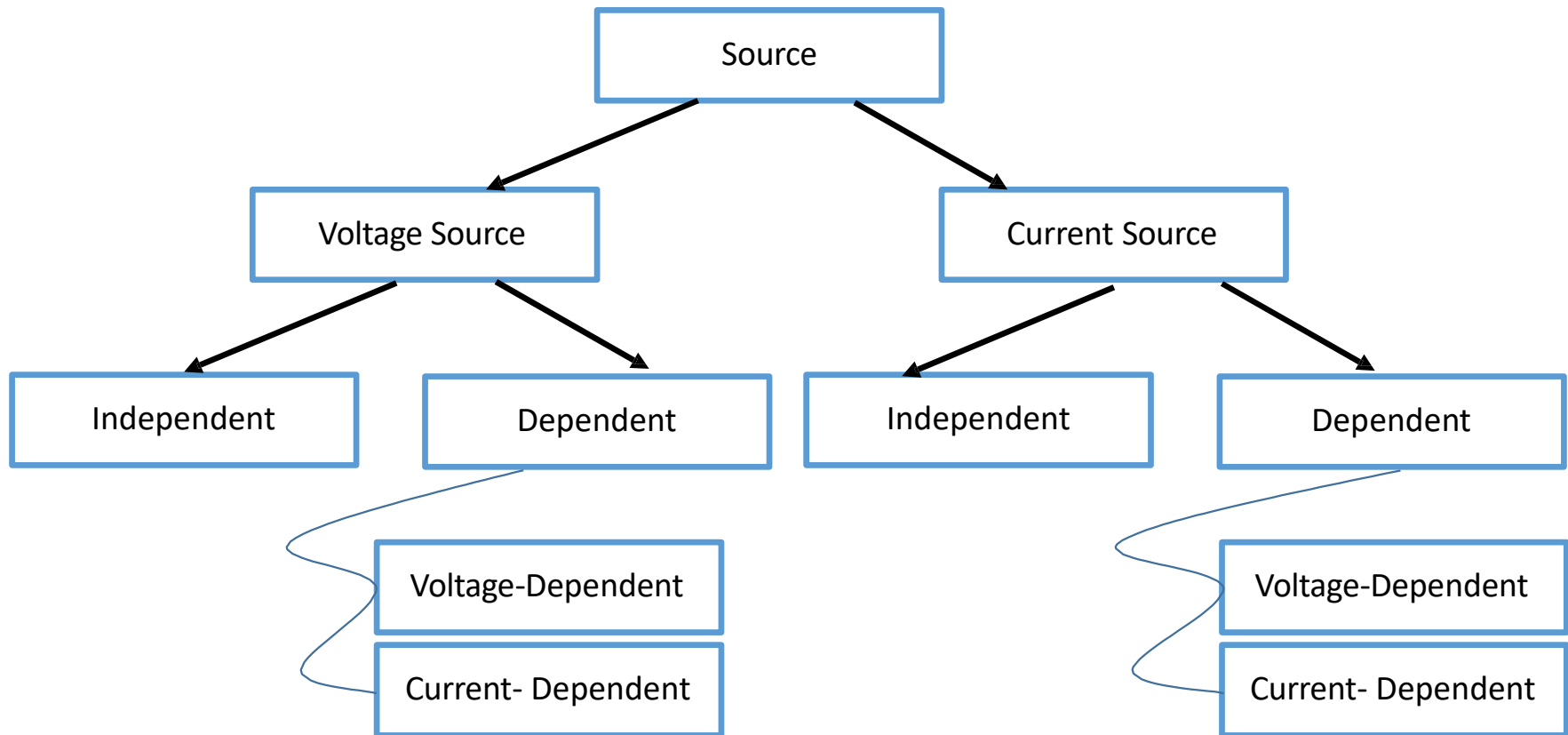


# UNIT 1: DC CIRCUITS

Lecture 4 & 5

# Energy Sources




# Independent and Dependent Sources


- **Independent sources** are those which **does not depend on any other quantity** in the circuit. They are two terminal devices and have a **constant value**, i.e. the voltage across the two terminals remains constant **irrespective of all circuit conditions**. The Independent sources are represented by a **circular shape**.
- **Dependent or Controlled** sources are those whose **output voltage or current is NOT fixed** but depends on the voltage or current in **another part** of the circuit. When the strength of voltage or current changes in the source for any change in the **connected network**, they are called dependent sources. The dependent sources are represented by a **diamond shape**.

# Independent and Dependent Sources

- Independent

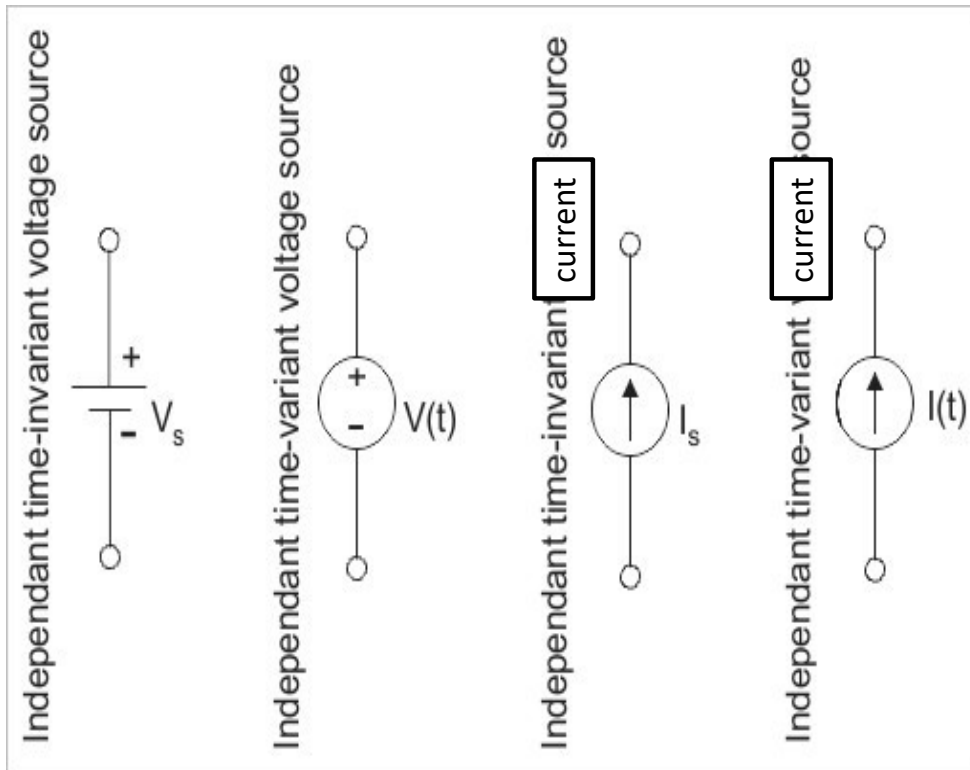

- Dependent

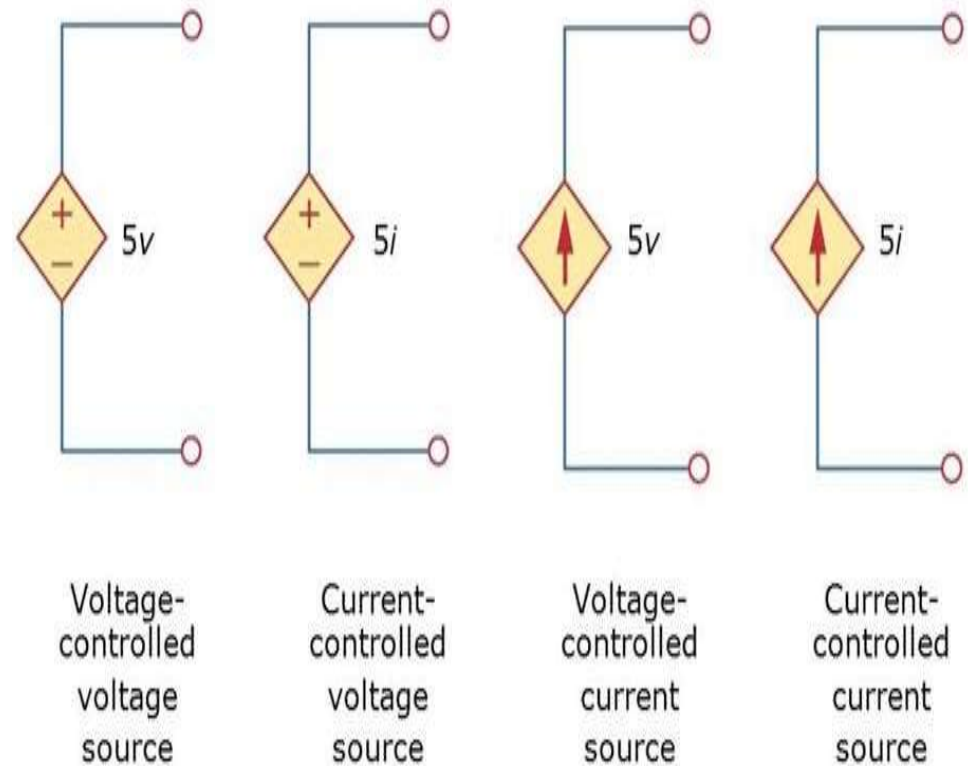

# Ideal and Practical Voltage Source

- Ideal source is one where internal resistance does NOT exist.

## NOTE:

1. For a voltage source, internal resistance must be ZERO.
  2. For a current source, internal resistance must be INFINITY.
- Practical source is one where internal resistance is present.

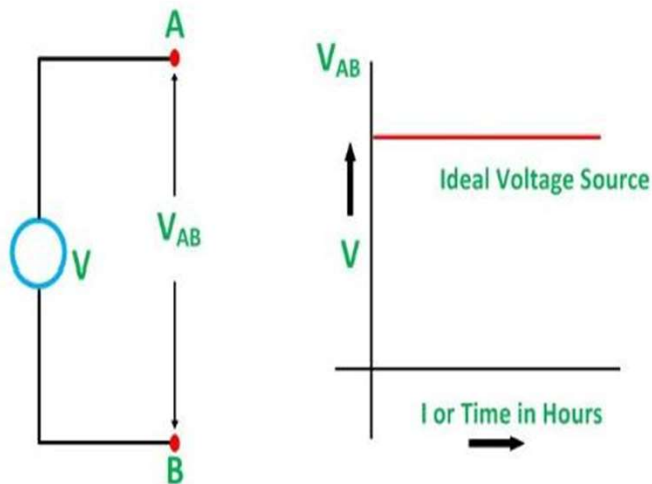


Figure A

Circuit Globe

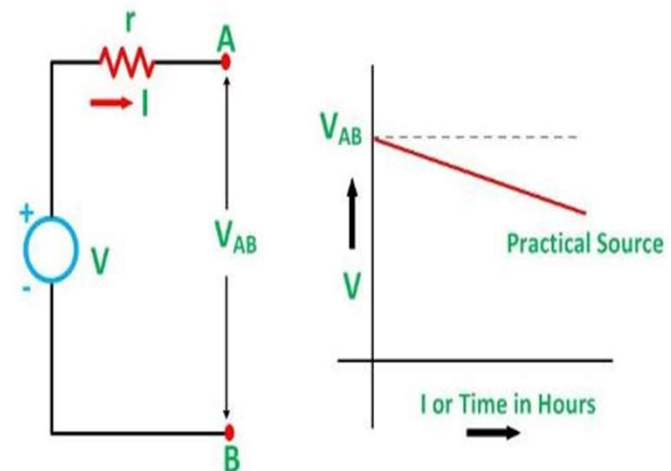


Figure B

Circuit Globe

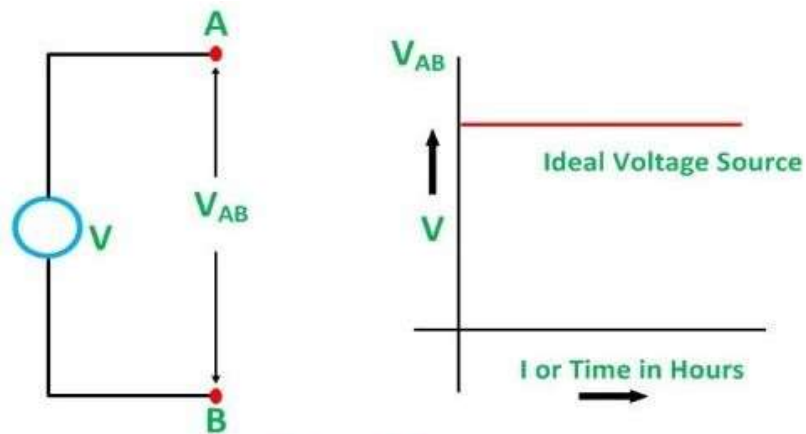


Figure A

Circuit Globe

The figure B shown below gives the circuit diagram and characteristics of Practical Voltage Source

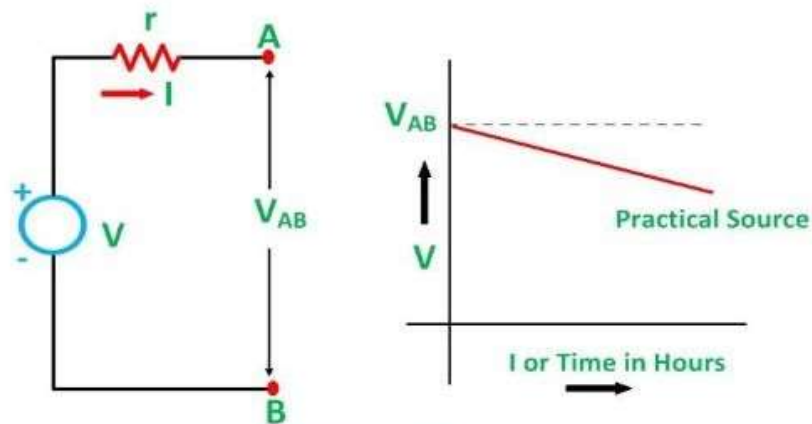


Figure B

Circuit Globe

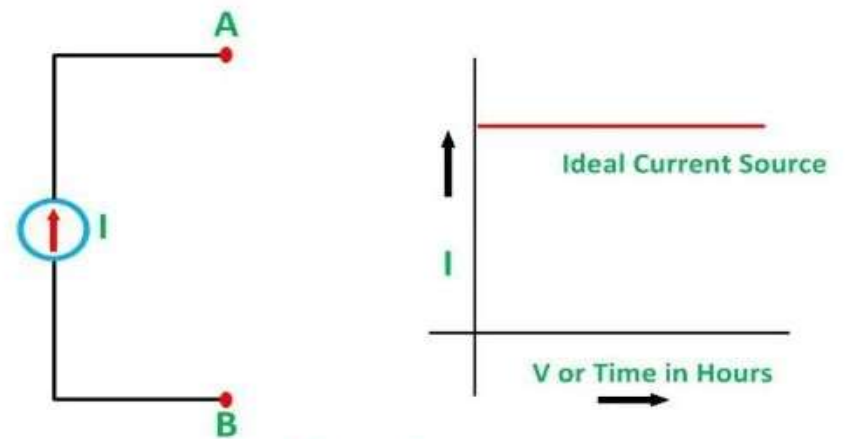


Figure C

Circuit Globe

Figure D shown below shows the characteristics of Practical Current Source.

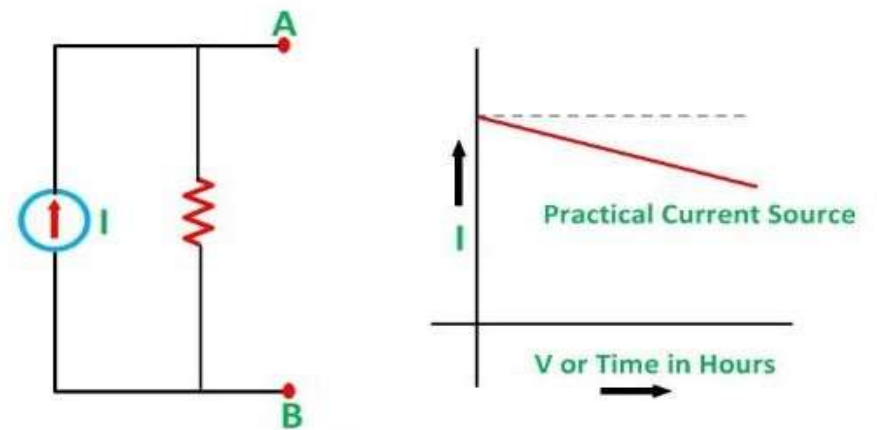



Figure D

Circuit Globe

# Source transformation

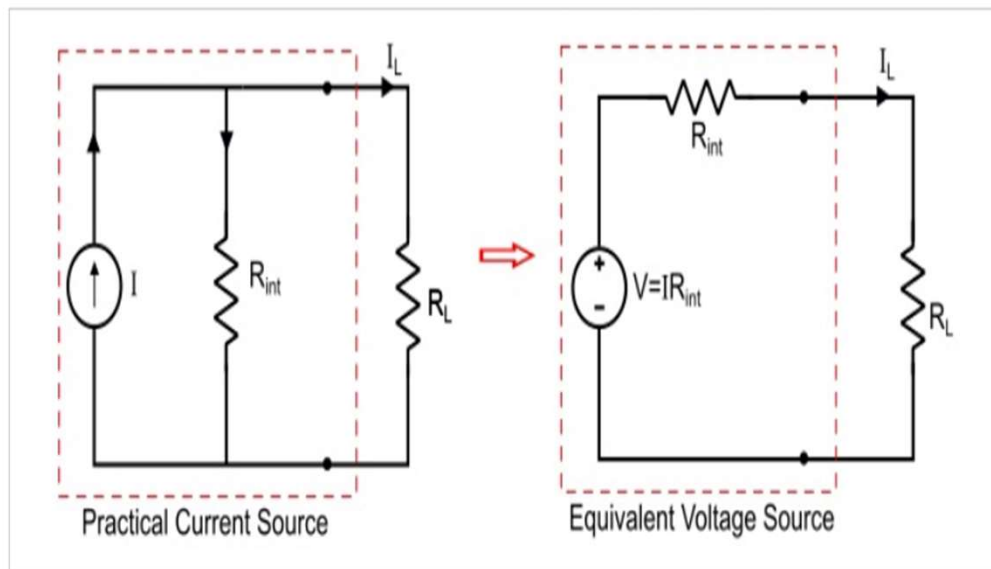
## Current to Voltage Source Transformation

Consider a practical current source of constant current  $I$  amperes with a parallel internal resistance  $R_{int}$ , it can be converted into an equivalent voltage source as follows.


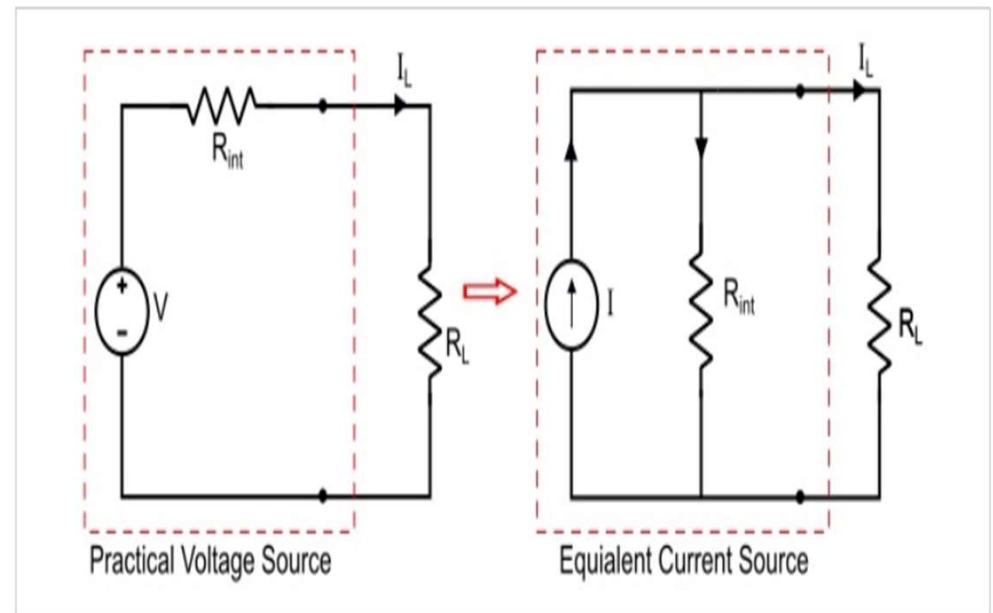
## Voltage to Current Source Transformation

Consider a practical voltage of  $V$  volts having a series internal resistance  $R_{int}$  ohms. A load resistance of  $R_L$  ohms is connected across the load terminals.



## Source transformation

### Numerical Example - 1

Convert a voltage source of 24 V having a series internal resistance of  $2\ \Omega$  into an equivalent current source.




## Source transformation

### Numerical Example - 1

Convert a voltage source of 24 V having a series internal resistance of 2  $\Omega$  into an equivalent current source.

Solution

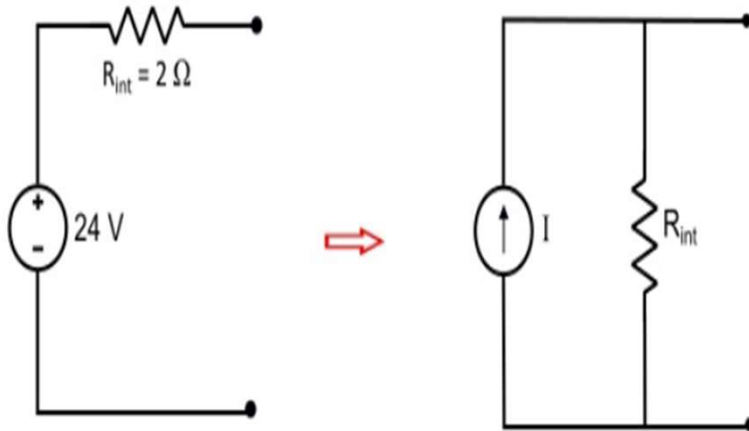

Here, the source current of equivalent current source is

$$I = \frac{V}{R_{int}} = \frac{24}{2} = 12 \text{ A}$$


The internal resistance  $R_{int}$  of the equivalent current source has the same value as the original voltage source, thus

$$R_{int} = 2 \Omega$$

## QUICK QUIZ (Poll 3)

Identify the type of dependent source used in the network:

- A. VCVS
- B. CCCS
- C. VCCS
- D. CCVS

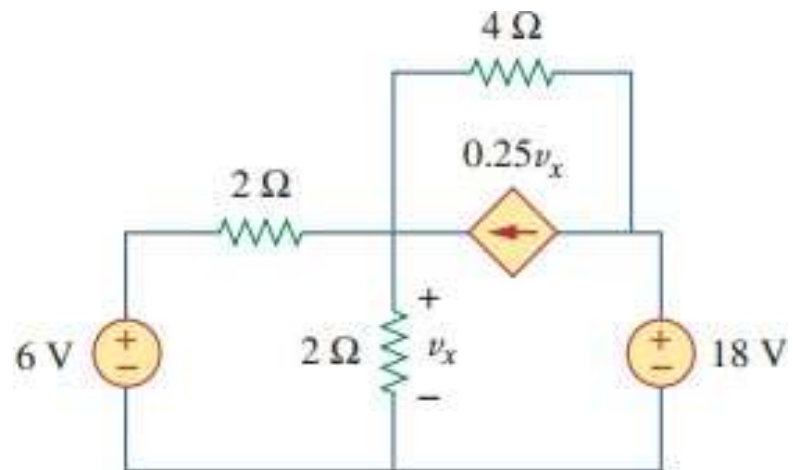

# Nodal Analysis

- Nodal analysis provides a general procedure for analyzing circuits using node voltages as the circuit variables.
- Choosing node voltages instead of element voltages as circuit variables is convenient and it *reduces the number of equations.* (one must solve simultaneously)
- Applicable to nodes only.
- It is used to find the unknown node voltages.
- This Method is Application of KCL+ Ohm's Law Only.

**There are two types of nodes in nodal analysis:**

- Non-reference node
- Reference node (Ground or datum node)

**Node:** The common point where two or more elements are connected.

✓ principal node -

**Procedure:** 1) Identify the total number of nodes.

2) Assign the voltage at each node. One node is taken as reference node (datum).

3) Develop the KCL equation for each non-reference node.

4) Solve the KCL equations to get the node voltage.

↓  
pot. = 0V

# Steps to Determine Node Voltages

1. Select **one** nodes out of 'n' node as the **reference node**. Assign voltages to the **remaining nodes**. The voltages are referenced with respect to the reference node.
2. **Apply KCL** to each of the non-reference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. **Solve the resulting simultaneous equations** to obtain the unknown node voltages.

- The number of non-reference nodes is **equal** to the number of **independent equations** that we have to derive.
- Current flows from a **higher potential to a lower potential** in a resistor



$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$


## QUICK QUIZ

For “N” number of nodes, the number of non-reference nodes is equal to:

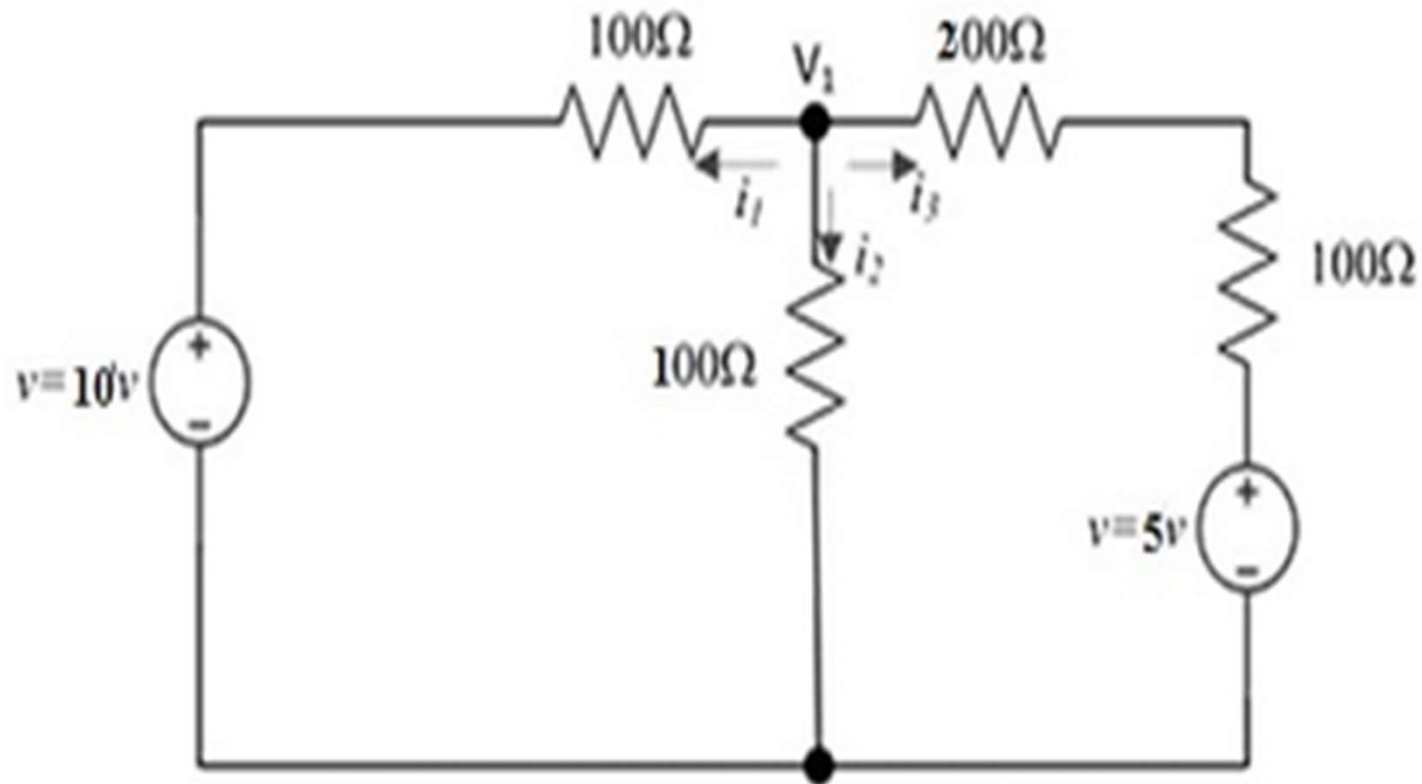- A.  $N + 1$
- B.  $N - 1$
- C.  $2N$
- D.  $2N - 1$



Find the node voltage 'V1' by applying nodal analysis in the following circuit.



$$i_1 + i_2 + i_3 = 0$$

$$(V_1 - 10/100) + (V_1/100) + (V_1 - 5/200 + 100)$$

$$(V_1/100 - 10/100) + V_1/100 + (V_1 - 5/200 + 100)$$

$$(V_1/100 + V_1/100 + V_1/300) - (10/100) - (5/300)$$

$$V_1(1/100 + 1/100 + 1/300) - (10/100) - (5/300)$$

$$(3 + 3 + 1/300)V_1 = (30/300 + 5/300)$$

$$(7/300)V_1 = 30 + 5/300$$

$$V_1 = (35/300) \times (300/7)$$

$$V_1 = (35/7)$$

$$V_1 = 5V$$


## QUICK QUIZ

Nodal analysis, which is based on KCL is used to find unknown:

- A. current
- B. voltage


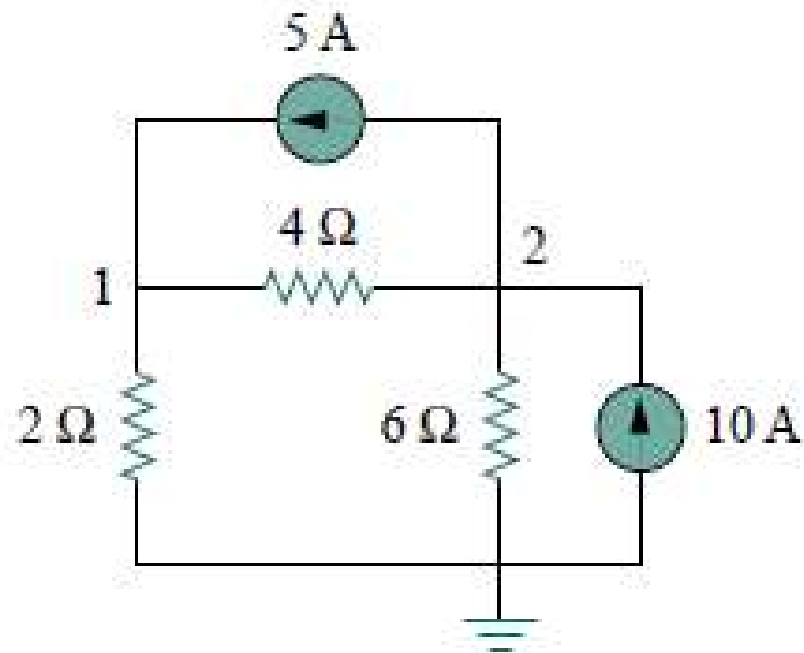
# Example 1

- Obtain the node voltages in the given circuit?


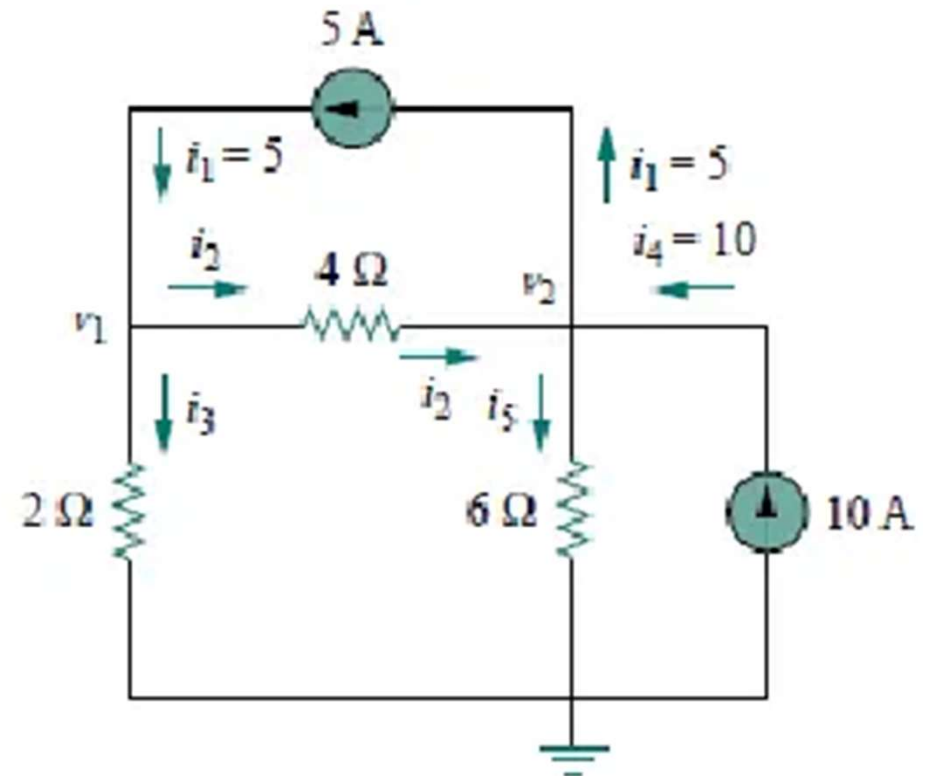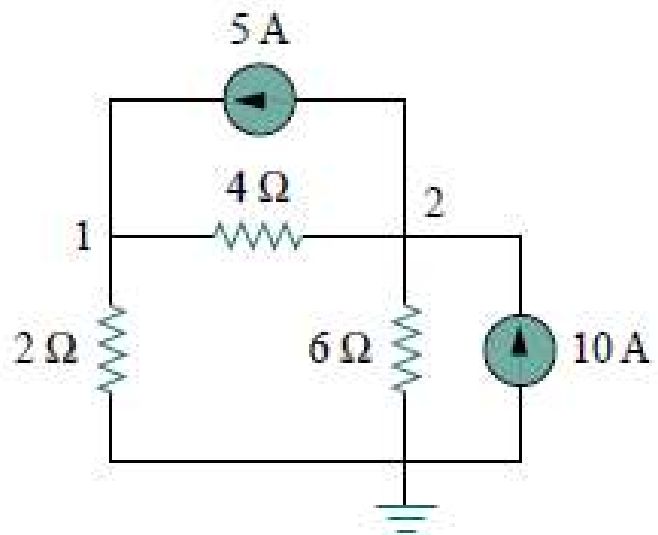
# Example 1

- Obtain the node voltages in the given circuit?



$$i_1 = i_2 + i_3$$

$$5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

Multiplying each term in the last equation by 4, we obtain

$$20 = v_1 - v_2 + 2v_1$$

or

$$3v_1 - v_2 = 20 \quad (1)$$

At node 2, we do the same thing and get

$$i_2 + i_4 = i_1 + i_5$$

$$\frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2 - 0}{6}$$

Multiplying each term by 12 results in

$$3v_1 - 3v_2 + 120 = 60 + 2v_2$$

or

$$-3v_1 + 5v_2 = 60 \quad (2)$$

Using the elimination technique, we add Eqs. (1) and (2).

$$4v_2 = 80 \Rightarrow v_2 = 20V$$

Substituting  $v_2 = 20$  in Eq. (1) gives

$$3v_1 - 20 = 20 \Rightarrow 3v_1 = 40$$

$$v_1 = 13.33V$$

# Mesh Analysis

- Mesh analysis provides another general procedure for analyzing circuits, using **mesh currents** as the circuit variables.
- It is based on **KVL**.

## RECALL!



- **LOOP**: A loop is **any closed path going through circuit elements**.
- **MESH**: A mesh is a loop that does not contain any other loop within it.
- Mesh analysis is not quite as general as nodal analysis because it is only applicable to a circuit that is **planar**.
- **PLANAR CIRCUIT**: A planar circuit is one that can be drawn in a plane **with no branches crossing one another**; otherwise it is nonplanar.

# Steps to Determine Mesh Currents

1. Assign mesh currents to 'n' meshes
2. Apply **KVL** to each of the '**n**' meshes.
3. **Solve the resulting 'n' simultaneous equations** to obtain the unknown mesh currents.





# Examples of Planar Circuits

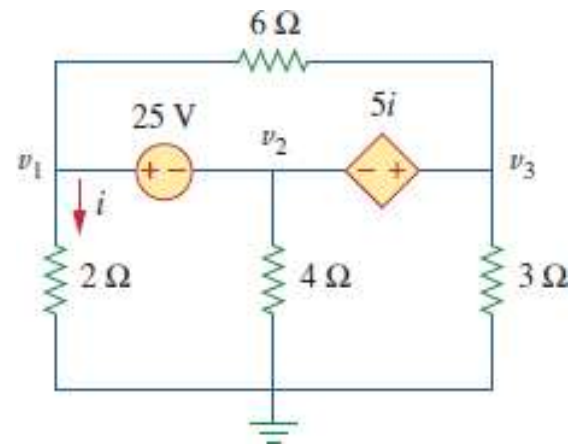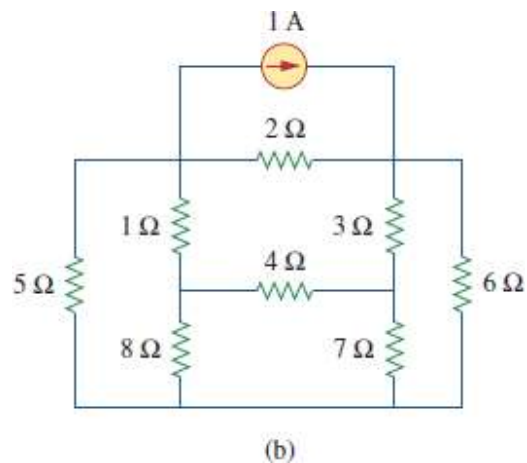

NOTE: A **mesh** is a loop which does not contain any other loops within it.

Mesh Analysis can be applied to meshes only inside the circuit, **Not to LOOP**.

# Examples of Non-Planar Circuits

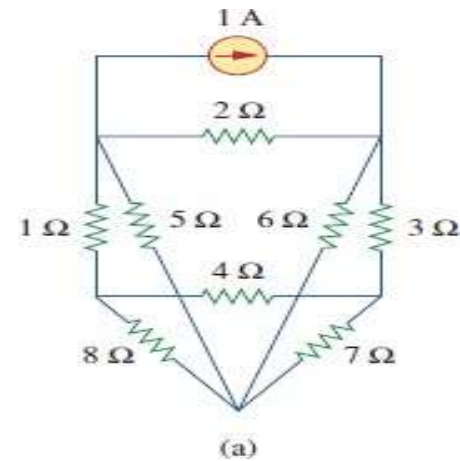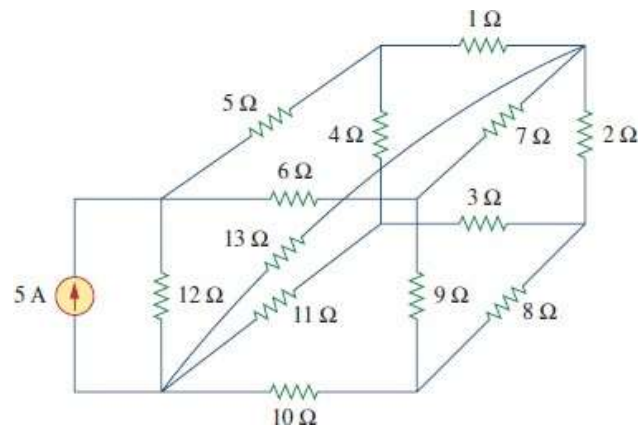

## QUICK QUIZ

Mesh Analysis to applicable to\_\_\_\_\_type networks.:

- A. Planar and Loop
- B. Non planar and mesh
- C. Planar and mesh
- D. Non planar and Loop


## QUICK QUIZ

Mesh analysis, which is based on KVL is used to find unknown:

- A. current
- B. voltage
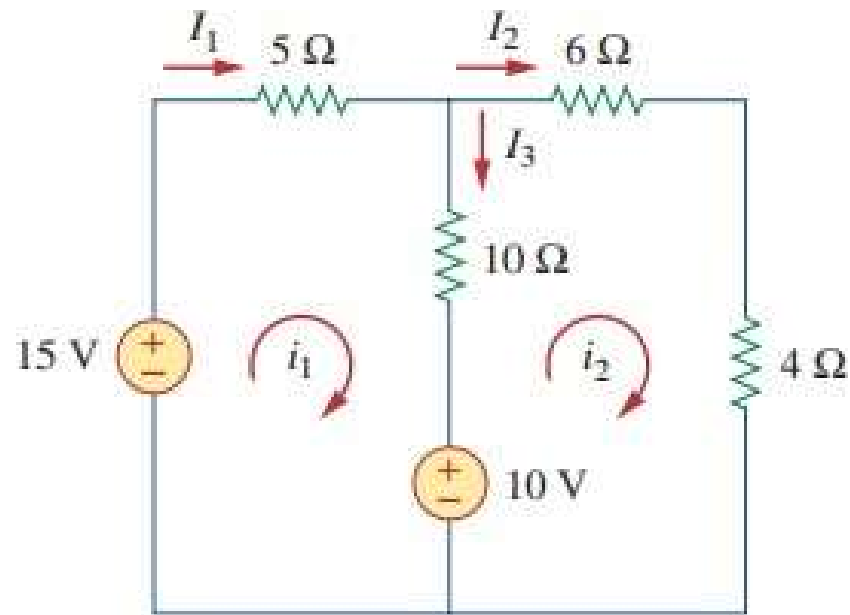
# Example 1

- Obtain the mesh currents in the given circuit?



## Example 1

$$+15 - 5I_1 - 10(I_1 - I_2) - 10 = 0$$

$$+15 - 5I_1 - 10I_1 + 10I_2 - 10 = 0$$

$$15I_1 - 10I_2 = 5 \quad \text{--- (1)}$$

$$-6I_2 - 4I_2 + 10 + 10(I_1 - I_2) = 0$$

$$-10I_1 + 20I_2 = 10 \quad \text{--- (2)}$$

$$\Rightarrow I_1 = I_2 = 1A$$

$$\text{as } I_1 = I_2 + I_3$$

$$I_3 = 0$$

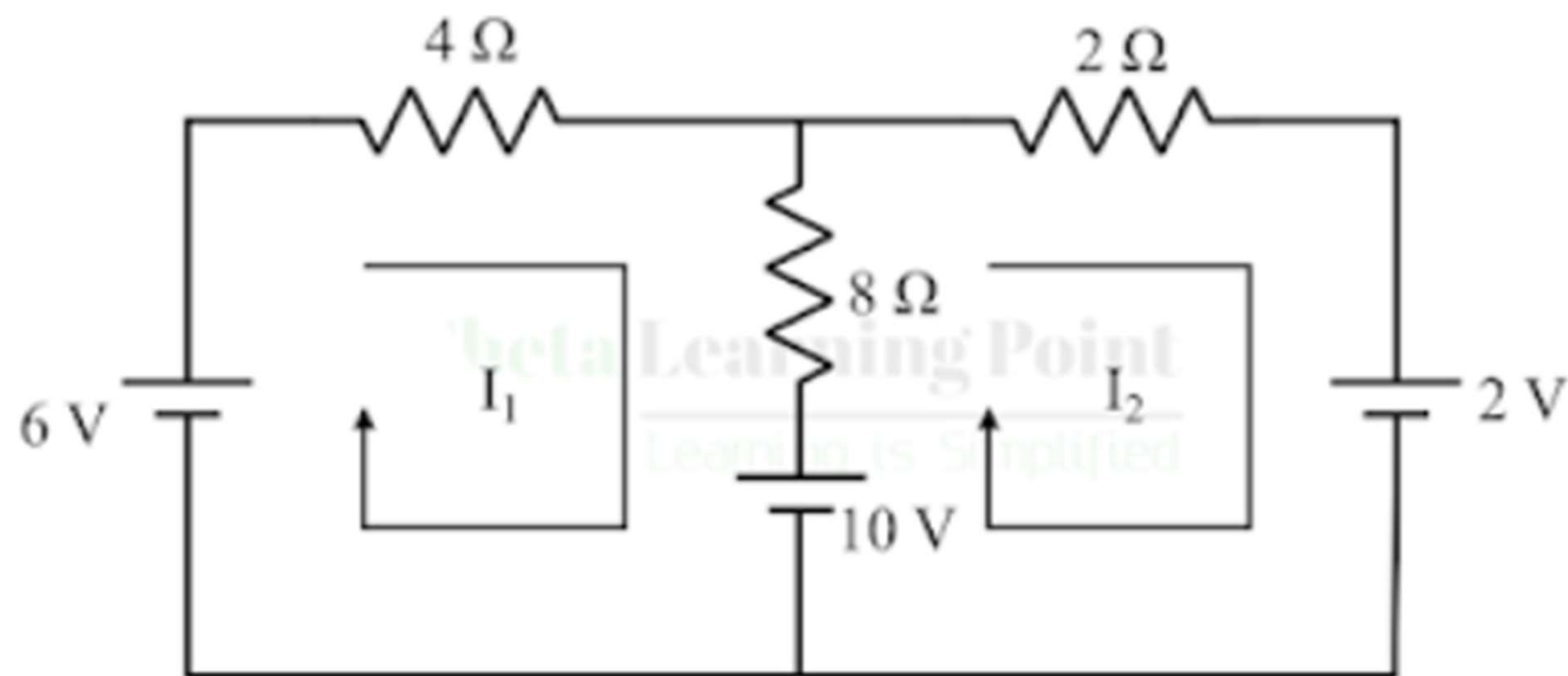


Figure 1 - Mesh Analysis with Voltage Sources Only

The KVL equation for mesh 1 is,

$$\begin{aligned}6 - 4I_1 - 8(I_1 - I_2) - 10 &= 0 \\ \Rightarrow -12I_1 + 8I_2 &= 4 \quad \dots(1)\end{aligned}$$

The KVL equation for mesh 2 is,

$$\begin{aligned}-2 + 10 - 8(I_2 - I_1) - 2I_2 &= 0 \\ \Rightarrow 8I_1 - 10I_2 &= -8 \quad \dots(2)\end{aligned}$$

By rearranging equation (2), we get,

$$I_1 = \frac{10I_2 - 8}{8} \quad \dots(3)$$

On substituting the value of current  $I_1$  from equation (3) into equation (1), we get,

$$-12\left(\frac{10I_2 - 8}{8}\right) + 8I_2 = 4$$


On solving this equation, we get,

$$I_2 = \frac{8}{7} \text{ A}$$

Also, by putting this value of current  $I_2$  into equation (3), we get,
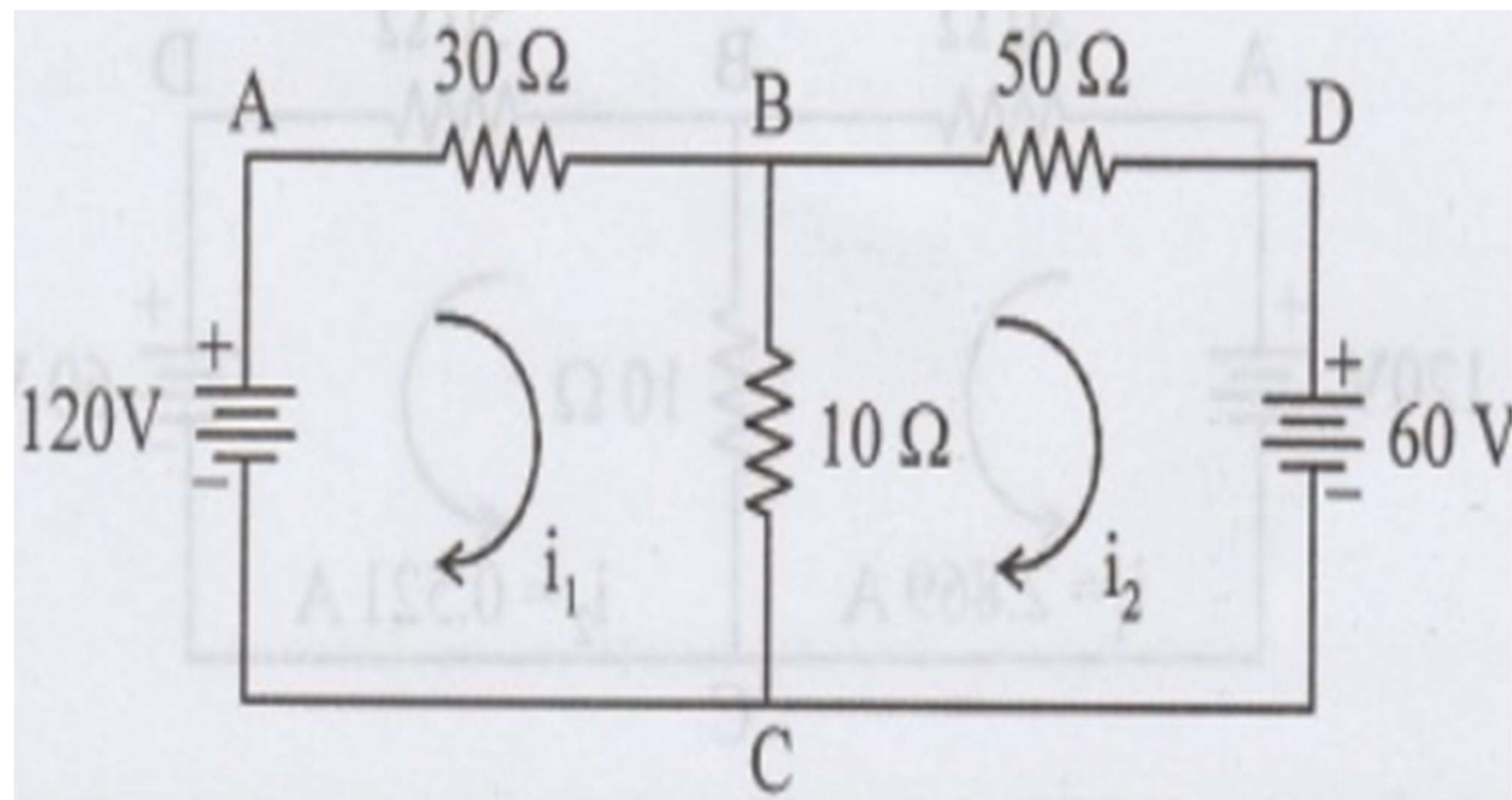
$$\begin{aligned}I_1 &= \frac{\left(10 \times \frac{8}{7}\right) - 8}{8} \\ \therefore I_1 &= \frac{3}{7} \text{ A}\end{aligned}$$





$$-30i_1 - 10(i_1 - i_2) + 120 = 0$$

$$-30i_1 - 10i_1 + 10i_2 + 120 = 0$$

$$-40i_1 + 10i_2 + 120 = 0$$

$$120 = 40i_1 - 10i_2 \dots\dots\dots(1)$$

Mesh BDCB

$$-50i_2 - 60 - 10(i_2 - i_1) = 0$$

$$-50i_2 - 10i_2 + 10i_1 - 60 = 0$$

$$-60i_2 + 10i_1 - 60 = 0$$

$$-60 = -10i_1 + 60i_2 \dots\dots\dots(2)$$

Multiplying equ (2) by 4 and adding the equ (2) in to equ (1)

$$120 = 40i_1 - 10i_2$$

$$-240 = -40i_1 + 240i_2$$

---

$$-120 = 230i_2$$

$$i_2 = -120/230 = -0.521 \text{ A}$$


The  $i_1$  value is substituted in equ (1)

$$40 i_1 - 10 (-0.521) = 120$$

$$40 i_1 + 5.21 = 120$$

$$40 i_1 = 114.79$$

$$i_1 = 114.79/40 = 2.869 \text{ A}$$

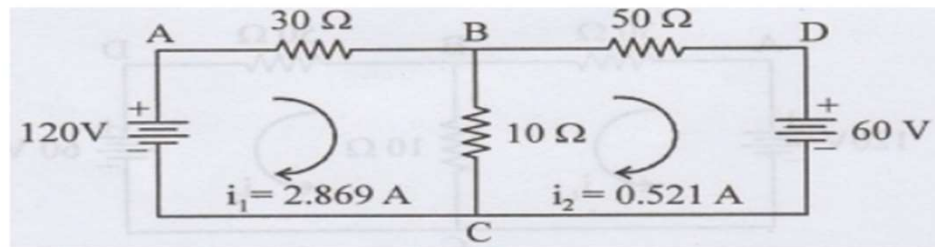

The actual direction of flow of mesh currents is shown in above fig

The mesh currents  $i_1 = 2.869 \text{ A}$

$$i_2 = 0.521 \text{ A}$$


Current in branch CAB is

$$i_1 = 2.869 \text{ A}$$

Current in branch CDB is

$$i_2 = 0.521 \text{ A}$$

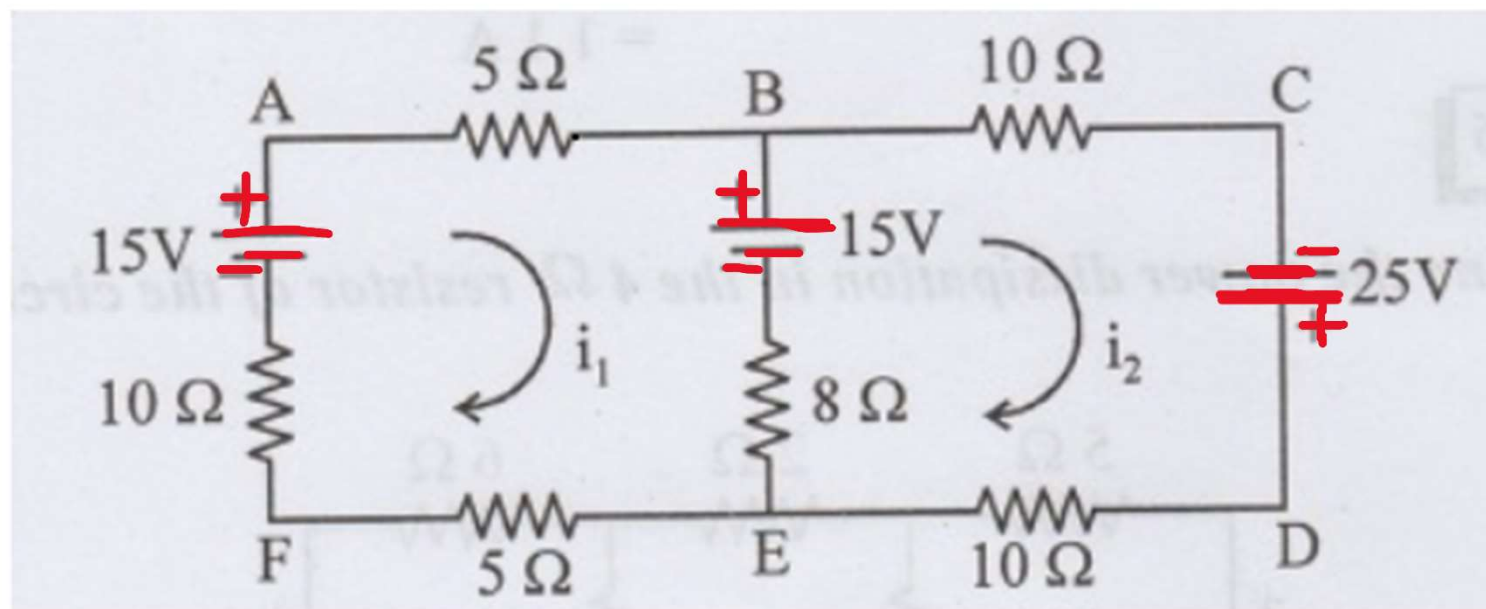**Find the current in the  $8\ \Omega$  resistor in the circuit shown in figure.**



$$-10 (i_1) + 15 - 5 i_1 - 15 - 8 (i_1 - i_2) - 5 i_1 = 0$$

$$-10 i_1 - 5 i_1 - 8 i_1 + 8 i_2 - 5 i_1 = 0$$

$$-28 i_1 + 8 i_2 = 0$$

$$-28 i_1 = -8 i_2$$

$$i_2 = 28 i_1 / 8 = 3.5 i_1$$

For mesh BCDEB

$$-10 i_2 + 25 - 10 i_2 - 8 (i_2 - i_1) + 15 = 0$$

$$-10 i_2 + 25 - 10 i_2 - 8 i_2 + 8 i_1 + 15 = 0$$

$$-28 i_2 + 8 i_1 + 40 = 0$$

$$40 = 28 i_2 - 8 i_1 \dots\dots\dots(2)$$

Sub  $i_2$  in equ (2)

$$40 = 28 (3.5 i_1) - 8 i_1$$

$$40 = 98 i_1 - 8 i_1$$

$$40 = 90 i_1$$

$$i_1 = 40 / 90 = 0.44 \text{ A}$$

$$i_2 = 3.5 (0.44)$$