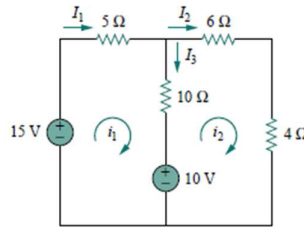


## Tutorial Sheet-2 (Unit-1)

Q1. For the circuit in Fig., find the branch currents  $I_1$ ,  $I_2$ , and  $I_3$  using mesh analysis.



Ans1:  $i_1 = i_2 = 1 \text{ A}$

We first obtain the mesh currents using KVL. For mesh 1,

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

or

$$3i_1 - 2i_2 = 1$$


For mesh 2,

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

or

$$i_1 = 2i_2 - 1$$

Q2. Find current through  $4\Omega$  resistance.

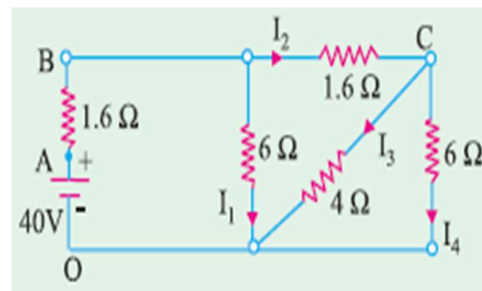

Ans2:

**Solution.** Simplifying the series-parallel combinations, and solving the circuit, the source current is 10 amp. With respect to 0,  $V_A = 40$ ,  $V_B = 40 - 16 = 24$  volts.

$$I_1 = 4 \text{ amp, hence } I_2 = 6 \text{ amp}$$

$$V_C = V_B - I_2 \times 1.6 = 24 - 9.6 = 14.4 \text{ volts}$$

$$I_3 = 14.4/4 = 3.6 \text{ amp, which is the required answer. Further } I_4 = 24 \text{ amp.}$$

**Q3:** Using Node voltage method, find the current in the  $3\Omega$  resistance for the network.


**Ans 3:**

**Solution.** As shown in the figure node 2 has been taken as the reference node. We will now find the value of node voltage  $V_1$ . Using the technique developed in Art. 2.10, we get

$$V_1 \left( \frac{1}{5} + \frac{1}{2} + \frac{1}{2} \right) - \frac{4}{2} - \left( \frac{4+2}{5} \right) = 0$$


The reason for adding the two battery voltages of 2 V and 4 V is because they are connected in additive series. Simplifying above, we get  $V_1 = 8/3$  V. The current flowing through the  $3\Omega$

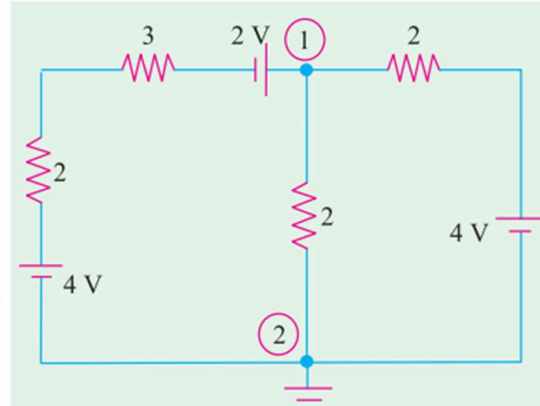resistance towards node 1 is  $= \frac{6 - (8/3)}{(3+2)} = \frac{2}{3}$  A



**Q4.**

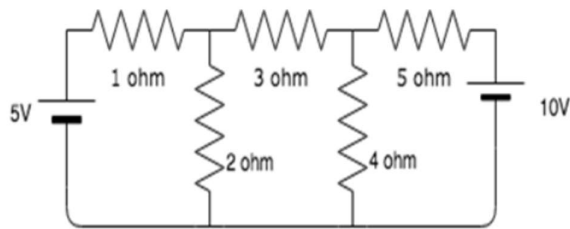1. Find the value of the currents  $I_1$ ,  $I_2$  and  $I_3$  flowing clockwise in the first, second and third mesh respectively.



**Ans.**

Explanation: The three mesh equations are:

$$-3I_1 + 2I_2 - 5 = 0$$


$$2I_1 - 9I_2 + 4I_3 = 0$$

$$4I_2 - 9I_3 - 10 = 0$$

Solving the equations, we get  $I_1 = 1.54$  A,  $I_2 = -0.189$  and  $I_3 = -1.195$  A.

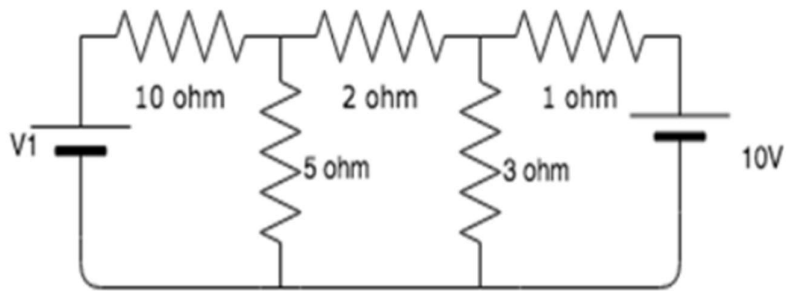**Q5.**

Find the value of  $V_1$  if the current through the 1 ohm resistor = 0A.



**Ans.**

Explanation: Taking  $I_1$ ,  $I_2$  and  $I_3$  as the currents in the three meshes and taking  $I_3=0$  since it is the current across the 1 ohm resistor, the three mesh equations are:


$$15I_1 - 5I_2 = V_1$$

$$-5I_1 + 10I_2 = 0$$

$$3I_2 = 10$$

Solving these equations simultaneously we get  $V_1 = 83.33V$ .

**Q6.**

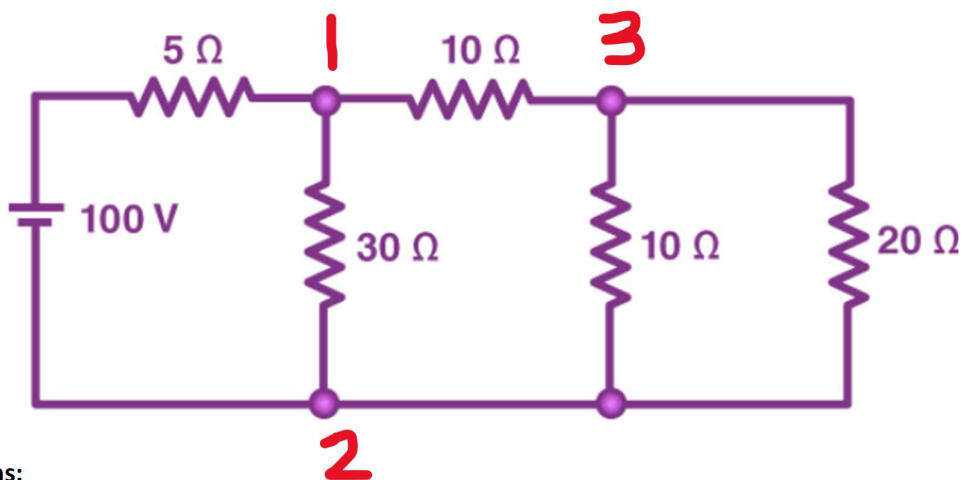

**Ans:**

Let node 2 be the reference node, and this node's voltage will be zero

Using Kirchhoff's current law at each node, we get

$$\frac{V_1}{30} + \frac{V_1 - 100}{5} + \frac{V_1 - V_3}{10} = 0$$

(eq.1)

This is a result of KCL at node 1

$$\frac{V_3 - V_1}{10} + \frac{V_3}{10} + \frac{V_3}{20} = 0$$

(eq.2)

This is a result of KCL at node 3

$$\left(\frac{1}{30} + \frac{1}{5} + \frac{1}{10}\right)V_1 - \left(\frac{1}{10}\right)V_3 = \frac{100}{5}$$

$$-\left(\frac{1}{10}\right)V_1 + \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{20}\right)V_3 = 0$$


Solving the above equations we get

$$V_1 = 68.2\text{v}$$

$$V_3 = 27.3\text{v}$$

### Assignment for H.W.

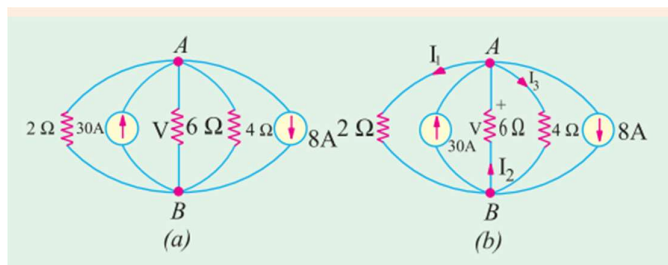*Q. 1 Using Kirchhoff's Current Law and Ohm's Law, find the magnitude and polarity of voltage  $V$  in Fig. 2.9 (a). Directions of the two current sources are as shown.*



**Solution.** Let us arbitrarily choose the directions of  $I_1$ ,  $I_2$  and  $I_3$  and polarity of  $V$  as shown in Fig. 2.9.(b). We will use the sign convention for currents as given in Art. 2.3. Applying KCL to node  $A$ , we have

$$-I_1 + 30 + I_2 - I_3 - 8 = 0$$

or  $I_1 - I_2 + I_3 = 22 \quad \dots(i)$

Applying Ohm's law to the three resistive branches in Fig. 2.9 (b), we have

$$I_1 = \frac{V}{2}, I_3 = \frac{V}{4}, I_2 = -\frac{V}{6} \quad (\text{Please note the -ve sign.})$$

Substituting these values in (i) above, we get


$$\frac{V}{2} - \left(-\frac{V}{6}\right) + \frac{V}{4} = 22 \quad \text{or} \quad V = 24 \text{ V}$$

$$\therefore I_1 = V/2 = 24/2 = 12 \text{ A}, I_2 = -24/6 = -4 \text{ A}, I_3 = 24/4 = 6 \text{ A}$$

The negative sign of  $I_2$  indicates that actual direction of its flow is opposite to that shown in Fig. (b). Actually,  $I_2$  flows from  $A$  to  $B$  and not from  $B$  to  $A$  as shown.

Incidentally, it may be noted that all currents are outgoing except 30A which is an incoming current.

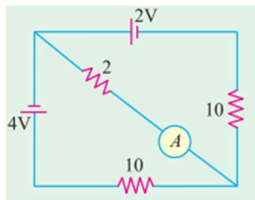Q. 2 Find the ammeter current in Fig. by using loop analysis



Ans: 1.7 A

### MCQs(Gate Question)

1. Kirchhoff's Current Law (KCL) is based on the principle of:

- |                                  |                             |
|----------------------------------|-----------------------------|
| a) Conservation of energy        | b) Conservation of momentum |
| c) <b>Conservation of charge</b> | d) Conservation of mass     |

2. In a circuit, the sum of all voltages around a closed loop is zero. This statement is based on:

- |                                  |                                         |
|----------------------------------|-----------------------------------------|
| a) Ohm's Law                     | b) <b>Kirchhoff's Voltage Law (KVL)</b> |
| c) Kirchhoff's Current Law (KCL) | d) Norton's Theorem                     |

3. What is the equivalent resistance of a network if a 12V battery produces a current of 3A through it?

- a)  $4\Omega$                       b)  $6\Omega$                       c)  $3\Omega$                       d)  $2\Omega$

4. Kirchhoff's Voltage Law (KVL) is based on the principle of:

- a) Conservation of charge                      b) **Conservation of energy**  
c) Conservation of momentum                      d) Conservation of mass

5. Thevenin's Theorem states that any linear electrical network with voltage and current sources and resistances can be replaced at terminals A-B with:

- a) A single current source and a parallel resistance  
b) **A single voltage source and a series resistance**  
c) A single resistance only  
d) None of the above

6. To find the Thevenin equivalent voltage ( $V_{th}$ ), you:

- a) Short all voltage sources and open all current sources  
b) Open all voltage sources and short all current sources  
c) **Measure the open-circuit voltage at the terminals**  
d) Measure the short-circuit current at the terminals

7. Norton's Theorem is used to:

- a) Transform a network of voltage sources into a current source  
b) Transform a network of current sources into a voltage source  
c) Find the equivalent voltage and resistance  
d) **Find the equivalent current and resistance**

8. In a parallel circuit, applying Kirchhoff's Current Law (KCL) at a node means:

- a) Summing the voltages at the node to zero  
b) **Summing the currents entering and leaving the node to zero**  
c) Summing the resistances at the node to zero  
d) Summing the power at the node to zero

9. To find the Norton equivalent current ( $I_n$ ), you:

- a) Short all voltage sources and open all current sources  
b) Open all voltage sources and short all current sources  
c) Measure the open-circuit voltage at the terminals  
d) **Measure the short-circuit current at the terminals**

10. Which theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source in parallel with a resistor?

- a) Thevenin's Theorem                      b) **Norton's Theorem**  
c) Superposition Theorem                      d) Millman's Theorem

11. In applying Kirchhoff's Voltage Law (KVL) around a loop, we consider the sum of:

- a) Voltages in any direction to be zero
- b) Voltage drops to be zero
- c) Voltage sources to be zero
- d) Voltages around the loop to be zero

12. When determining the Thevenin equivalent resistance, the independent sources are:

- a) Short-circuited for voltage sources and open-circuited for current sources
- b) Open-circuited for voltage sources and short-circuited for current sources
- c) Removed from the circuit
- d) Not considered

13. Kirchhoff's Current Law (KCL) is applied to:

- a) Closed loops in a circuit
- b) Nodes in a circuit
- c) Series resistances in a circuit
- d) Parallel resistances in a circuit

14. For a given linear network, the Norton equivalent circuit consists of:

- a) A voltage source in series with a resistor
- b) A current source in parallel with a resistor
- c) A voltage source in parallel with a resistor
- d) A current source in series with a resistor

15. Thevenin's and Norton's Theorems are applicable to:

- a) Non-linear circuits
- b) Linear circuits
- c) Both linear and non-linear circuits
- d) AC circuits only

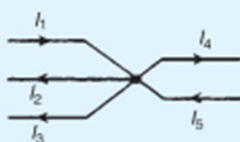


Figure 13.88

2. Which of the following statements is true?  
For the circuit shown in Fig. 13.89:
- $E_1 + E_2 + E_3 = Ir_1 + Ir_2 + Ir_3$
  - $E_2 + E_3 - E_1 - I(r_1 + r_2 + r_3) = 0$
  - $I(r_1 + r_2 + r_3) = E_1 - E_2 - E_3$
  - $E_2 + E_3 - E_1 = Ir_1 + Ir_2 + Ir_3$

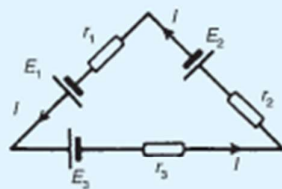


Figure 13.89

3. For the circuit shown in Fig. 13.90, the internal resistance  $r$  is given by:
- $\frac{I}{V - E}$
  - $\frac{V - E}{I}$
  - $\frac{I}{E - V}$
  - $\frac{E - V}{I}$

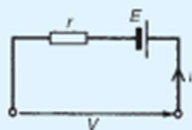


Figure 13.90

4. For the circuit shown in Fig. 13.91, voltage  $V$  is:
- 12 V
  - 2 V
  - 10 V
  - 0 V

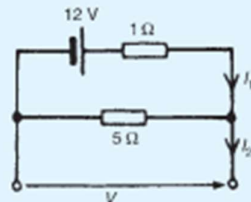


Figure 13.91

5. For the circuit shown in Fig. 13.91, current  $I_1$  is:
- 2 A
  - 14.4 A
  - 0.5 A
  - 0 A
6. For the circuit shown in Fig. 13.91, current  $I_2$  is:
- 2 A
  - 14.4 A
  - 0.5 A
  - 0 A
7. The equivalent resistance across terminals AB of Fig. 13.92 is:
- 9.31 Ω
  - 7.24 Ω
  - 10.0 Ω
  - 6.75 Ω

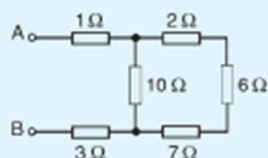


Figure 13.92

8. With reference to Fig. 13.93, which of the following statements is correct?
- $V_{PQ} = 2$  V
  - $V_{PQ} = 15$  V
  - When a load is connected between P and Q, current would flow from Q to P
  - $V_{PQ} = 20$  V

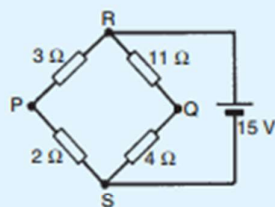


Figure 13.93

9. In Fig. 13.93, if the 15 V battery is replaced by a short-circuit, the equivalent resistance across terminals PQ is:
- 20 Ω
  - 4.20 Ω
  - 4.13 Ω
  - 4.29 Ω