

## Tutorial Sheet-3 (Unit-1)

Q 1. Find the average and effective values of voltage of sinusoidal waveform shown in Fig. 11.33.

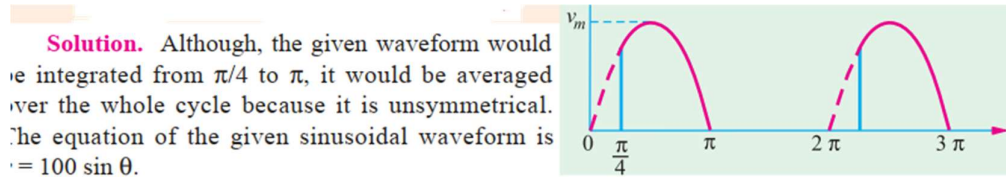



Fig. 11.33

$$\therefore V_{av} = \frac{1}{2\pi} \int_{\pi/4}^{\pi} 100 \sin \theta \, d\theta = \frac{100}{2\pi} \left[ -\cos \theta \right]_{\pi/4}^{\pi} = 27.2 \, \text{V}$$

$$V^2 = \frac{1}{2} \int_{\pi/4}^{\pi} 100^2 \sin^2 \theta \, d\theta = \frac{100^2}{4} \int_{\pi/4}^{\pi} (1 - \cos 2\theta) \, d\theta = \frac{100^2}{4} \left[ \theta - \frac{\sin 2\theta}{2} \right]_{\pi/4}^{\pi} = \frac{100^2}{4} \left[ \frac{\pi}{4} - \frac{1}{2} \right]$$

$$\therefore V = 47.7 \, \text{V}$$

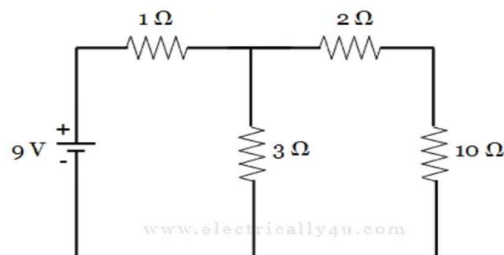Q2. Solve the given circuit to find the current through  $10 \, \Omega$  using Thevenin's Theorem.



**Ans.**

$$R_{TH} = 2 + \frac{1 * 3}{1 + 3} = 2.75 \, \Omega$$

By Ohm's law,


$$I = \frac{V}{R} = \frac{9}{4} = 2.25 \, \text{A}$$

Thus, the voltage across  $3 \, \Omega$  resistor (or Thevenin's voltage  $V_{TH}$ ) is given by,


$$V_{ab} = V_{TH} = I * R = 2.25 * 3 = 6.75 \, \text{V}$$

$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{6.75}{2.75 + 10} = 0.529 \, \text{A}$$

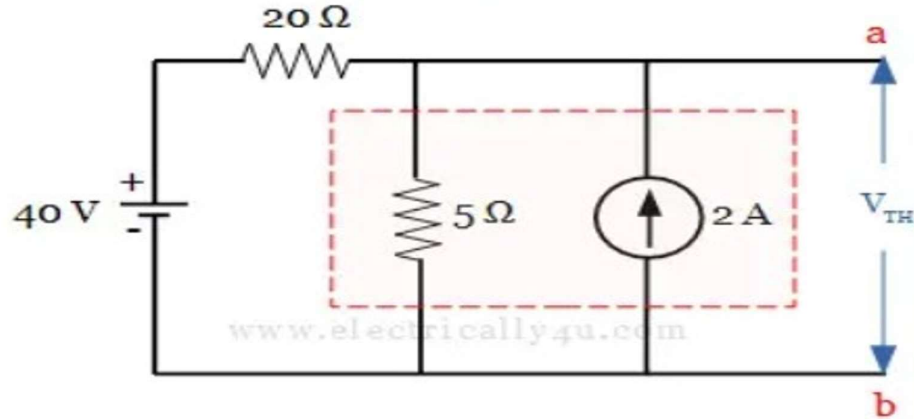**Q3. Solve the given circuit to find the current through  $15\ \Omega$  using Thevenin's Theorem.**



Ans.

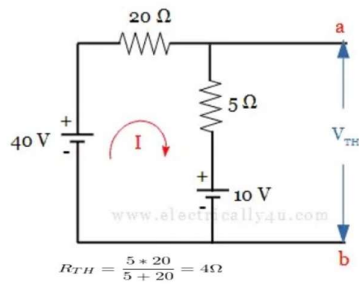

Let us apply Kirchoff's Voltage Law to this loop and find the value of loop current.


Applying KVL,  $20I + 5I + 10 - 40 = 0$


$$25I = 30$$

$$I = 1.2\text{ A}$$

$$V_{TH} = 10 + (5 * 1.2) = 16\text{ v}$$

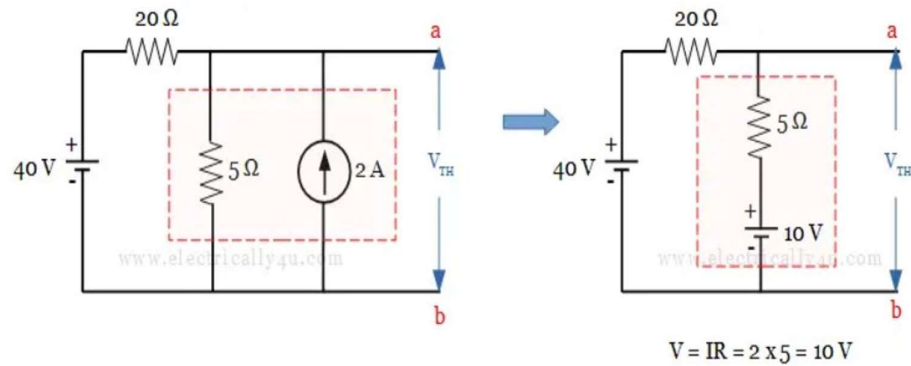
By source transformation, let us convert this current source into its equivalent voltage source in series with  $5\ \Omega$  resistor.



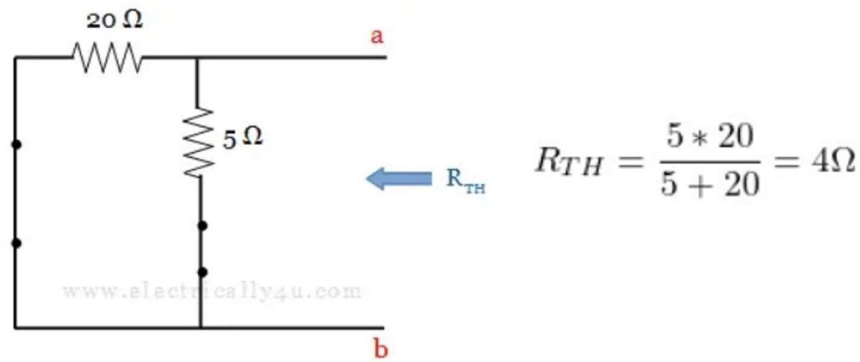


$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{16}{4 + 15} = 0.842A$$

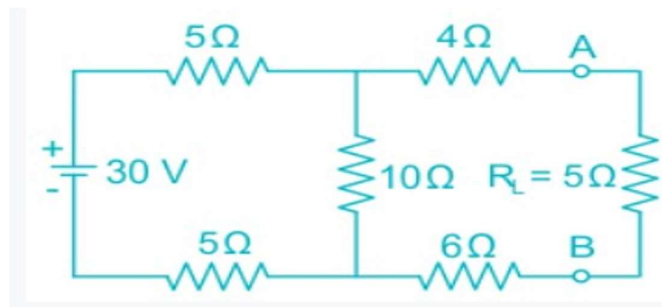**Example 4:** In the network shown in figure, calculate the current through the load resistor  $R_L$  by using Norton's Theorem.



Ans.

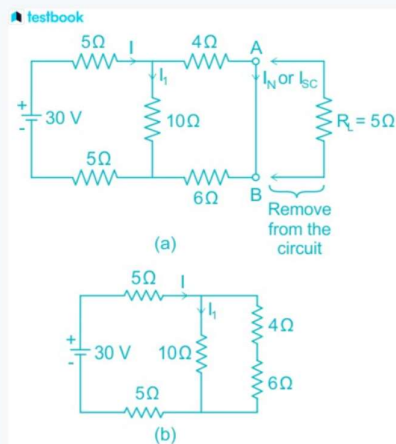Step 1 : Remove the load resistance  $R_L = 5\Omega$  and short circuit the terminals A and B



Step 2 : Find the current  $I_N$  flowing through A and B

Total resistance  $R = (5 + 5)\Omega + (10\Omega) \parallel (4 + 6)\Omega$

$$= 10 + \frac{10 \times 10}{10 + 10} = 10 + 5 = 15\Omega$$

Current  $I = \frac{V}{R}$


$$I = \frac{30}{15} = 2A$$

Short circuit current,  $I_{SC}$  or  $I_N = I \times \frac{10}{10 + 4 + 6}$

$$2 \times \frac{10}{20} = 1A$$

Step 3: Short circuit the voltage source and find the Norton equivalent resistance  $R_N$  as seen from the terminal A and B.


testbook

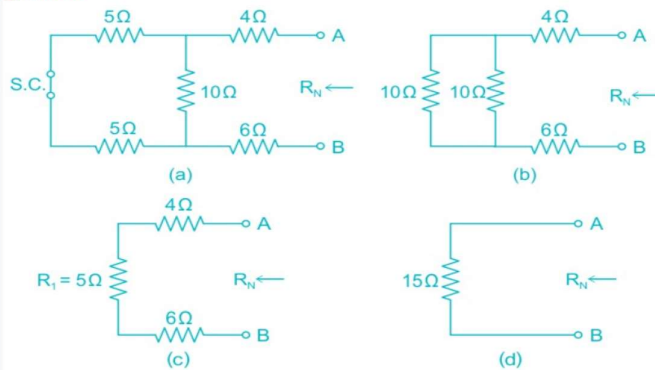

$$R_1 = 10\Omega || 10\Omega = \frac{10 \times 10}{10 + 10} = 5\Omega$$


$$R_N = R_{AB} = 4 + R_1 + 6$$

$$4 + 5 + 6 = 15\Omega$$

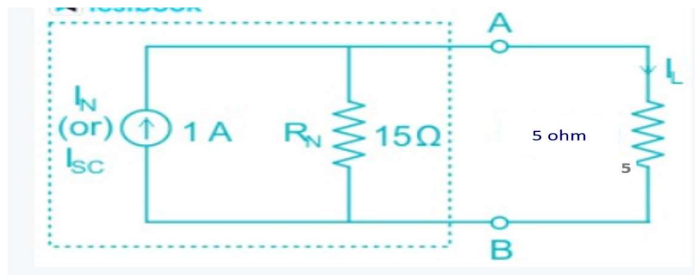

### Assignment Home Work

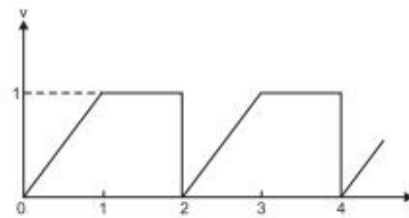Q1. Calculate the RMS value of power supply of given wave function in fig.




Ans:  $5/4V$  [Area of graph from 0 to 2-time unit and divided by 2]


Q2.

**Q. Find the value of current through  $1\Omega$  Resistor in the given circuit using Thevenin's theorem.**

**Find the current across  $1\text{ ohm}$  resistor  
Using Thevenin's Theorem**

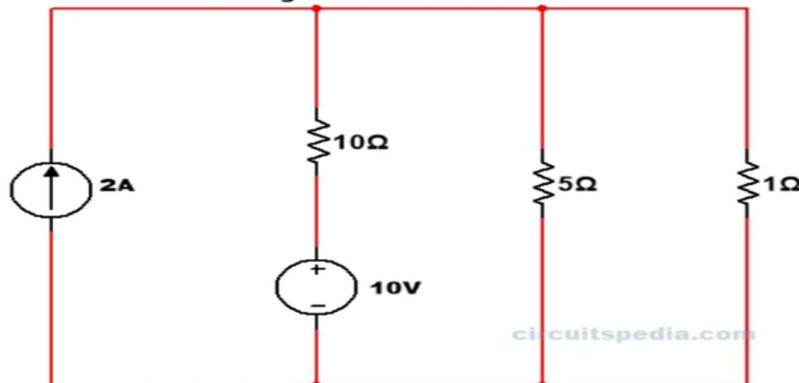

**Ans 1:**

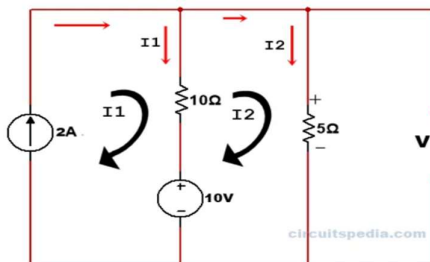

Applying KVL in All meshes.

$$I = 2A$$


$$10 - 10(I_2 - I_1) - 5I_2 = 0$$

$$-15I_2 = 10I_1 - 10$$

$$-15I_2 = -10 - 20 = -30$$

$$-15I_2 = -30$$

$$I_2 = 30 / 15 = 2A$$

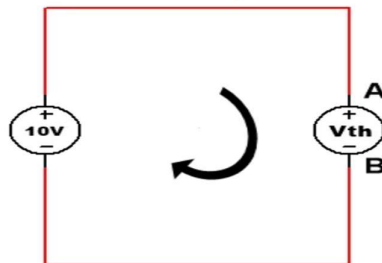

The voltage across the  $5\Omega$  resistor is  $V = I \cdot R = 2 \cdot 5 = 10V$

Q . A sine wave voltage has a maximum value of  $20\text{ V}$  and a frequency of  $50\text{ Hz}$ . Determine the instantaneous voltage present (a)  $2.5\text{ ms}$  and (b)  $15\text{ ms}$  from the start of the cycle.

**Solution**

We can find the voltage at any instant of time using:

$$v = V_{\max} \sin(2\pi f t)$$

where  $V_{\max} = 20\text{ V}$  and  $f = 50\text{ Hz}$ . In (a),  $t = 2.5\text{ ms}$ , hence:

$$v = 20 \sin(2\pi \times 50 \times 0.0025) = 20 \sin(0.785) = 20 \times 0.707 = 14.14\text{ V}$$

In (b),  $t = 15\text{ ms}$ , hence:

$$v = 20 \sin(2\pi \times 50 \times 0.015) = 20 \sin(4.71) = 20 \times -1 = -20\text{ V}.$$

.....

### **MCQs (Gate question)**

**1.Thevenin's theorem states that any linear bilateral network can be replaced by a single voltage source in series with a:**

- a. Current source
- b. Impedance
- c. Capacitor
- d. Resistor

**Answer: d. Resistor**

**2.Thevenin's equivalent voltage is:**

- a. The open-circuit voltage at the terminals of the load
- b. The short-circuit current at the terminals of the load
- c. The voltage across the load resistor
- d. The voltage across the source resistor

**Answer: a. The open-circuit voltage at the terminals of the load**

**3.To find Thevenin's resistance, we need to:**

- a. Short all voltage sources and open all current sources
- b. Open all voltage sources and short all current sources
- c. Open all voltage and current sources
- d. Short all voltage and current sources

**Answer: a. Short all voltage sources and open all current sources**

**4.In Thevenin's equivalent circuit, the load resistor is connected:**

- a. In parallel with the Thevenin resistance
- b. In series with the Thevenin resistance
- c. Across the voltage source
- d. Between the Thevenin voltage and ground

**Answer: b. In series with the Thevenin resistance**

**5.Thevenin's theorem is applicable to:**

- a. Linear circuits only
- b. Non-linear circuits
- c. Both linear and non-linear circuits
- d. AC circuits only

**Answer: a. Linear circuits only**

**6.Norton's theorem states that any linear bilateral network can be replaced by a single current source in parallel with a:**

- a. Voltage source
- b. Capacitor
- c. Impedance

d. Resistor

**Answer: d. Resistor**

**7. Norton's equivalent current is:**

- a. The open-circuit current at the terminals of the load
- b. The short-circuit current at the terminals of the load
- c. The current through the load resistor
- d. The current through the source resistor

**Answer: b. The short-circuit current at the terminals of the load**

**8. To find Norton's resistance, we need to:**

- a. Short all voltage sources and open all current sources
- b. Open all voltage sources and short all current sources
- c. Open all voltage and current sources
- d. Short all voltage and current sources

**Answer: a. Short all voltage sources and open all current sources**

**9. In Norton's equivalent circuit, the load resistor is connected:**

- a. In series with the Norton resistance
- b. In parallel with the Norton resistance
- c. Across the current source
- d. Between the Norton current and ground

**Answer: b. In parallel with the Norton resistance**

**10. Norton's theorem is applicable to:**

- a. Linear circuits only
- b. Non-linear circuits
- c. Both linear and non-linear circuits
- d. DC circuits only

**Answer: a. Linear circuits only**

**11. The average value of a full-wave rectified sinusoidal current over one complete cycle is:**

- a. Zero
- b.  $2I_m/\pi$
- c.  $I_m/\sqrt{2}$
- d.  $I_m$

**Ans b**

The RMS value of a sinusoidal voltage  $v(t) = V_m \sin(\omega t)$  is:

- a.  $V_m$
- b.  $\frac{V_m}{\sqrt{2}}$
- c.  $\frac{V_m}{2}$
- d.  $\frac{V_m}{\pi}$

Answer: b.  $\frac{V_m}{\sqrt{2}}$

The average value of a pure sinusoidal voltage over one complete cycle is:

- a. Zero
- b.  $\frac{V_m}{\pi}$
- c.  $\frac{2V_m}{\pi}$
- d.  $V_m$

Answer: a. Zero

For a triangular waveform with peak value  $V_m$ , the RMS value is:

- a.  $\frac{V_m}{\sqrt{3}}$
- b.  $\frac{V_m}{2}$
- c.  $\frac{V_m}{\sqrt{2}}$
- d.  $\frac{V_m}{\pi}$

Answer: a.  $\frac{V_m}{\sqrt{3}}$