


LOGIC GATES
Boolean Algebra
Simplification
SOP-POS/Minterm-Maxterm

Logic Gate

- Digital systems are said to be constructed by using logic gates.
- These gates are the **AND, OR, NOT, NAND, NOR, EXOR and EXNOR** gates.
- The basic operations are described below with the aid of truth tables
- Truth tables are used to help show the function of a logic gate
- Boolean functions are practically implemented by using electronic gates
- Generally logic gate have 2 input 1 output
- Gate **INPUTS** are driven by voltages having two nominal values,
0V logic 0 and 5V logic 1
- The **OUTPUT** of a gate provides two nominal values of voltage only
0V logic 0 and 5V logic 1

Logic Gate

AND gate

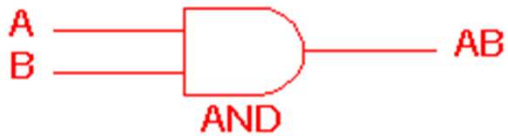

2 Input AND gate		
A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

high output (1) only if **all** its inputs are high

OR gate



2 Input OR gate		
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

high output (1) if **one or more** of its inputs are high.

NOT gate



NOT gate	
A	\bar{A}
0	1
1	0

produces an inverted version of the input at its output.

Circuit Implementation with Logic Gate

Step-1 Truthtable

Step-2 Minterm/SOP equation

Step-3 Simplification (Boolean algebra/K-Map)

Step-4 Circuit Design

1. Design a 2 input circuit produces high output for atleast 1 input logic low.
2. Design a 3-input circuit that produces a high output when at least one input is high.

Simplification



Draw schematic diagram of

$$Q(x,y) = x'y + xy'$$

Simplification

Draw schematic diagram of
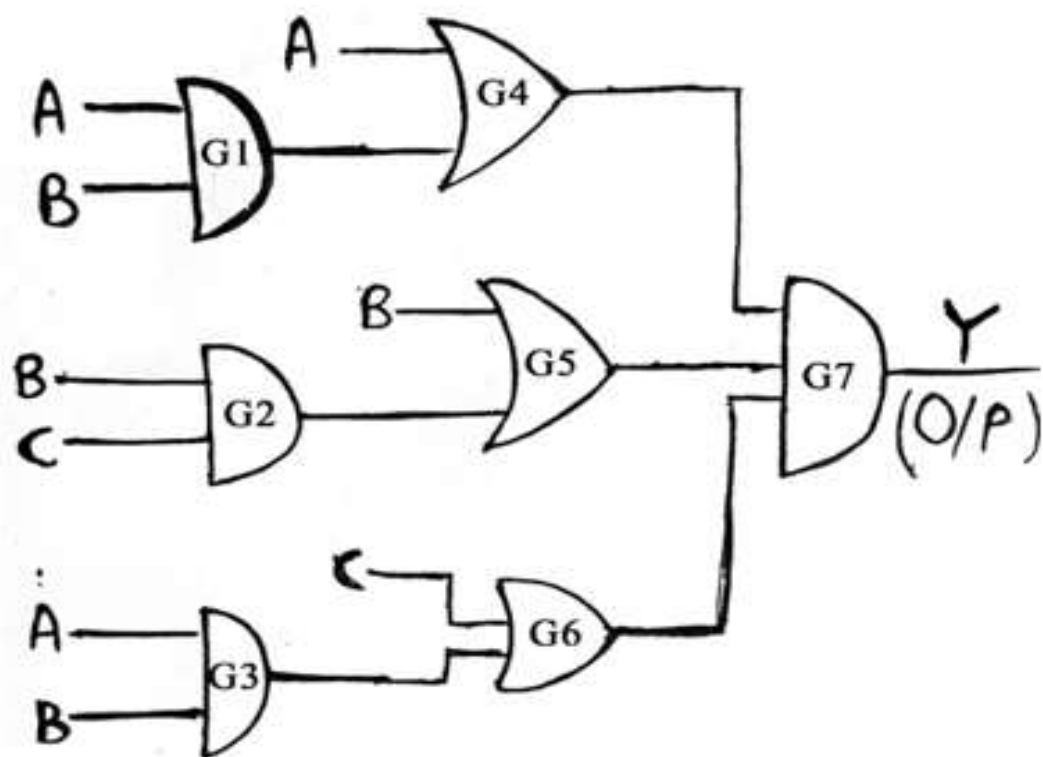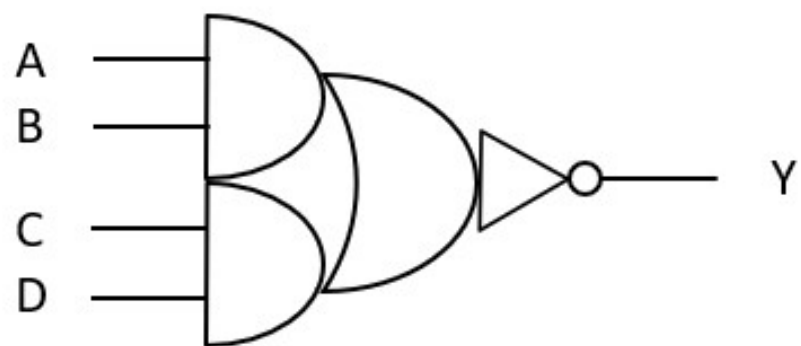
$$Q(A,B,C)=A\bar{B} + BC\overline{(B+C)}$$



Complement

When complement is opened:

- Variable is complemented
- Functions change $(+ \rightarrow .)$ $(. \rightarrow +)$

Logic Gate

NAND GATE

AND gate followed by a NOT gate.



2 Input NAND gate		
A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

high output (1) only if **all** its inputs are low

NOR GATE

OR gate followed by a NOT gate.



2 Input NOR gate		
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Low output (0) if **one or more** of its inputs are high.

NAND and NOR gates are called *universal*

Logic Gate


EXOR GATE/XOR



2 Input EXOR gate		
A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

high output (1) for different input

EXNOR GATE/XNOR

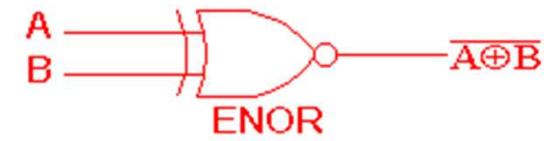

2 Input EXNOR gate		
A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

High output (1) for same input

Quiz Time

Identify the universal gate

A. AND-OR

B. NAND-NOR 

C. XOR-XNOR

D. All of above

Boolean Algebra

Analyze and simplify the digital (logic) circuits.

Variable used can have only two values, Binary 1 for HIGH and Binary 0 for LOW.

Commutative law

$$(i) A.B = B.A$$

$$(ii) A + B = B + A$$

Associative law

$$(i) (A.B).C = A.(B.C)$$

$$(ii) (A + B) + C = A + (B + C)$$

Distributive law

$$A.(B + C) = A.B + A.C$$

AND law

$$(i) A.0 = 0$$

$$(ii) A.1 = A$$

$$(iii) A.A = A$$

$$(iv) A.\overline{A} = 0$$

OR law

$$(i) A + 0 = A$$

$$(ii) A + 1 = 1$$

$$(iii) A + A = A$$

$$(iv) A + \overline{A} = 1$$

INVERSION law

$$\overline{\overline{A}} = A$$

	Postulate / Theorem	Dual
1. Identity Element	$x + 0 = x$	$x \cdot 1 = x$
2. Complementation	$x + x' = 1$	$x \cdot x' = 0$
3. Idempotency	$x + x = x$	$x \cdot x = x$
4. Null Law	$x + 1 = 1$	$x \cdot 0 = 0$
5. Involution (Double negation)	$(x')' = x$	-
6. Commutative	$x + y = y + x$	$xy = yx$
7. Associative	$x + (y + z) = (x + y) + z$	$x(yz) = (xy)z$
8. Distributive	$x + yz = (x + y)(x + z)$	$x(y + z) = xy + xz$
9. De Morgan	$(x + y)' = x' y'$	$(xy)' = x' + y'$
10. Absorption	$x + xy = x$	$x(x + y) = x$
11. Simplification	$x + x'y = x + y$	$x(x' + y) = xy$
12. Consensus	$xy + x'z + yz = xy + x'z$	$(x+y)(x'+z)(y+z) = (x+y)(x'+z)$

Duality Theorem in Boolean Algebra

AND \longleftrightarrow OR

1 \longleftrightarrow 0

Example : Find the dual form of :



1) $A \cdot 0 = 0$

2) $A \cdot (A + B) = A$

De Morgan Law



$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NAND = Bubbled OR

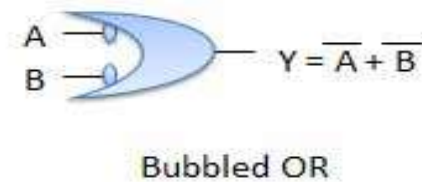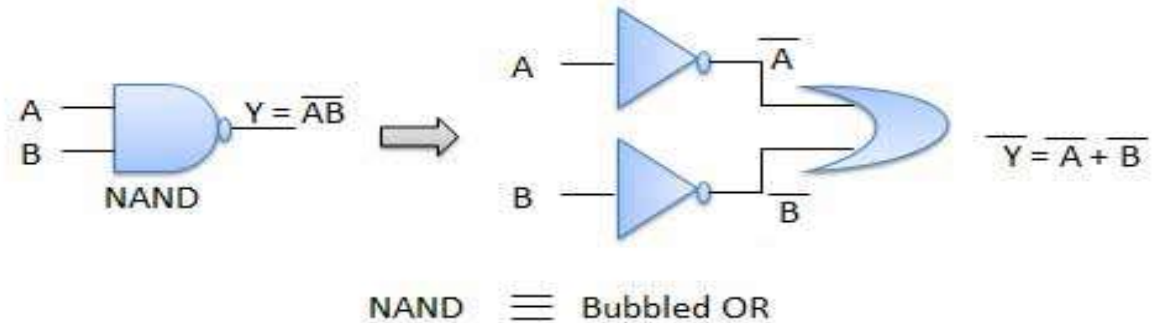

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

NOR = Bubbled AND

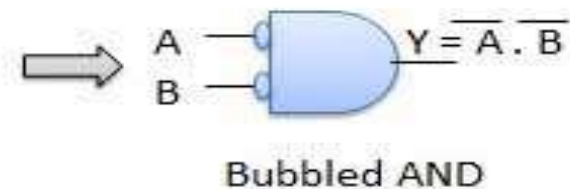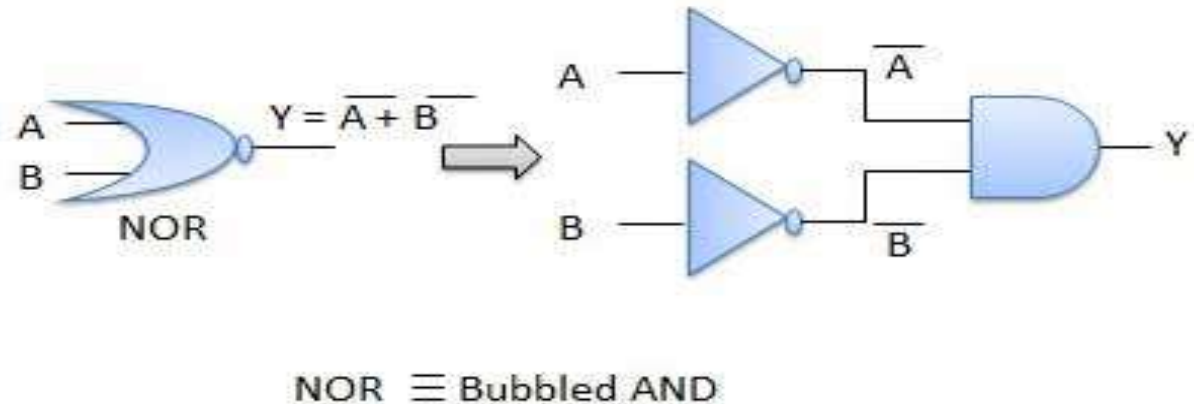


Implementation with NAND


NAND Gate Symbol




NOT Gate
(Inverter)

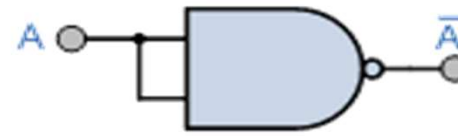


AND Gate

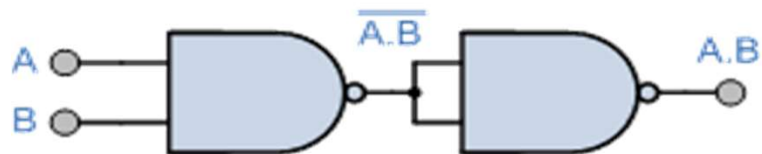


Buffer

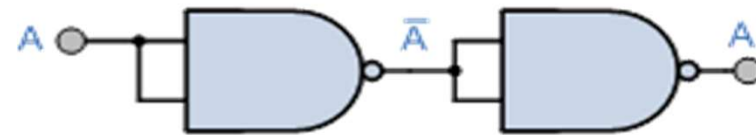


OR Gate

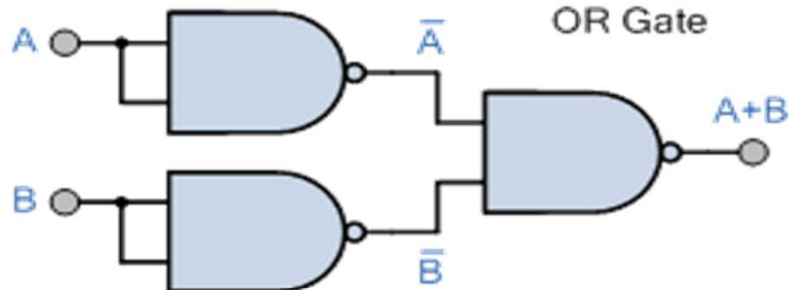


Exclusive-OR

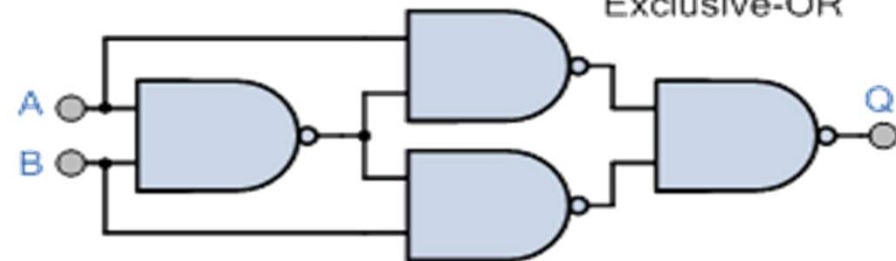

NOR Gate

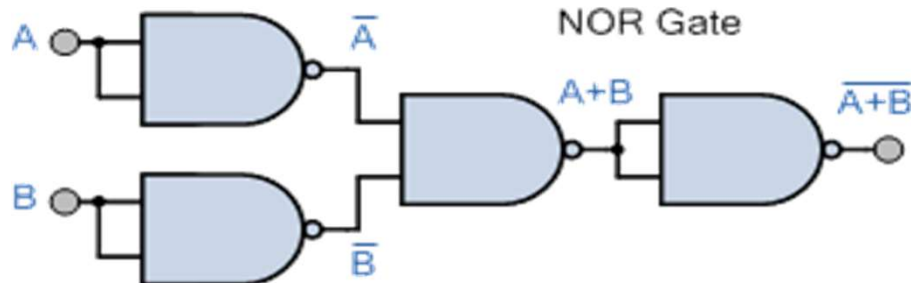


Exclusive-NOR

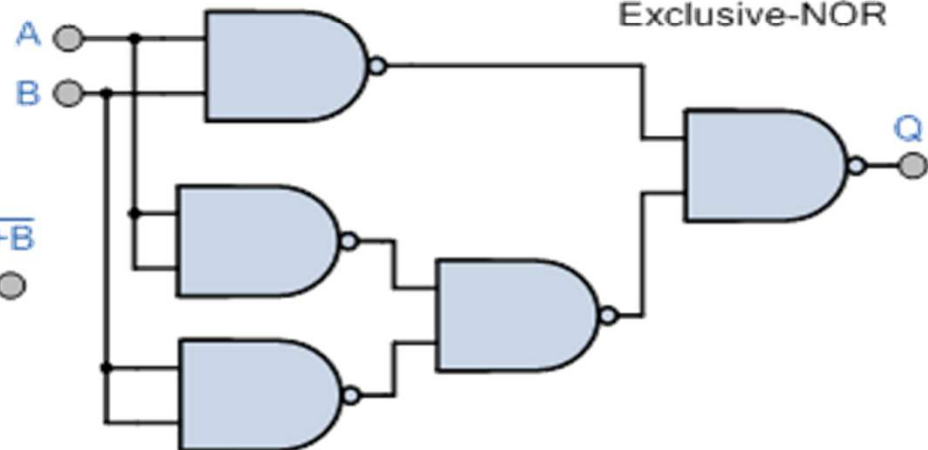


Implementation with NOR


NOR Gate Symbol

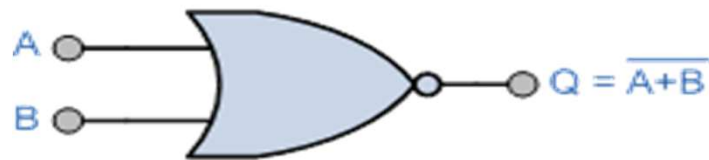


NOT Gate (Inverter)

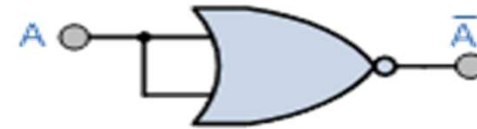


OR Gate

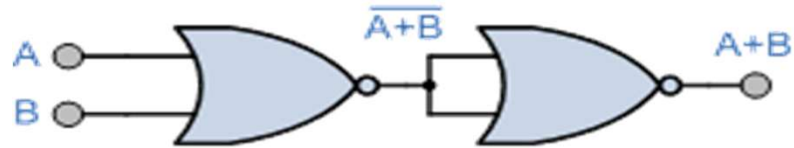


Buffer

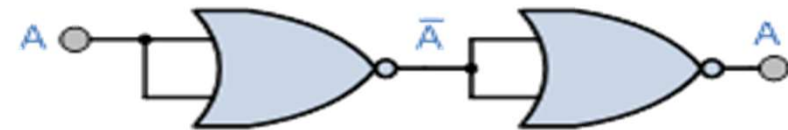


AND Gate

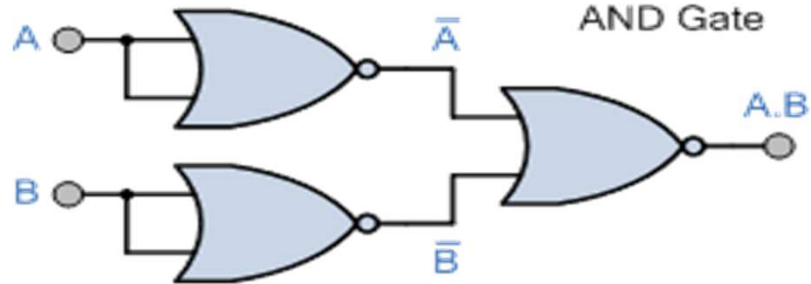


Exclusive-OR

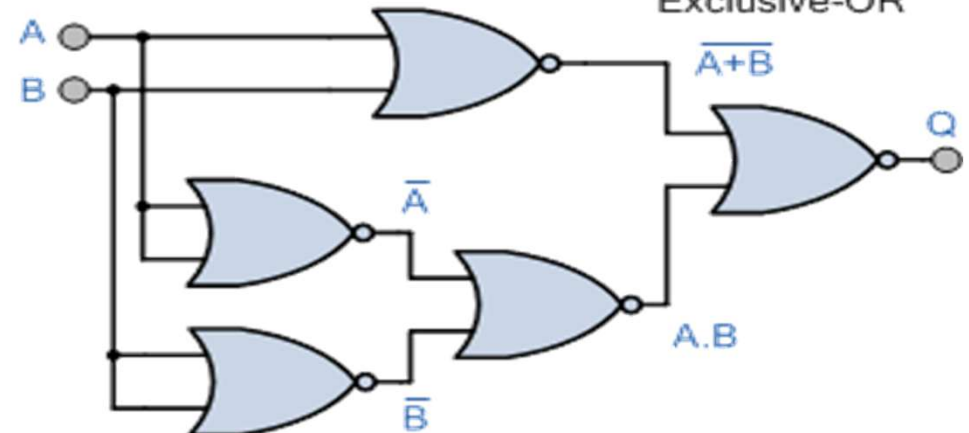


NAND Gate

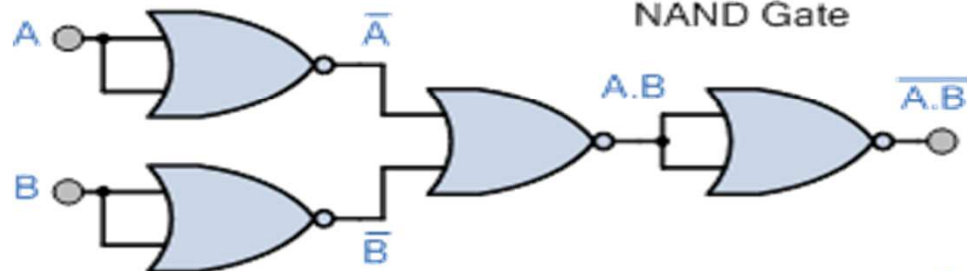

Exclusive-NOR

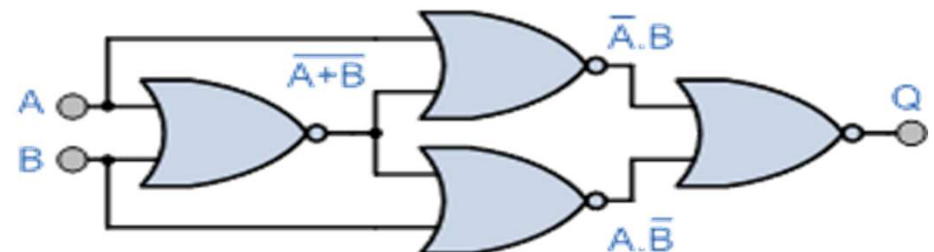


Convert AOI to NAND/NOR logic

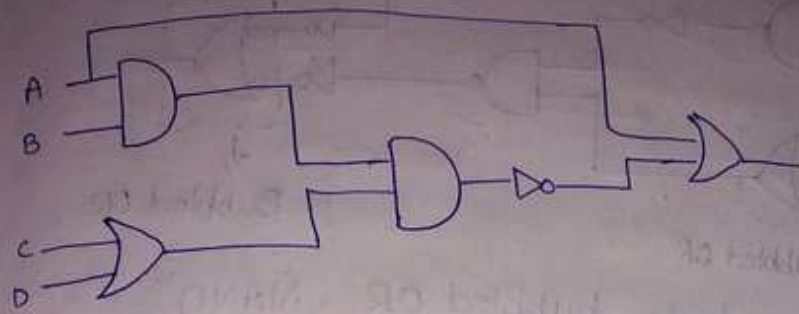


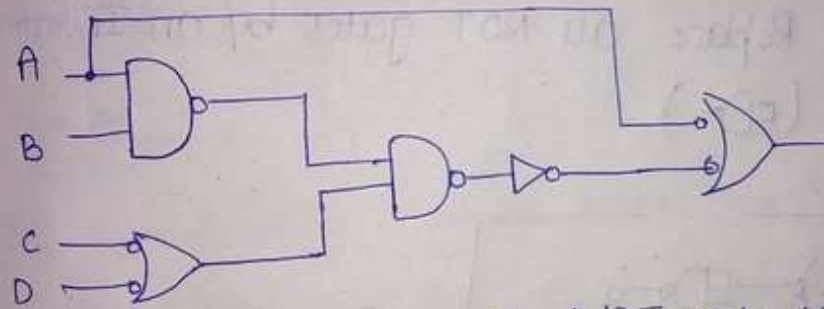1. NAND logic:-

Step 1:- Add bubbles to the above circuit at the input of OR gates and the output of AND gate.



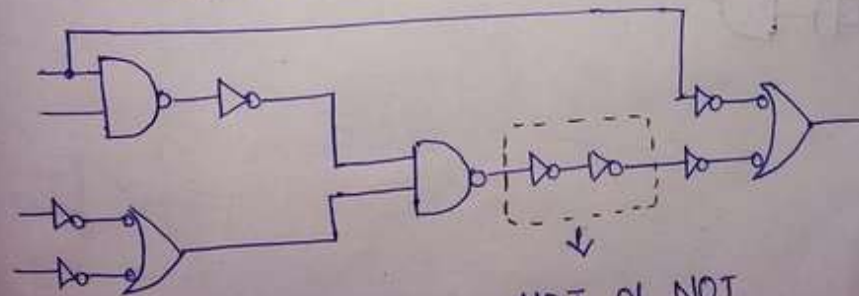
Step 2:- Now add NOT gates wherever the bubbles are added




NOT of NOT


i.e. $\overline{\overline{x}} = x$


So these can be eliminated

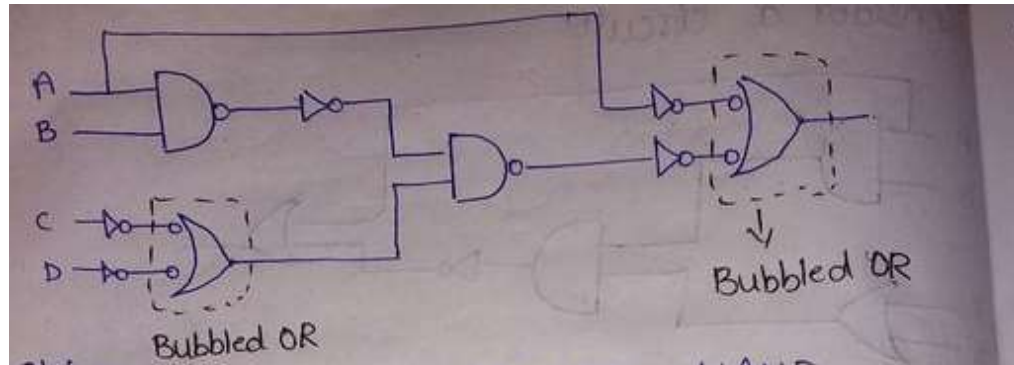


Step 3:-
In AOI logic bubbled OR = NAND

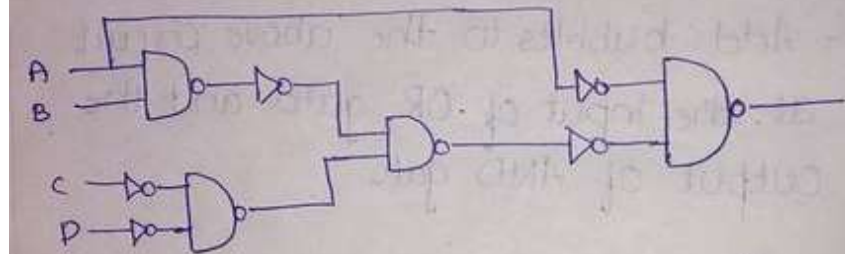

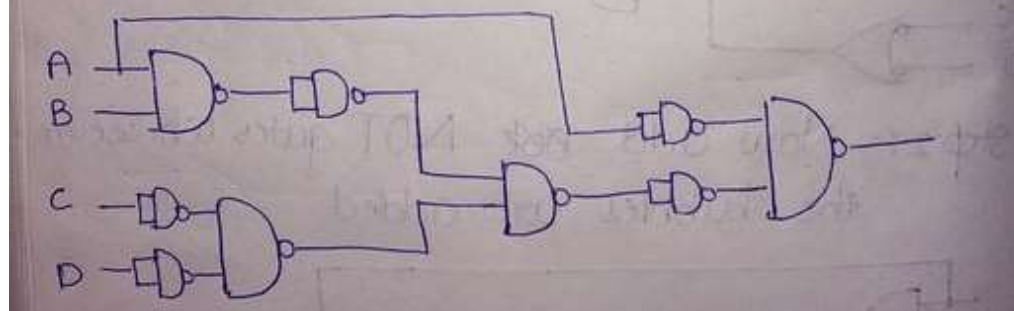
Step 4:- Replace all NOT gates by an Inverter
()




2. NOR Logic :-

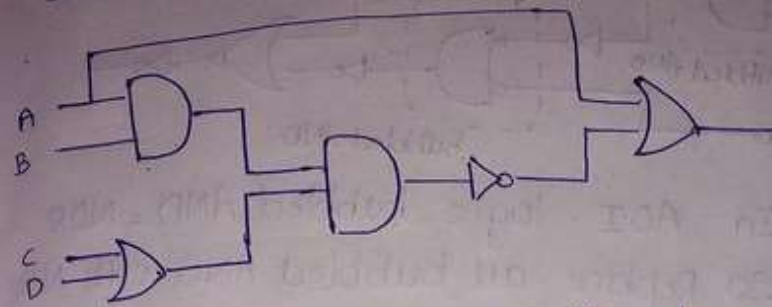

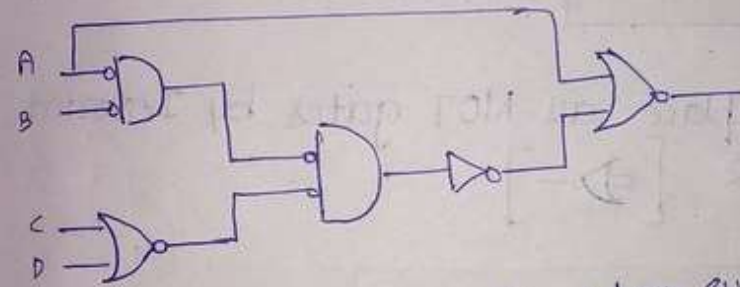
Step 1:- Add bubbles to the above circuit at the output of OR gate and the input of AND gate.



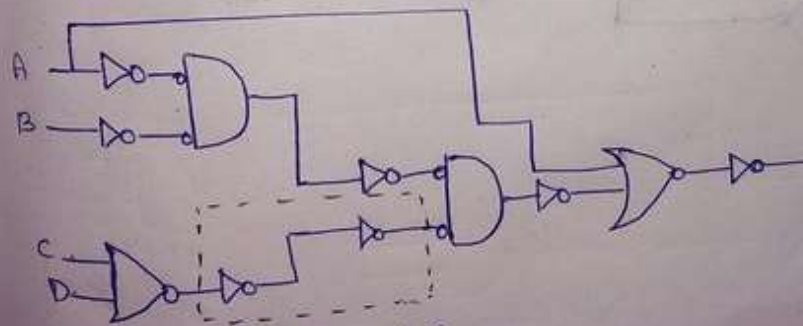
Step 2:- Add NOT gates where ever the bubbles are added.




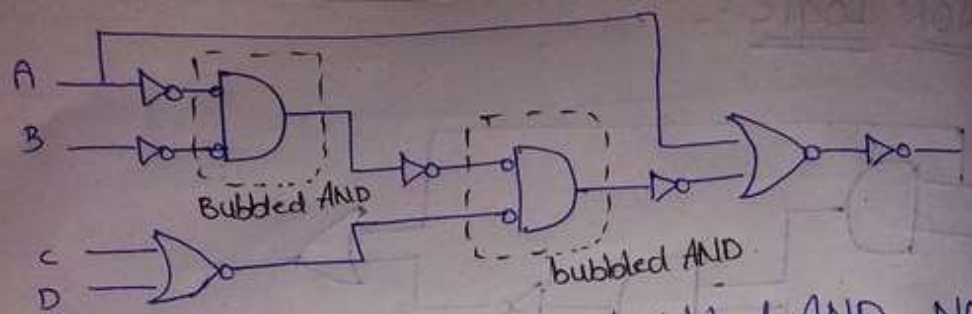
NOT of NOT
So these NOT gates can
be eliminated



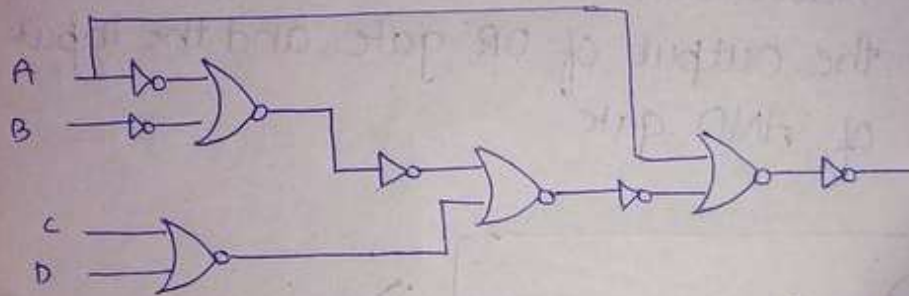Step 3:- In AOI logic bubbled AND = NOR
 so Replace all bubbled AND with NOR




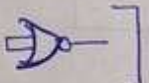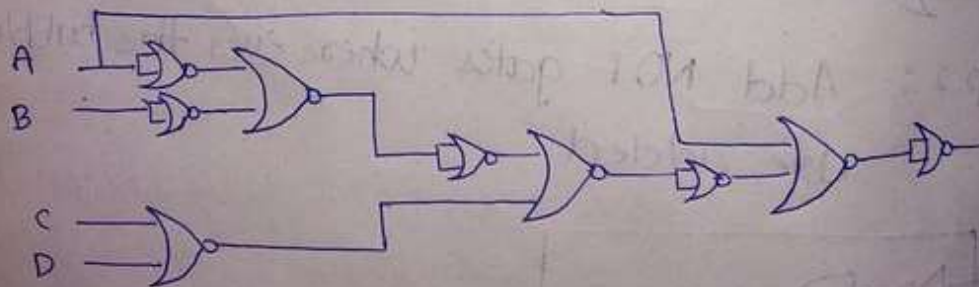Step 4:- Replace all NOT gates by Inverted
 OR []




Convert AOI to NAND/NOR logic

Ex. 1

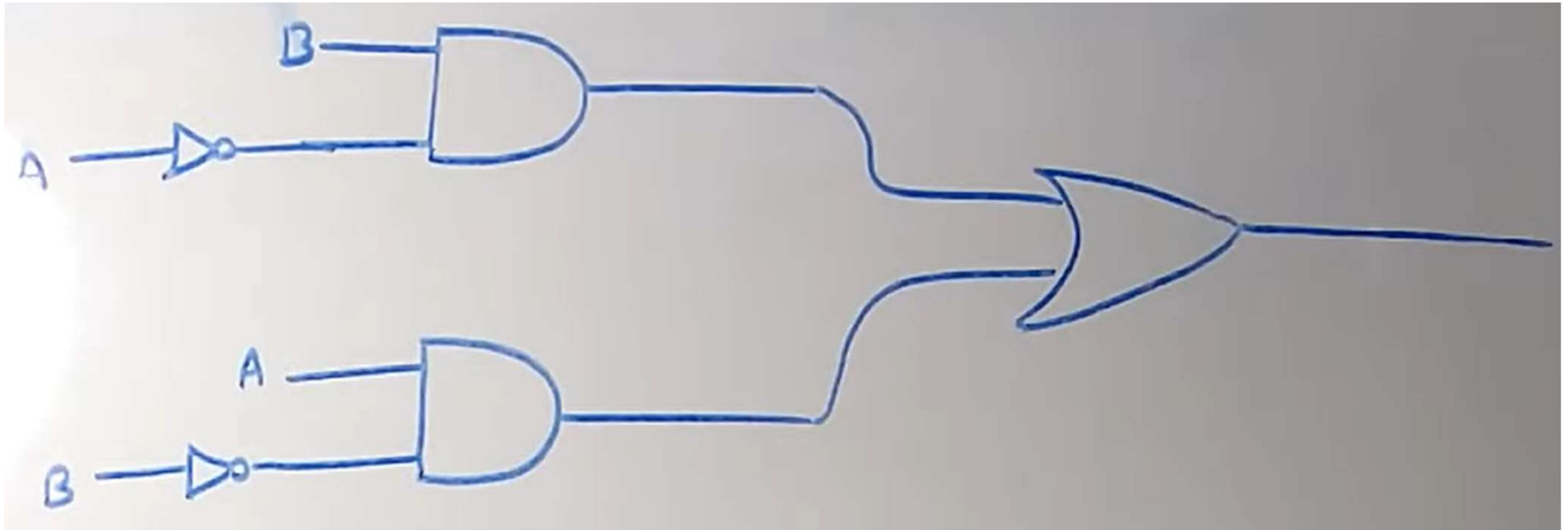

1. NAND
2. NOR
3. AOI to NOR

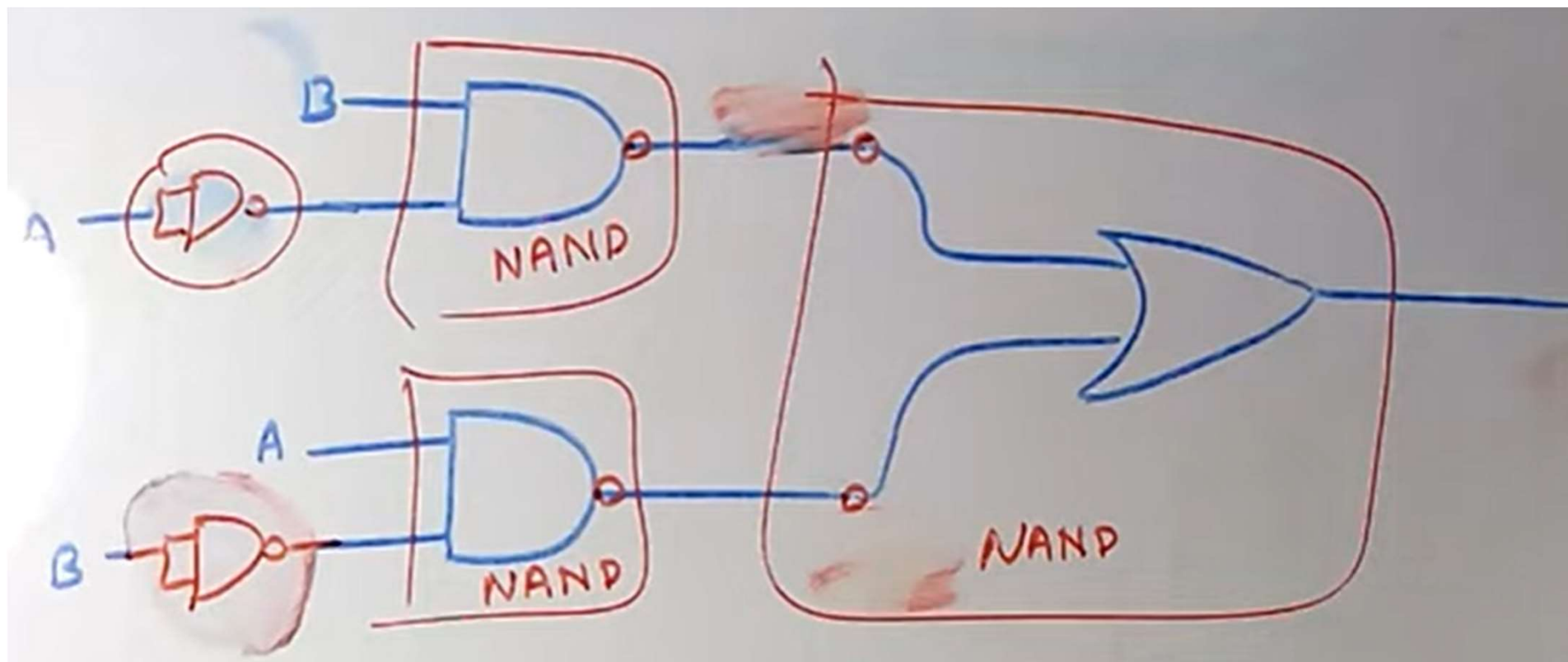

Sum of Product (SOP): Group of product terms (minterms) are ORed together

$$f(A, B, C) = \overline{A} B C + A \overline{B} \overline{C}$$

product terms

sum

$$f(P, Q, R, S) = \overline{P} Q + Q R + R S$$

Product terms

sum

Product of Sum (POS): Group of OR terms (maxterms) are ANDed together

$$f(A, B, C) = (A + B) \cdot (\overline{B} + C)$$

Sum terms

Product

$$f(P, Q, R, S) = (P + Q) \cdot (R + \overline{S}) \cdot (P + S)$$

Sum terms

Product

- **Minterms**- It is known as the product term. In the minterm, each uncomplemented term is indicated by '1', and each complemented term is indicated by '0'.
- **Maxterms**— It is known as the sum term. In maxterm, each uncomplemented term is indicated by '0' and each complemented term is indicated by '1'.

SOP

- **Sum-of-Products (SOP)/ Minterm Form** - variables operated by AND (product) are ORed(sum) together.
- *Each product term is called a **minterm (m)**.*

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

SOP Expression

1. Write AND term for each input combination that produces a HIGH o/p.
2. Write the input variables for 1 and complement for 0.
3. OR the AND terms to obtain the output function.

$$F(\text{SOP}) = \underset{m3}{A'BC} + \underset{m5}{AB'C} + \underset{m6}{ABC'} + \underset{m7}{ABC}$$

POS is complement of SOP

POS

- **Product-of-sums (POS)/Maxterm form** - variables operated by OR (sum) are ANDed (product) together.
- *Each sum term is called a **maxterm (M)**.*

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

POS Expression

1. Write OR term for each input combination that produces a LOW o/p.
2. Write the input variables for 0 and complement for 1
3. AND the OR terms to obtain the output function.

$$F(\text{POS}) = (A + B + C) (A + B + C') (A + B' + C) (A' + B + C)$$

M0 . M1 . M2 . M4

POS is complement of SOP

Table (1) Minterms and maxterms

<i>Variables</i>			<i>Minterms</i>	<i>Maxterms</i>
<i>A</i>	<i>B</i>	<i>C</i>		
0	0	0	$\bar{A}\bar{B}\bar{C} = m_0$	$A + B + C = M_0$
0	0	1	$\bar{A}\bar{B}C = m_1$	$A + B + \bar{C} = M_1$
0	1	0	$\bar{A}B\bar{C} = m_2$	$A + \bar{B} + C = M_2$
0	1	1	$\bar{A}BC = m_3$	$A + \bar{B} + \bar{C} = M_3$
1	0	0	$A\bar{B}\bar{C} = m_4$	$\bar{A} + B + C = M_4$
1	0	1	$A\bar{B}C = m_5$	$\bar{A} + B + \bar{C} = M_5$
1	1	0	$AB\bar{C} = m_6$	$\bar{A} + \bar{B} + C = M_6$
1	1	1	$ABC = m_7$	$\bar{A} + \bar{B} + \bar{C} = M_7$

Each Minterm is represented by m_i and each Maxterm is represented by M_i . The subscript i is the decimal number. The logical function can be represented with the help of these shorthand notations as follows:

$$\begin{aligned} 1. \quad Y &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + ABC \\ &= m_0 + m_2 + m_5 + m_7 \\ &= \sum m(0, 2, 5, 7) \end{aligned}$$

$$\begin{aligned} 2. \quad Y &= (A + B + C)(\bar{A} + B + C)(\bar{A} + \bar{B} + \bar{C}) \\ &= M_1 + M_4 + M_7 \\ &= \prod M(1, 4, 7) \end{aligned}$$

where \sum and \prod denote the sum of product and product of sum respectively.

Table (2) Minterms

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>	
0	0	0	0	
0	0	1	1	← $\bar{A}\bar{B}C$
0	1	0	0	
0	1	1	0	
1	0	0	1	← $A\bar{B}\bar{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	← ABC

$Y = 1$ when $A = 0$, $B = 0$ and $C = 1$. Or, $\bar{A}\bar{B}C$ will make $Y = 1$ only. Similarly, $Y = 1$ for $A\bar{B}\bar{C}$ and ABC .

Thus, the standard SOP form becomes

$$Y = \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$

Table (3) Maxterms

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>	
0	0	0	1	
0	0	1	0	$\leftarrow A + B + \bar{C}$
0	1	0	1	
0	1	1	1	
1	0	0	1	
1	0	1	0	$\leftarrow \bar{A} + B + \bar{C}$
1	1	0	1	
1	1	1	1	

From Table (3), $Y = 0$ when $A = 0$, $B = 0$ and $C = 1$. Therefore, $A + B + C$ gives $Y = 0$. Similarly, $A + B + C$ gives $Y = 0$. Thus, the standard product of sum form is

$$Y = (A + B + \bar{C})(\bar{A} + B + \bar{C})$$

SOP-POS Conversion

- Convert the SOP expression to an equivalent POS expression:

$$\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C + ABC$$

- The evaluation is as follows:


$$000 + 010 + 011 + 101 + 111$$

- There are 8 possible combinations. The SOP expression contains five of these, so the POS must contain the other 3 which are: 001, 100, and 110.

$$(A + B + \overline{C})(\overline{A} + B + C)(\overline{A} + \overline{B} + C)$$

Canonical/Standard Boolean Expression

Every product term involves every literal (all the variables of a function) or its complement.

$$f(A, B, C) = \boxed{A\bar{B}C} + \boxed{ABC} + \boxed{\bar{A}B\bar{C}}$$


Each product term consists of all literals in either complemented form or uncomplemented form


Canonical/Standard Boolean Expression

Convert the given expression in standard SOP format

$$F(A,B,C) = AC + AB + BC$$

Canonical/Standard Boolean Expression

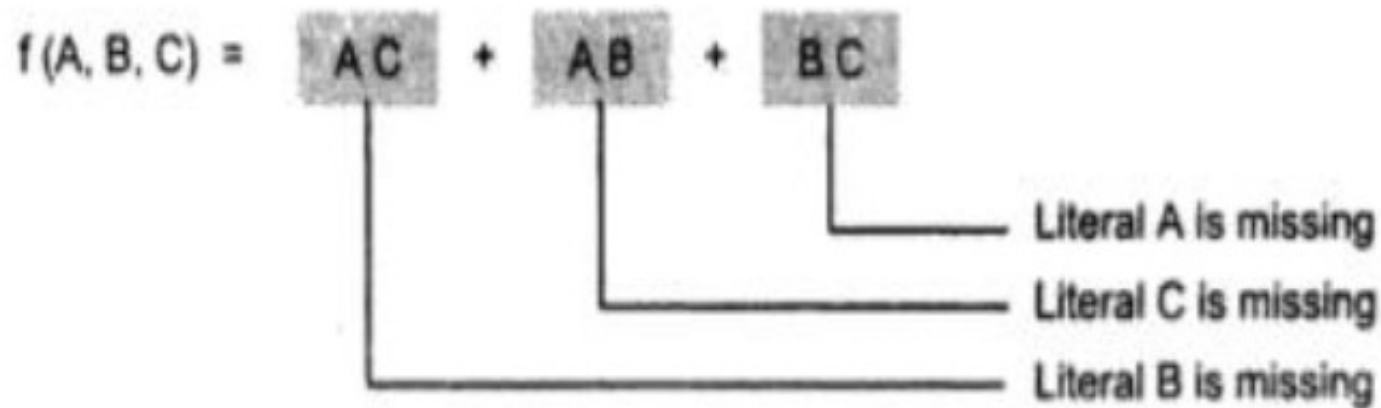Convert the given expression in standard SOP format



Canonical/Standard Boolean Expression

Convert the given expression in standard SOP format

$$f(A, B, C) = AC + AB + BC$$

Literal A is missing
Literal C is missing
Literal B is missing

Original product terms

$$f(A, B, C) = AC \cdot (B + \bar{B}) + AB \cdot (C + \bar{C}) + BC \cdot (A + \bar{A})$$

Missing literals and their complements

Omit repeated product terms

$$f(A, B, C) = ABC + A\bar{B}C + \cancel{ABC} + AB\bar{C} + \cancel{ABC} + \bar{A}BC$$
$$\therefore f(A, B, C) = ABC + A\bar{B}C + AB\bar{C} + \bar{A}BC$$

Convert the given expression in standard SOP format

$$f(\bar{A}, B, C) = A + ABC$$

Canonical/Standard Boolean Expression


Convert the given expression in standard POS format

$$F(A,B,C) = (A+B).(B+C).(A+C)$$

Convert the given expression in standard POS format

$$F(A,B,C) = (A+B).(B+C).(A+C)$$

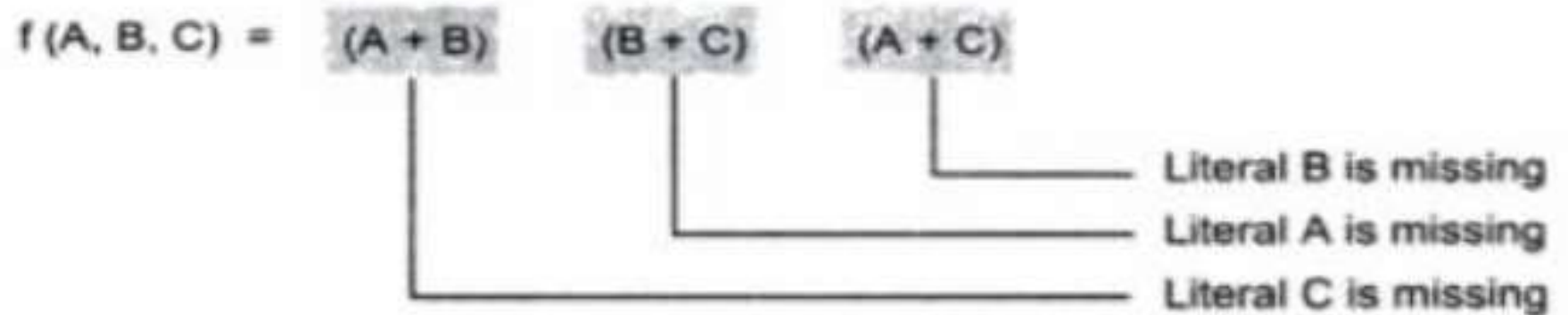
Find the missing literal/s in each sum term





Convert the given expression in standard POS format

$F(A,B,C) = (A+B).(B+C).(A+C)$

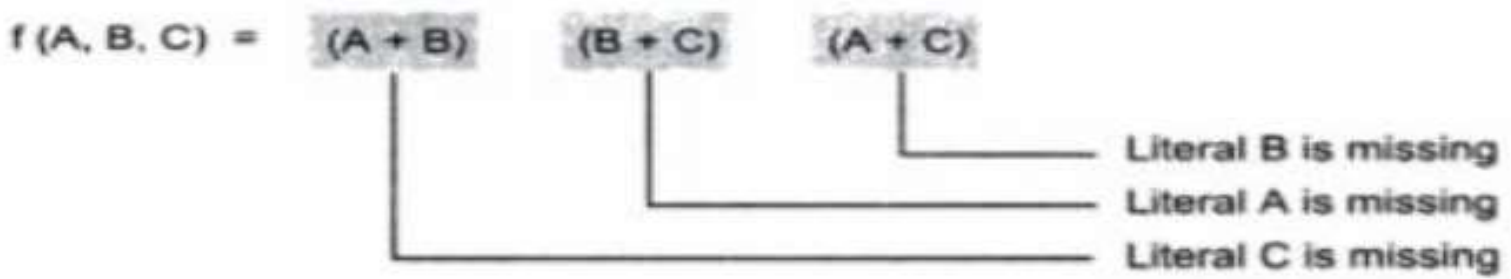Find the missing literal/s in each sum term



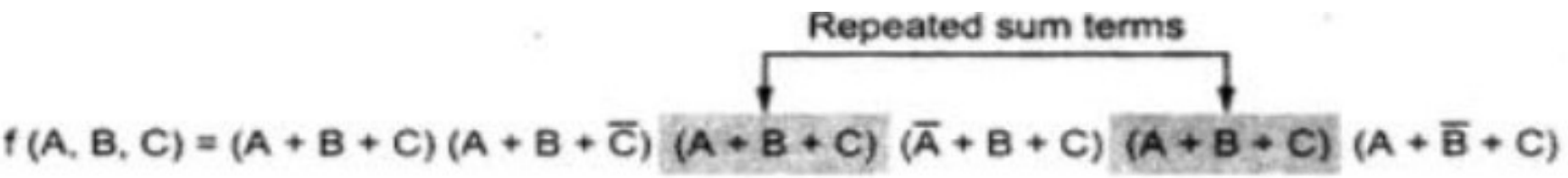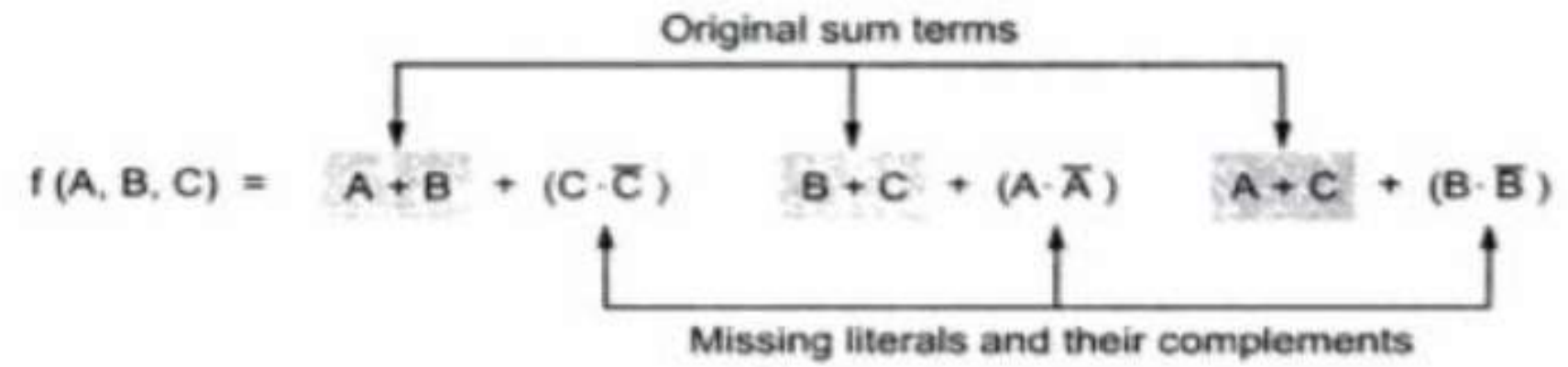OR sum term with (missing literal • its complement)



$\therefore f(A, B, C) = (A + B + C) (A + B + \overline{C}) (\overline{A} + B + C) (A + \overline{B} + C)$

We can show that a product of sums form derived from a truth table is logically equivalent to a sum of products form derived from the same truth table. From Table (3), we get

$$\text{SOP Form: } Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC\overline{C} + ABC$$

$$\text{POS Form: } Y = (A + B + \overline{C})(\overline{A} + B + \overline{C})$$

Let us simplify the POS form:

$$\begin{aligned} Y &= (A + B + \overline{C})(\overline{A} + B + \overline{C}) \\ &= A\overline{A} + AB + A\overline{C} + \overline{A}B + BB + B\overline{C} + \overline{A}\overline{C} + B\overline{C} + \overline{C}\overline{C} \\ &= AB + A\overline{C} + \overline{A}B + B + B\overline{C} + \overline{A}\overline{C} + B\overline{C} + \overline{C}\overline{C} \\ &= AB(C + \overline{C}) + A\overline{C}(B + \overline{B}) + \overline{A}B(C + \overline{C}) + (A + \overline{A})B(C + \overline{C}) + (A + \overline{A})B\overline{C} \\ &\quad + \overline{A}\overline{C}(B + \overline{B}) + (A + \overline{A})B\overline{C} + (A + \overline{A})(B + \overline{B})\overline{C} \\ &= ABC + ABC\overline{C} + ABC\overline{C} + A\overline{B}\overline{C} + \overline{A}BC + \overline{A}B\overline{C} + ABC\overline{C} + ABC + \overline{A}BC + \overline{A}B\overline{C} \\ &\quad + ABC\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}\overline{C} + ABC\overline{C} + \overline{A}B\overline{C} + ABC\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}\overline{C} \\ &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}BC + ABC\overline{C} + ABC \end{aligned}$$

∴

$$\begin{aligned} Y &= m_0 + m_2 + m_3 + m_4 + m_6 + m_7 \\ &= \sum m(0, 2, 3, 4, 6, 7) \\ &= \prod M(1, 7) \end{aligned}$$

- Hence, a complementary relationship exists between a function expressed in Minterms and Maxterms.
- Therefore, we can find logical expression in Minterms if the function's Maxterms are known, and vice versa.

Practice Question

Prove that $XY + XYZ + XYZ' + X'YZ = Y(X + Z)$

Practice Question

$$XY + XYZ + XY\bar{Z} + \bar{X}YZ$$

$$= XY(1 + Z) + XY\bar{Z} + \bar{X}YZ$$

$$= XY + XY\bar{Z} + \bar{X}YZ \quad \text{Theorem 2(a) : } [A + 1 = 1]$$

$$= XY(1 + \bar{Z}) + \bar{X}YZ \quad \text{Distributive}$$

$$= XY + \bar{X}YZ \quad \text{Theorem 2(a) : } [A + 1 = 1]$$

$$= Y(X + \bar{X}Z) \quad \text{Distributive}$$

$$= Y(X + Z) \quad \text{Theorem 5(a) : } [A + \bar{A}B = A + B]$$

Practice Question

Simplify **$AC + C(A + A'B)$**

Practice Question

$$\begin{aligned} AC + C(A + \bar{A}B) \\ &= AC + AC + \bar{A}BC \\ &= AC + \bar{A}BC \\ &= C(A + \bar{A}B) \\ &= C(A + B) \end{aligned}$$

Practice Question

Prove that

$$\overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} \overline{C} + A B \overline{C} = \overline{C} + \overline{A} \overline{B}$$

Practice Question

$$\begin{aligned} Y &= \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B \bar{C} \\ &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} B \bar{C} + A B \bar{C} + \bar{A} \bar{B} C \quad \text{rearranging terms} \\ &= \bar{B} \bar{C} (\bar{A} + A) + B \bar{C} (\bar{A} + A) + \bar{A} \bar{B} C \\ &= \bar{B} \bar{C} + B \bar{C} + \bar{A} \bar{B} C \quad \text{Postulate 5(a) : } [A + \bar{A} = 1] \\ &= \bar{C} (\bar{B} + B) + \bar{A} \bar{B} C \quad \text{Distributive} \\ &= \bar{C} + \bar{A} \bar{B} C \quad \text{Postulate 5(a) : } [A + \bar{A} = 1] \\ &= \bar{C} + \bar{A} \bar{B} \quad \text{Theorem 5(a) : } [A + \bar{A} B = A + B] \end{aligned}$$

Practice Question

Simplify

$$\overline{AB + \overline{A} + AB}$$

Prove that

$$AB + \overline{AC} + A\overline{B}C (AB + C) = 1$$

$$AB + \overline{AC} + A\overline{B}C (AB + C)$$

$$= AB + \overline{AC} + A\overline{A}\overline{B}BC + A\overline{B}CC \quad \text{Distributive}$$

$$= AB + \overline{AC} + A\overline{B}CC \quad \text{Postulate 5(b) : } [A \cdot \overline{A} = 0]$$

$$= AB + \overline{AC} + A\overline{B}C \quad \text{Theorem 1(b) : } [A \cdot A = A]$$

$$= AB + \overline{A} + \overline{C} + A\overline{B}C \quad \text{DeMorgan's Theorem 1 : } [\overline{AB} = \overline{A} + \overline{B}]$$

$$= \overline{A} + B + \overline{C} + A\overline{B}C \quad \text{Theorem 5(a) : } [A + \overline{A}B = A + B]$$

$$= \overline{A} + A\overline{B}C + B + \overline{C} \quad \text{Commutative}$$

$$= \overline{A} + \overline{B}C + B + \overline{C} \quad \text{Theorem 5(a) : } [A + \overline{A}B = A + B]$$

$$\text{Here } B = \overline{B}C$$

$$= \overline{A} + B + \overline{C} + \overline{B}C \quad \text{Commutative}$$

$$= \overline{A} + B + \overline{C} + \overline{B} \quad \text{Theorem 5(a) : } [A + \overline{A}B = A + B]$$

$$= \overline{A} + \overline{C} + 1 \quad \text{Postulate 5(a) : } [A + \overline{A} = 1]$$

$$= 1 \quad \text{Theorem 2(a) : } [A + 1 = 1]$$

Practice Question

$$Z = A + \overline{B} + C$$

a) $\overline{A + \overline{B} + C}$

b) $\overline{\overline{A} + B + \overline{C}}$

c) $\overline{\overline{A} \cdot B \cdot \overline{C}}$

d) $\overline{A \cdot \overline{B} \cdot C}$

Practice Question

$$Z = A + \overline{B} + C$$

a) $\overline{A + \overline{B} + C}$


b) $\overline{\overline{A} + B + \overline{C}}$

c) $\overline{\overline{A} \cdot B \cdot \overline{C}}$




d) $\overline{A \cdot \overline{B} \cdot C}$

Logic Gate Implement with NAND-NOR

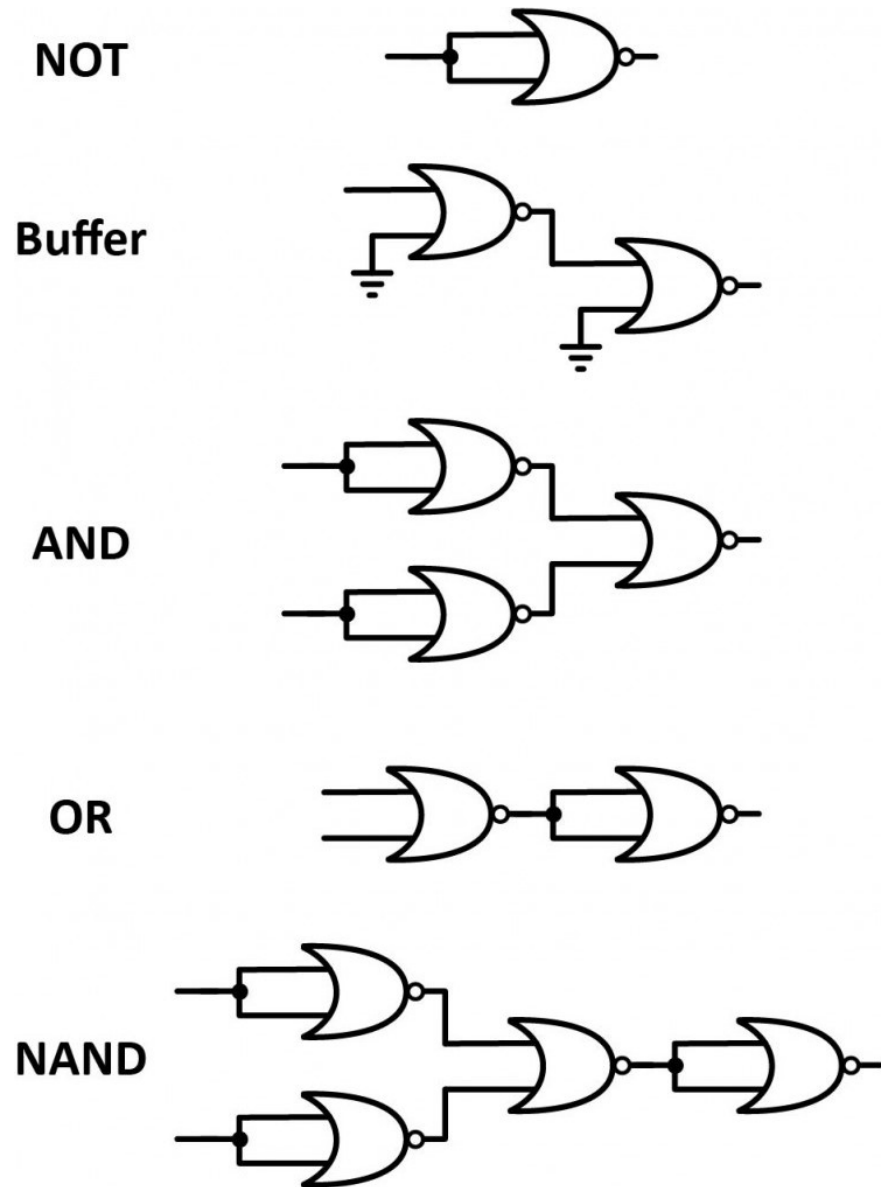

NOR

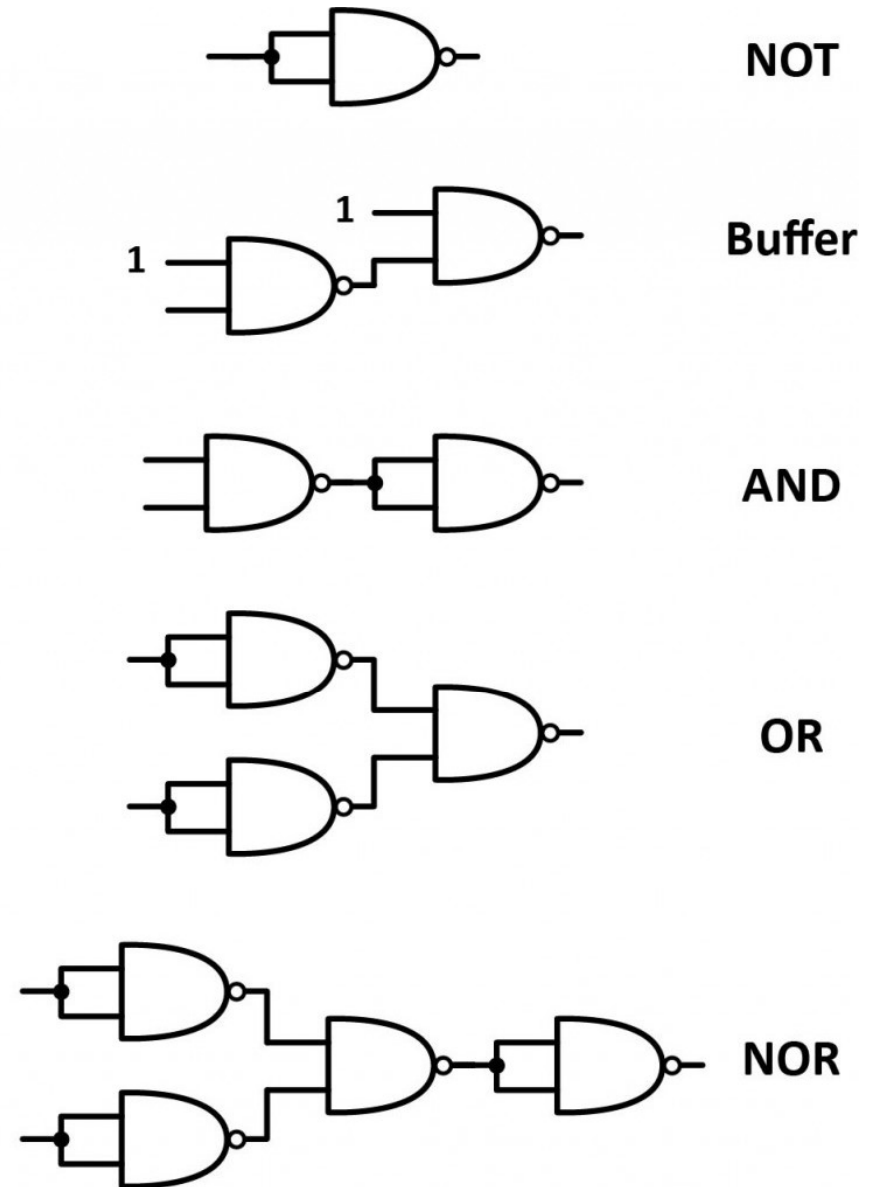

NAND

How many Boolean functions are possible from 2 input system?

1. n^{2^n}

2. 2^n

3. n^{n^2}

4. 2^{2^n}

How many Boolean functions are possible from 2 input system?

1. n^{2^n}

2. 2^n

3. n^{n^2}

4. 2^{2^n}



Quiz Time

How many Boolean functions are possible from 2 input system

- A. 2
- B. 4
- C. 8
- D. 16

Quiz Time

How many Boolean functions are possible from 2 input system

A. 2

B. 4

C. 8

D. 16



AB	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}
00	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
01	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
10	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
11	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

Answer: Option (4)

Any variable 'a' can have 2 value i.e, 0 or 1.

For 'n' variables there are 2^n entries in the truth table.

And each output of any particular row in the truth table can be 0 or 1.

Hence, we have 2^{2^n} different Boolean functions with n variables.

Let's understand with the help of an example -

Let's say there are 2 variables a, and b: **n = 2**

There are 2^2 entries in the truth table, and each entry can be 0 or 1

So, we have $2^{2^2} = 16$ different Boolean functions with 2 variables.

Function	x	0	0	1	1
	y	0	1	0	1
Constant 0	0	0	0	0	0
And	$x \cdot y$	0	0	0	1
x And Not y	$x \cdot \bar{y}$	0	0	1	0
x	x	0	0	1	1
Not x And y	$\bar{x} \cdot y$	0	1	0	0
y	y	0	1	0	1
Xor	$x \cdot \bar{y} + \bar{x} \cdot y$	0	1	1	0
Or	$x + y$	0	1	1	1
Nor	$\overline{x + y}$	1	0	0	0
Equivalence	$x \cdot y + \bar{x} \cdot \bar{y}$	1	0	0	1
Not y	\bar{y}	1	0	1	0
If y then x	$x + \bar{y}$	1	0	1	1
Not x	\bar{x}	1	1	0	0
If x then y	$\bar{x} + y$	1	1	0	1
Nand	$\overline{x \cdot y}$	1	1	1	0
Constant 1	1	1	1	1	1