

Tutorial Sheet-5 (Unit-2)

Question-1:

Given a BJT with a base-emitter voltage drop (V_{BE}) of 0.7 V and a collector current (I_C) of 2 mA, determine the values of base current (I_B) and collector-emitter voltage drop (V_{CE}) for the transistor in the active region. Assume $\beta = 100$.

Solution:

1. Calculate I_B using $I_C = \beta \times I_B$:

$$I_B = \frac{I_C}{\beta} = \frac{2 \text{ mA}}{100} = 0.02 \text{ mA} = 20 \mu\text{A}$$

2. Determine V_{CE} using $V_{CE} = V_{CC} - (I_C \times R_C)$, where V_{CC} is the collector supply voltage and R_C is the collector resistor. For simplicity, let's assume $V_{CC} = 10 \text{ V}$ and $R_C = 4 \text{ k}\Omega$:

$$V_{CE} = 10 \text{ V} - (2 \text{ mA} \times 4 \text{ k}\Omega) = 10 \text{ V} - 8 \text{ V} = 2 \text{ V}$$

So, $I_B = 20 \mu\text{A}$ and $V_{CE} = 2 \text{ V}$.

Question-2:

For a BJT with $\beta = 150$, if the base current (I_B) is $40 \mu\text{A}$, calculate the collector current (I_C) and the current gain (α).

Solution:

1. Use the current gain equation $I_C = \beta \times I_B$:

$$I_C = 150 \times 40 \mu\text{A} = 6 \text{ mA}$$

2. Calculate α using $\alpha = \frac{I_C}{I_E}$, where I_E is the emitter current. Since $I_E = I_C + I_B$:

$$I_E = I_C + I_B = 6 \text{ mA} + 40 \mu\text{A} = 6.04 \text{ mA}$$

$$\alpha = \frac{6 \text{ mA}}{6.04 \text{ mA}} \approx 0.993$$

So, $I_C = 6 \text{ mA}$ and $\alpha \approx 0.993$.

Question-3:

For an inverting amplifier with an input resistor (R_1) of $10 \text{ k}\Omega$ and a feedback resistor (R_f) of $20 \text{ k}\Omega$, calculate the voltage gain (A_v).

Solution:

The voltage gain for an inverting amplifier is given by $A_v = -\frac{R_f}{R_1}$.

$$A_v = -\frac{20 \text{ k}\Omega}{10 \text{ k}\Omega} = -2$$

So, the voltage gain is -2 .

Question-4:

Given a BJT with a collector current (I_C) of 2 mA, a base current (I_B) of 20 μ A, and a collector-emitter voltage drop (V_{CE}) of 5 V, calculate the current gain (β) and the transistor power dissipation (P_{diss}).

Solution:

1. Calculate β using the formula $\beta = \frac{I_C}{I_B}$:
$$\beta = \frac{2 \text{ mA}}{20 \mu\text{A}} = 100$$
2. Calculate the power dissipation using $P_{diss} = V_{CE} \times I_C$:
$$P_{diss} = 5 \text{ V} \times 2 \text{ mA} = 10 \text{ mW}$$

So, $\beta = 100$ and $P_{diss} = 10 \text{ mW}$.

Question-5:

For a non-inverting amplifier with an input resistor (R_1) of 5 k Ω and a feedback resistor (R_f) of 15 k Ω , calculate the voltage gain (A_v).

Solution:

The voltage gain for a non-inverting amplifier is given by $A_v = 1 + \frac{R_f}{R_1}$.


$$A_v = 1 + \frac{15 \text{ k}\Omega}{5 \text{ k}\Omega} = 1 + 3 = 4$$

So, the voltage gain is 4.

Question-6:

In the circuit shown in the figure, the input voltage V_i is 20 V, $V_{BE} = 0$ V and $V_{CE} = 0$ V. What are the values of I_B , I_C , β ?

Solution:

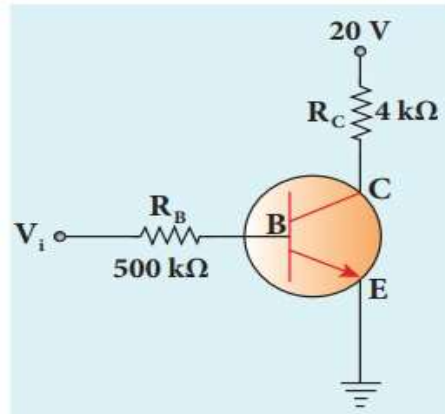

$$I_B = \frac{V_i}{R_B} = \frac{20\text{ V}}{500\text{ k}\Omega} = 40\text{ }\mu\text{A} \quad [\because V_{BE} = 0\text{ V}]$$

$$I_C = \frac{V_{CC}}{R_C} = \frac{20\text{ V}}{4\text{ k}\Omega} = 5\text{ mA} \quad [\because V_{CE} = 0\text{ V}]$$

$$\beta = \frac{I_C}{I_B} = \frac{5\text{ mA}}{40\text{ }\mu\text{A}} = 125$$

HomeWork

Question-1:

In a transistor connected in the common base configuration, $\alpha=0.95$, $I_E=1\text{ mA}$. Calculate the values of I_C and I_B .

Solution: $\alpha = I_C/I_E$


$$I_C = \alpha I_E = 0.95 \times 1 = 0.95\text{ mA}$$

$$I_E = I_B + I_C$$

$$\therefore I_B = I_C - I_E = 1 - 0.95 = 0.05\text{ mA}$$

Question-2:

In a BJT, the emitter current is 8 mA and $I_B = I_C/100$. Determine I_C and I_E .

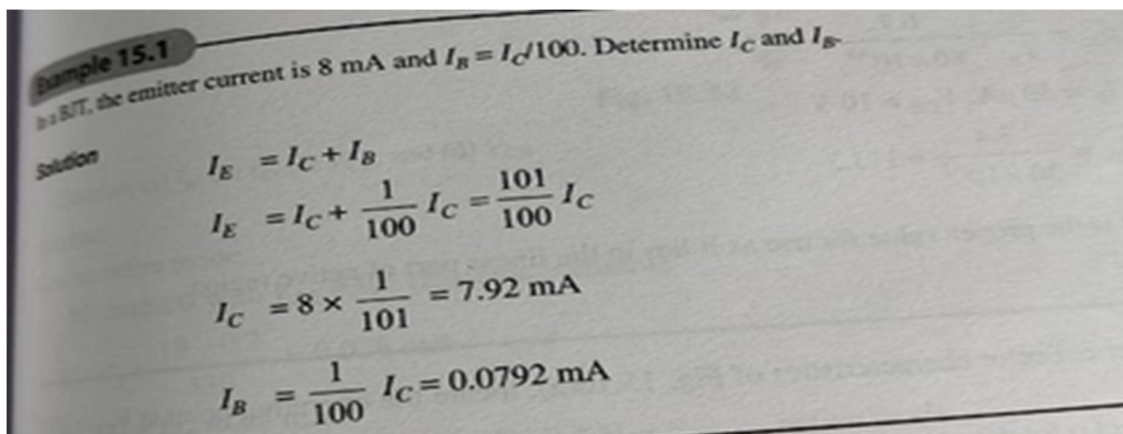

Example 15.1
In a BJT, the emitter current is 8 mA and $I_B = I_C/100$. Determine I_C and I_E .

Solution

$$I_E = I_C + I_B$$
$$I_E = I_C + \frac{1}{100} I_C = \frac{101}{100} I_C$$
$$I_C = 8 \times \frac{1}{101} = 7.92\text{ mA}$$
$$I_B = \frac{1}{100} I_C = 0.0792\text{ mA}$$

Question-3:

Find the output voltage for the circuit shown in Fig. below.

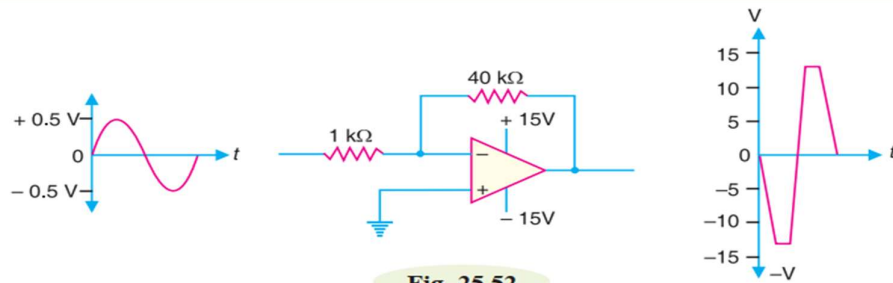


Fig. 25.52

Solution. Voltage gain, $A_{CL} = -\frac{R_f}{R_i} = -\frac{40 \text{ k}\Omega}{1 \text{ k}\Omega} = -40$

Question-4:

For the noninverting amplifier circuit shown in Fig., find peak-to-peak output voltage.

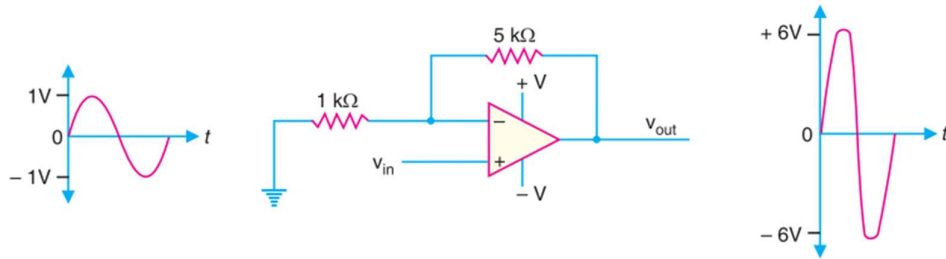


Fig. 25.59

Solution. The input signal is 2 V peak-to-peak.

$$\text{Voltage gain, } A_{CL} = 1 + \frac{R_f}{R_i} = 1 + \frac{5 \text{ k}\Omega}{1 \text{ k}\Omega} = 1 + 5 = 6$$

$$\therefore \text{Peak-to-peak output voltage} = A_{CL} \times v_{inpp} = 6 \times 2 = \mathbf{12 \text{ V}}$$

Question-5:

Consider an op-amp subtractor circuit with two input voltages, $V_1 = 3 \text{ V}$ and $V_2 = 1 \text{ V}$, and resistors $R_1 = 5 \text{ k}\Omega$ and $R_2 = 2 \text{ k}\Omega$ in the feedback loop.

Determine the output voltage (V_{out}).

Solution:

The output voltage (V_{out}) in an op-amp subtractor circuit is given by the formula:

$$V_{out} = -\left(\frac{R_f}{R_1} \cdot V_1 - \frac{R_f}{R_2} \cdot V_2\right)$$

In this case, R_f is the feedback resistor, which is $R_f = R_2 = 2 \text{ k}\Omega$.

MCQs

Q1. In a common-emitter configuration, the phase difference between the input and output signals is:

- a. 0 degrees
- b. 45 degrees
- c. 90 degrees
- d. 180 degrees

Answer: d. 180 degrees

2. The current gain (β) of a BJT in the common-emitter configuration is given by:

- a. I_E/I_B
- b. I_B/I_E
- c. I_C/I_B
- d. I_B/I_C

Answer: c. I_C/I_B

3. In a BJT, the region of operation where both the emitter-base junction and the collector-base junction are forward biased is called:

- a. Active region
- b. Cutoff region
- c. Saturation region
- d. Breakdown region

Answer: c. Saturation region

4. In a BJT, the majority charge carriers in the base region of an NPN transistor are:

- a. Electrons
- b. Holes
- c. Ions
- d. None

Answer: b. Holes

5. For a BJT to operate in the active region, the emitter-base junction must be:

- a. Forward biased, and the collector-base junction must be forward biased
- b. Reverse biased, and the collector-base junction must be forward biased
- c. Forward biased, and the collector-base junction must be reverse biased
- d. Reverse biased, and the collector-base junction must be reverse biased

Answer: c. Forward biased, and the collector-base junction must be reverse biased

6. The primary difference between enhancement-mode and depletion-mode MOSFETs is:

- a. The type of substrate used
- b. The gate structure

- c. The threshold voltage
- d. The channel formation

Answer: d. The channel formation

7. In an n-channel MOSFET, the channel is formed when:

- a. The gate-source voltage is less than the threshold voltage
- b. The gate-source voltage is equal to the threshold voltage
- c. The gate-source voltage is greater than the threshold voltage
- d. The gate-source voltage is zero

Answer: c. The gate-source voltage is greater than the threshold voltage

8. In a MOSFET, the region where the drain current is almost constant and independent of the drain-source voltage is called:

- a. Ohmic region
- b. Active region
- c. Saturation region
- d. Cutoff region

Answer: c. Saturation region

9. The primary function of the gate terminal in a MOSFET is to:

- a. Control the source voltage
- b. Control the drain current
- c. Control the body current
- d. Provide a reference voltage

Answer: b. Control the drain current

10. In a MOSFET, the body effect refers to the:

- a. Effect of the gate voltage on the body
- b. Effect of the source voltage on the body
- c. Effect of the drain voltage on the body
- d. Effect of the body voltage on the threshold voltage

Answer: d. Effect of the body voltage on the threshold voltage

Q11. In a MOSFET, the polarity of the inversion layer is the same as that of the

- a. Charge on the gate electrode
- b. Minority carriers in the drain
- c. Majority carriers in the substrate
- d. Majority carriers in the source

Answer: d

Q 12. The threshold voltage of an n-channel MOSFET can be increased by

- a. Increasing the channel dopant concentration.
- b. Reducing the channel dopant concentration.

- c. Reducing the gate oxide thickness.
- d. Reducing the channel length.

Answer: a

Q13. The transit time of the current carriers through the channel of an FET decides..... Characteristics

Answer: Switching

Q14. When a bipolar junction transistor is operating in the saturation mode, which one of the following is TRUE about the state of its collector-base (CB) and base-emitter (BE) junctions?

- a. The CB junction is forward biased, and the BE junction is reverse biased.
- b. The CB junction is reverse biased, and the BE junction is forward biased.
- c. Both CB and BE junctions are forward biased
- d. Both CB and BE junctions are reverse biased

Answer: c

15. In an ideal op-amp, the open-loop gain is:

- a. 1
- b. 100
- c. Infinite
- d. Zero

Answer: c. Infinite

16. In an inverting amplifier configuration, the input signal is applied to:

- a. The non-inverting terminal
- b. The inverting terminal
- c. Both terminals
- d. The output terminal

Answer: b. The inverting terminal

17. The primary difference between inverting and non-inverting op-amp configurations is:

- a. The type of feedback used
- b. The phase relationship between input and output
- c. The gain of the amplifier
- d. The bandwidth of the amplifier

Answer: b. The phase relationship between input and output

18. In an op-amp integrator circuit, the output voltage is proportional to:

- a. The integral of the input voltage
- b. The derivative of the input voltage
- c. The sum of the input voltages
- d. The difference between the input voltages

Answer: a. The integral of the input voltage